



山东科技大学
济南校区

SHANDONG UNIVERSITY OF SCIENCE & TECHNOLOGY IN JINAN



Operational Amplifiers

Kong Yingying

Shandong University of Science & Technology (Jinan Campus)



Contents

➤ Differential Amplifier Circuits

➤ Op-Amp Basics

➤ Operation Circuits

➤ Active Filters

➤ Comparator Unit Operation


➤ Schmitt Trigger

➤ Op-Amp Specification

Applications



Introduction

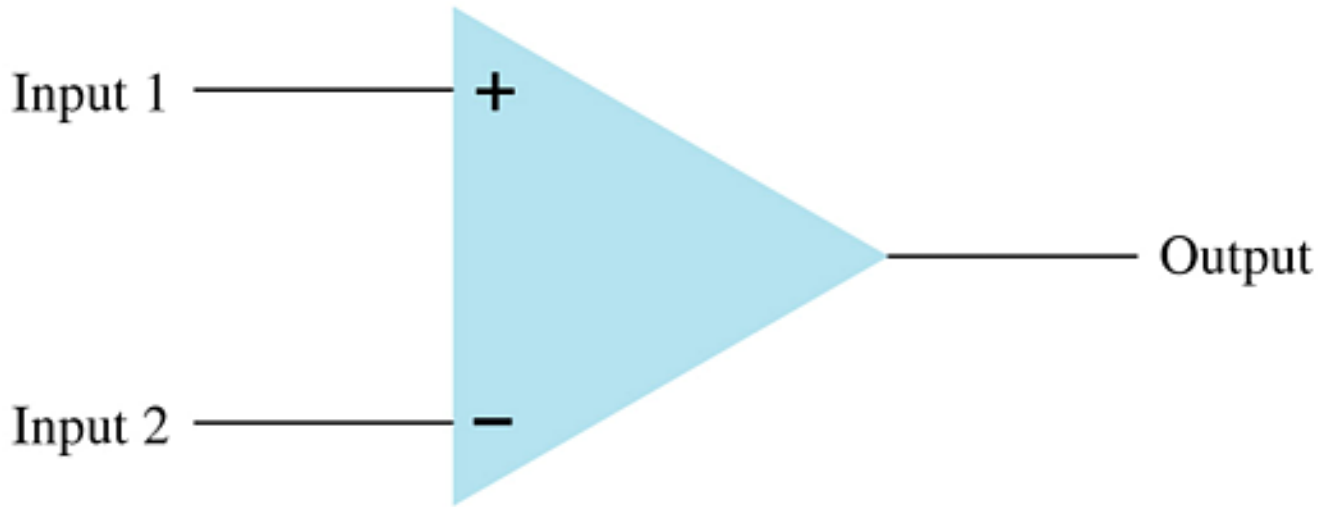


Operational amplifier or op-amp, is a **very high gain differential amplifier with **a high input impedance** and **low output impedance**.**








Introduction

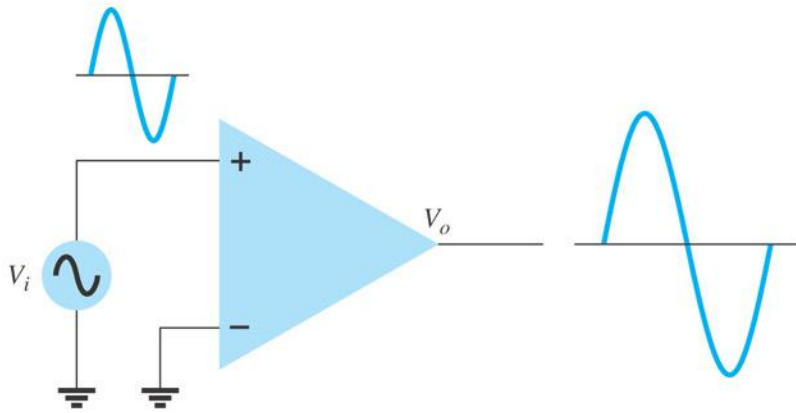

(a)

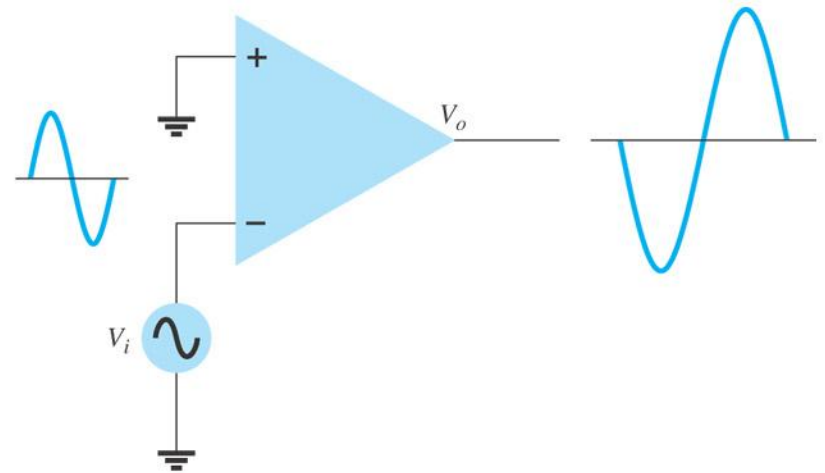


(b)


Single-ended operation



Introduction

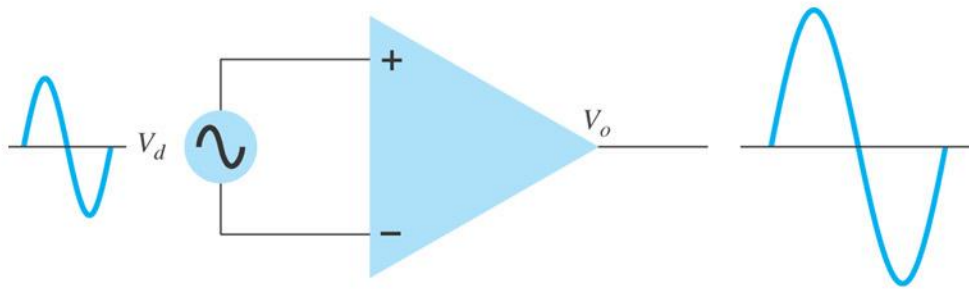

(a)

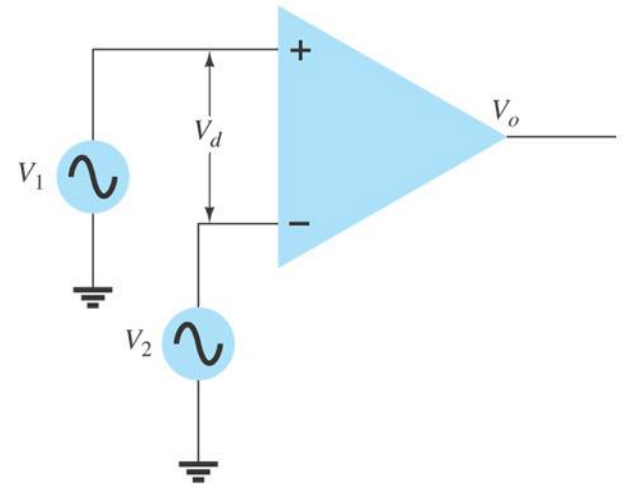


(b)

Double-ended (differential) operation.




Introduction

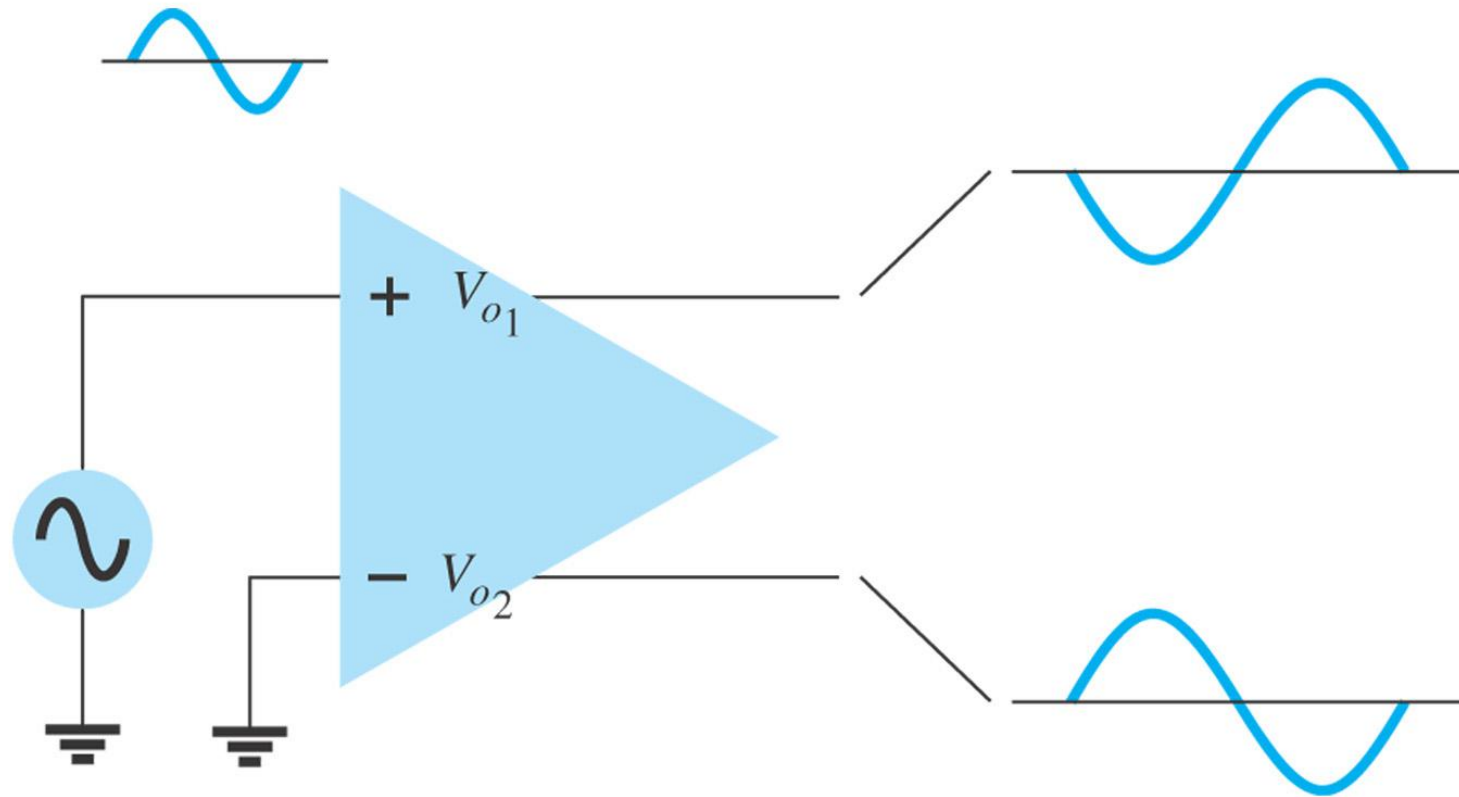

Double-ended output with single-ended input




Introduction

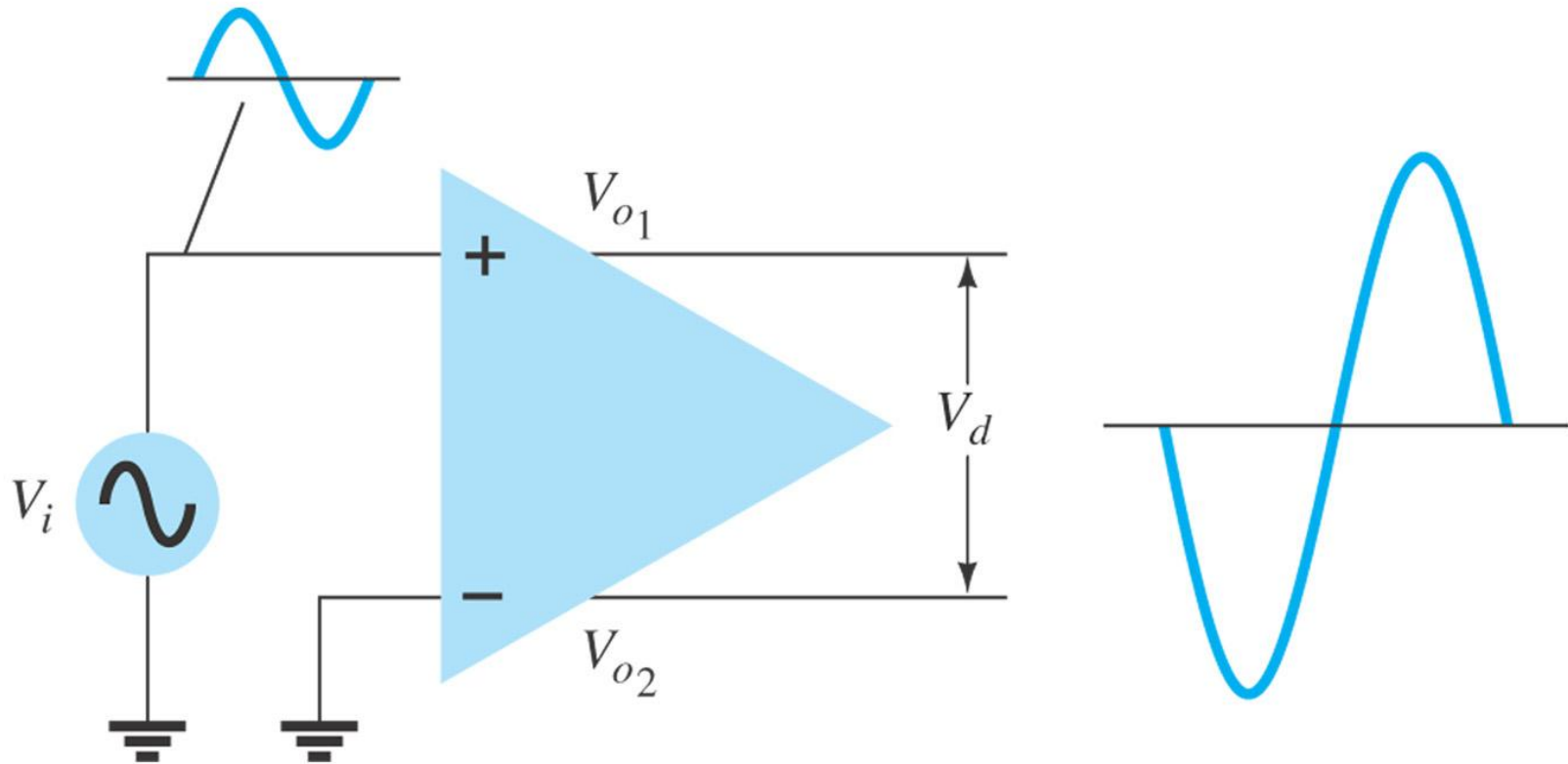

Double-ended output




Introduction

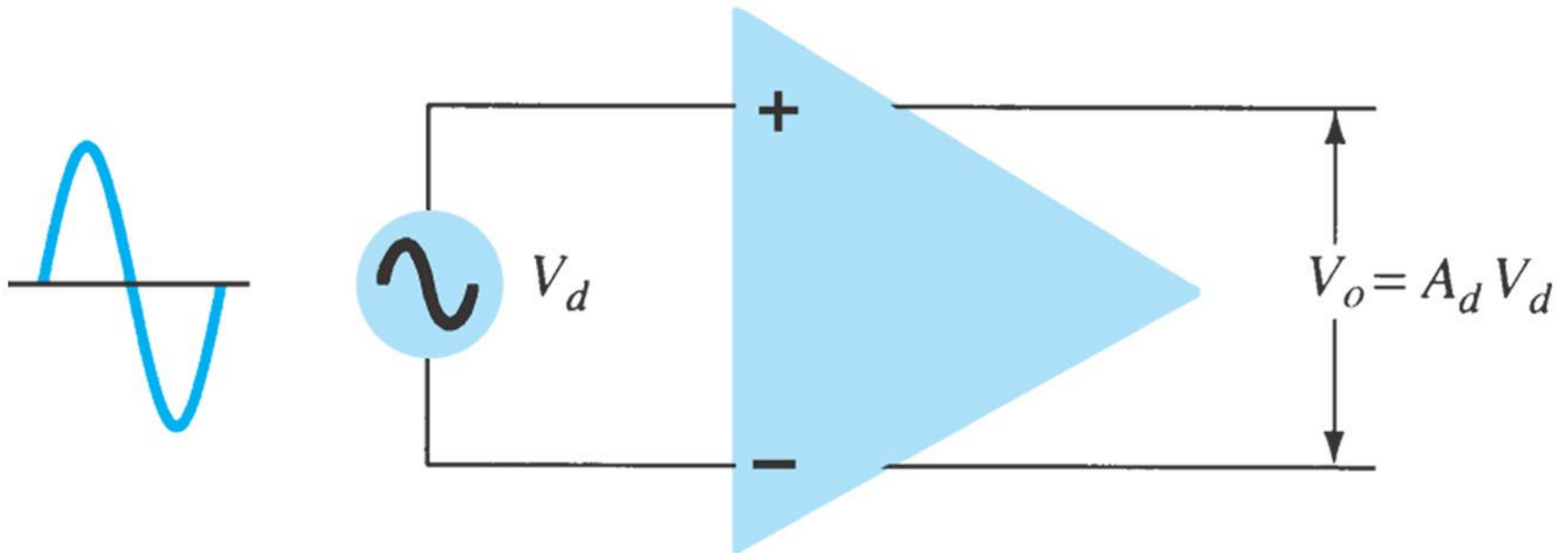

Differential-input, differential-output operation



Introduction

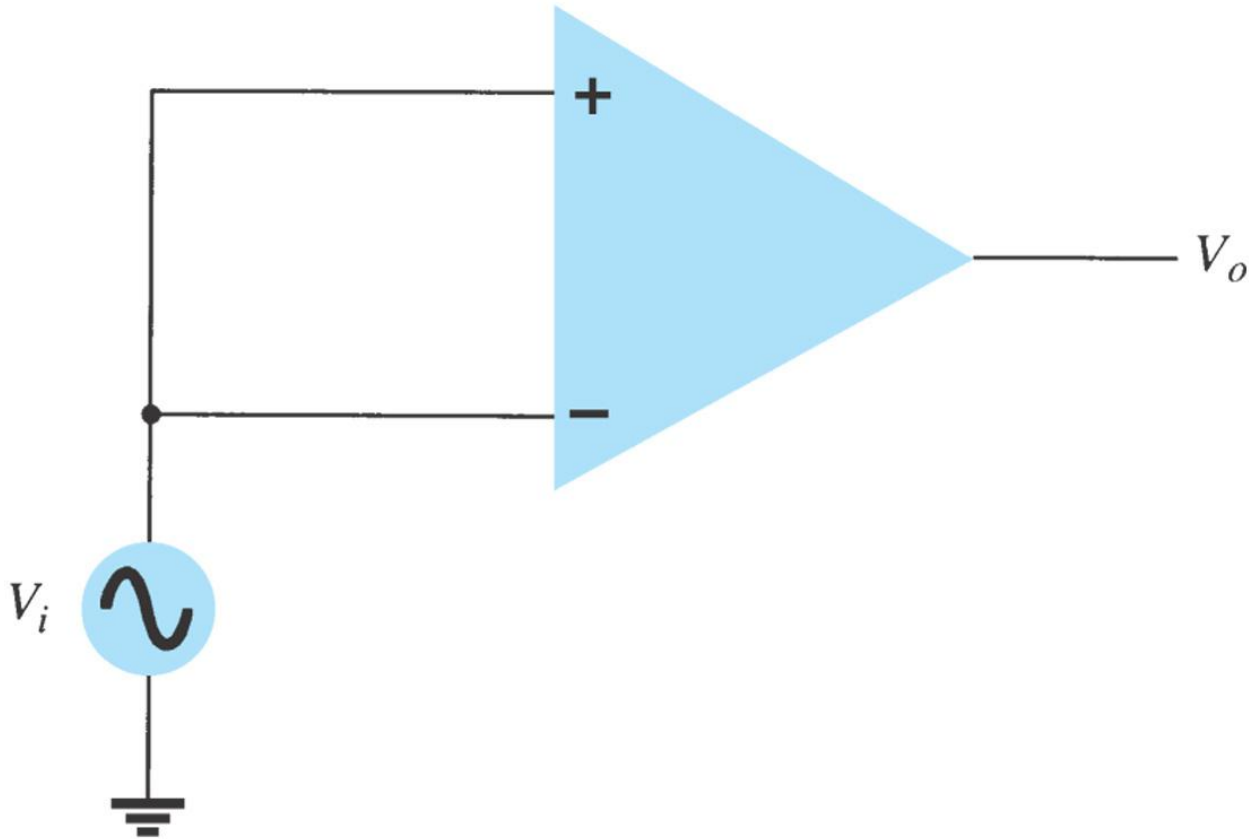


Common-mode operation



Differential Amplifier Circuits

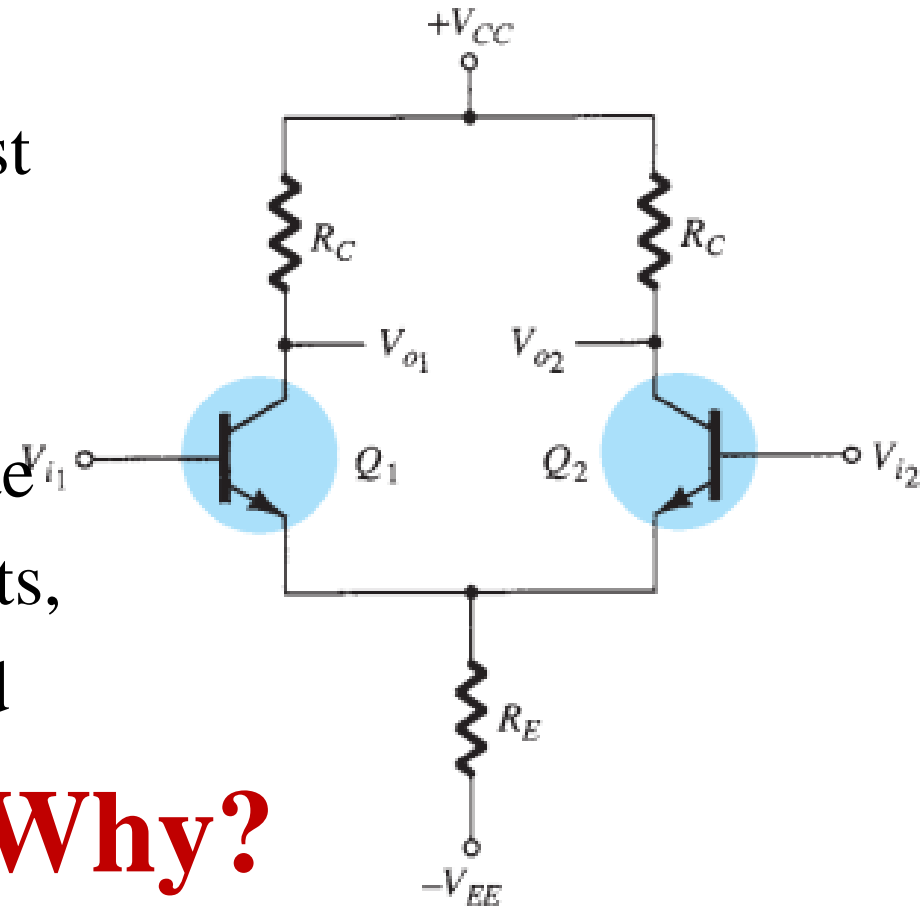- The differential amplifier (pair) configuration is the most widely used building block in analog IC design.
- The circuit has two separate inputs and two separate outputs, and the emitters are connected together.
- Two separate voltage supplies.




Why?

Basic differential amplifier circuit




Differential Amplifier Circuits

Reasons:

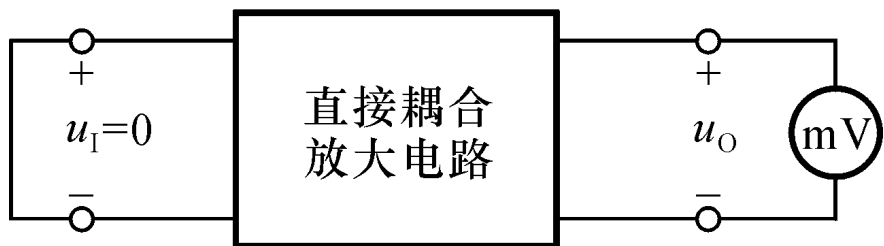

(a)

$$v_i = 0$$
$$v_o \neq 0$$

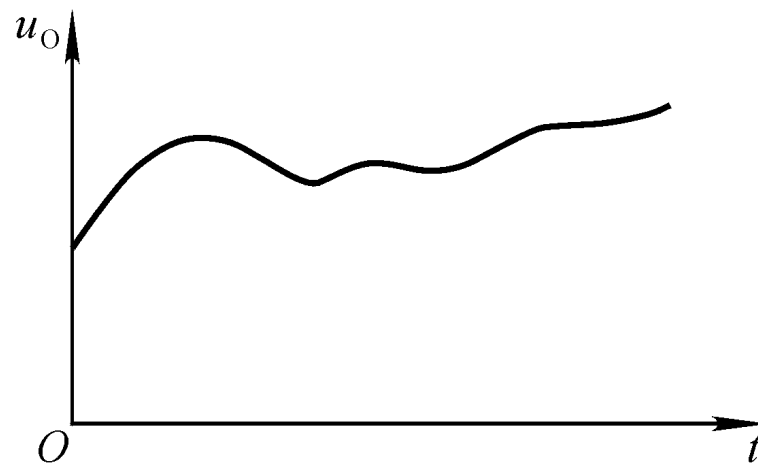



(b)

Direct coupling between signal source and amplifier will easily cause **Temperature Drift** (**Zero Drift**).


What shall we do?



Differential Amplifier Circuits

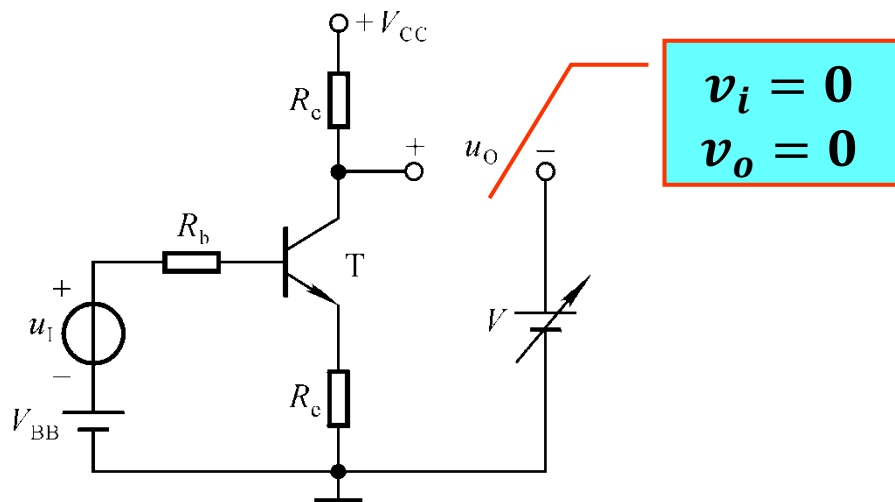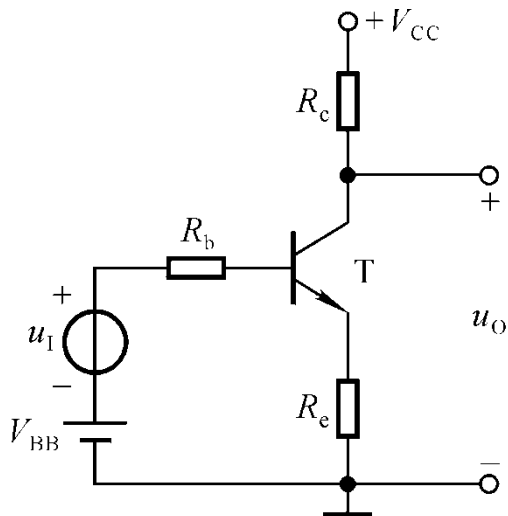

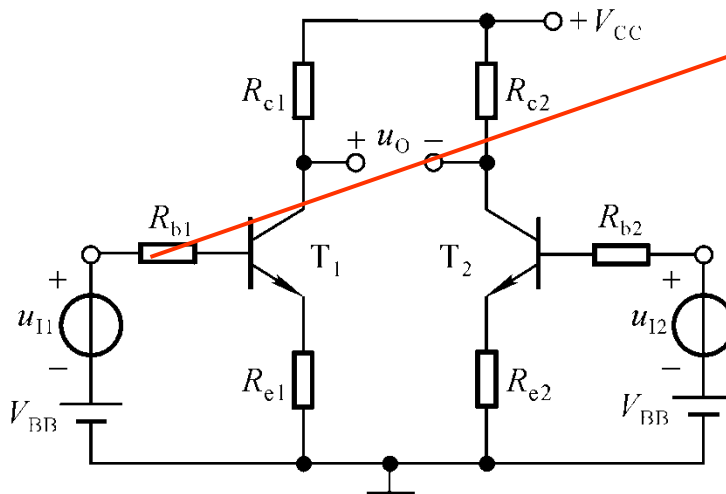*T1 and T2 are
identical transistors*
 $R_{b1} = R_{b2}, R_{c1} = R_{c2},$
 $R_{e1} = R_{e2}$




$v_{i1} = v_{i2}$

**Common-mode
input signal**


$v_o = 0$




Differential Amplifier Circuits

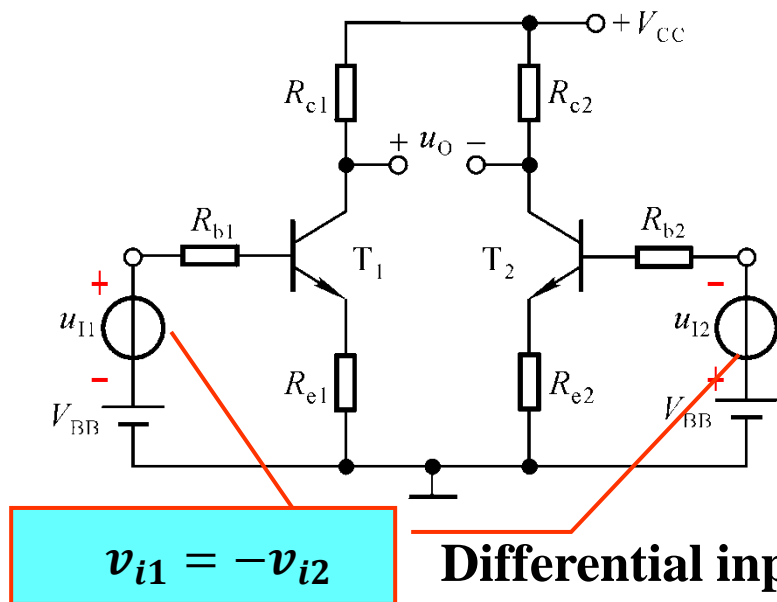

Differential input signal

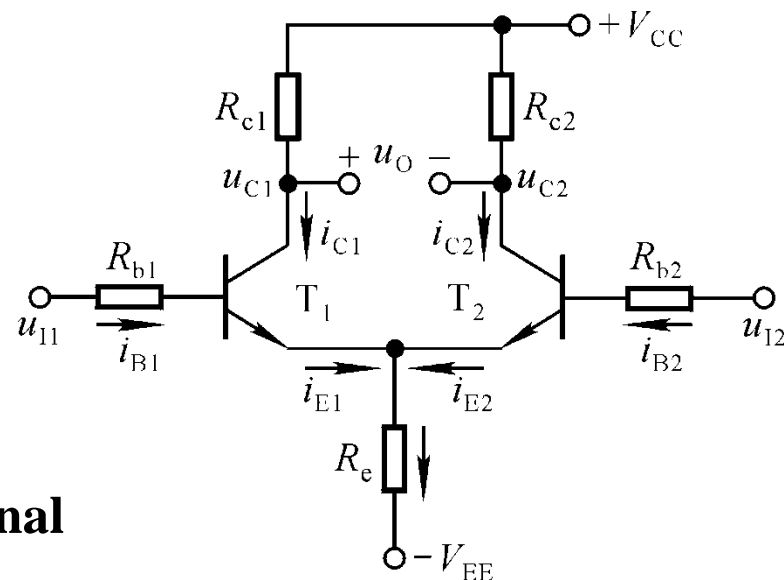

Typical Circuit

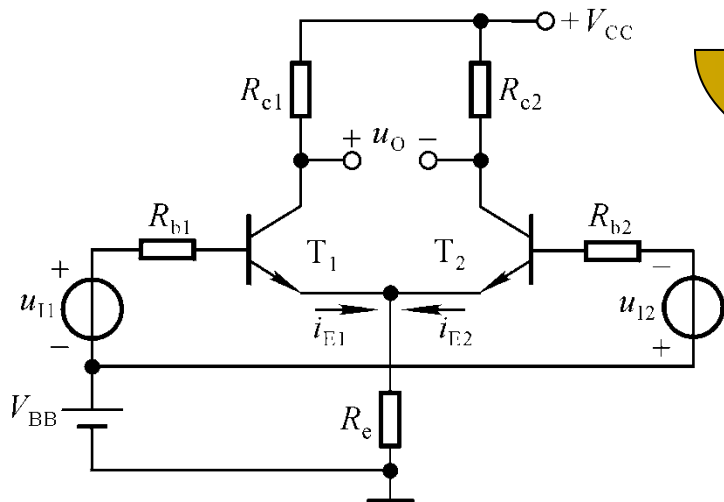


➤ One goal of the design of differential amplifiers is to minimize the effect of the common-mode input signal.



Differential Amplifier Circuits

DC Bias:

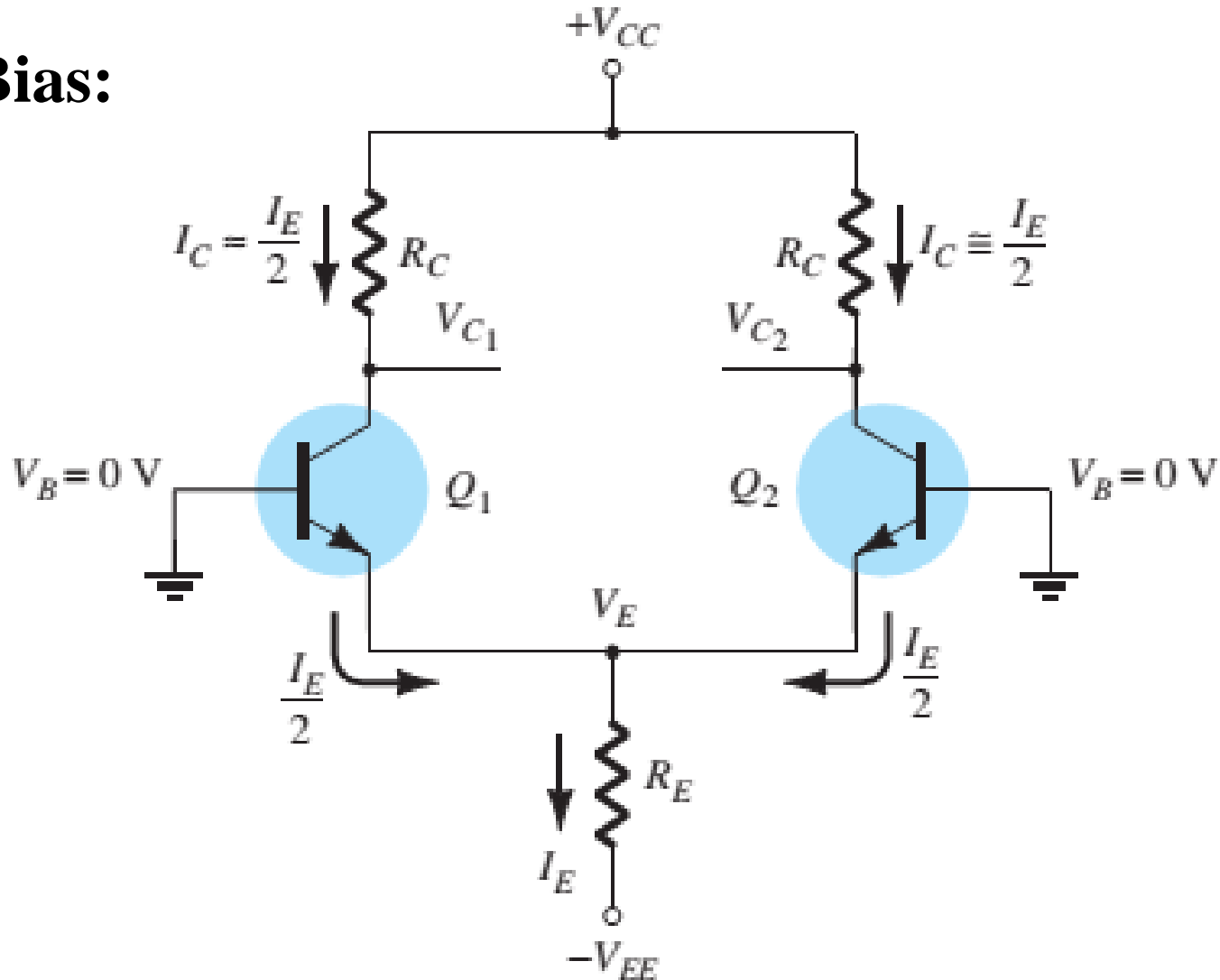




Differential Amplifier Circuits

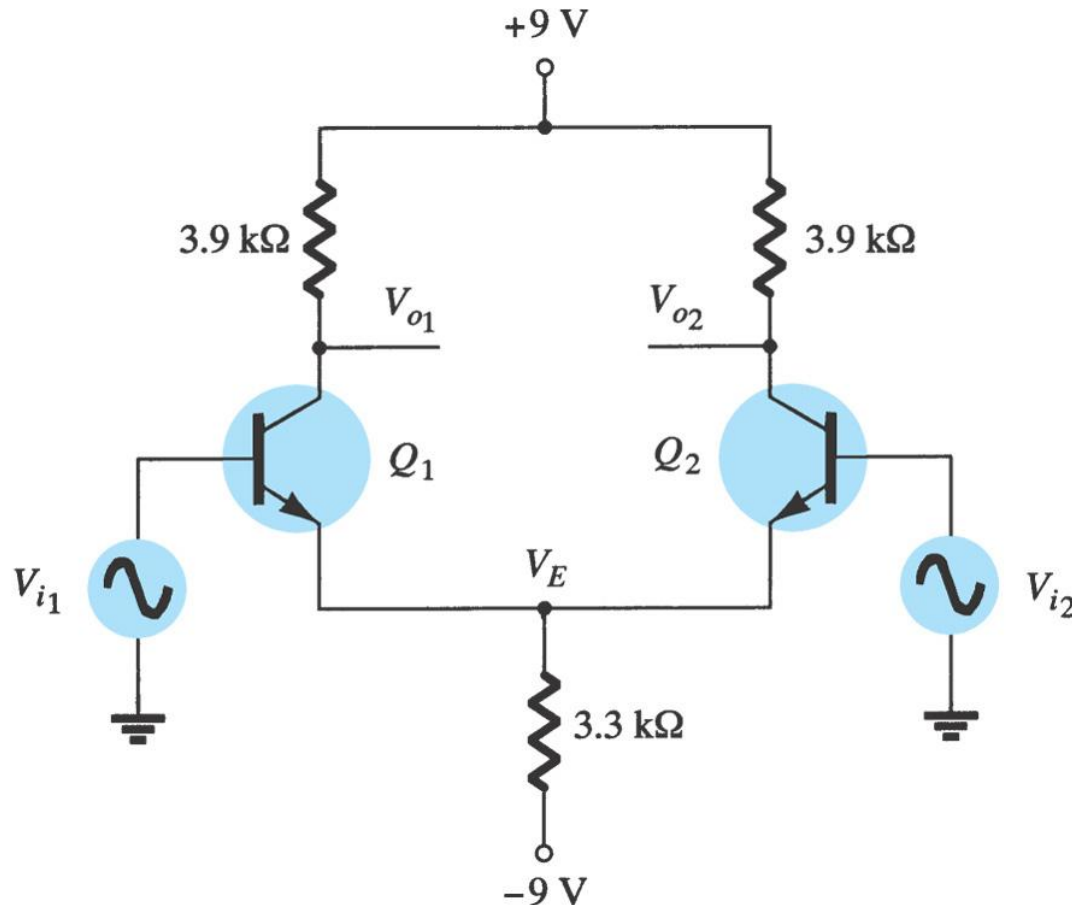Example:

Calculate the dc voltages and currents in the circuit






Differential Amplifier Circuits

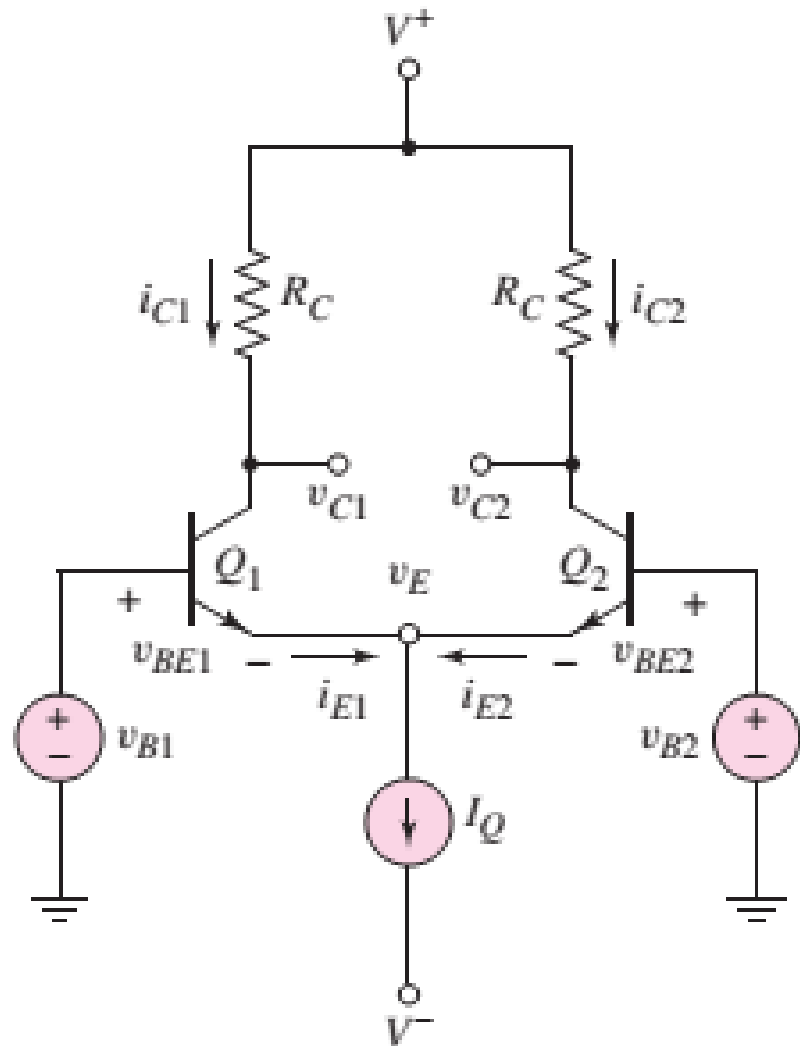Exercise:

For the differential amplifier, the parameters are: $V^+ = 10V$, $V^- = -10V$, $I_Q = 1mA$, $R_C = 10k\Omega$, $\beta = 200$. Find the voltages V_E , V_{C1} , V_{C2} , for $v_{B1} = v_{B2} = 0$.






AC Operation of Diff-Amp

Double-Ended AC Voltage Gain

$$\beta_1 = \beta_2 = \beta$$

$$v_{i1} = -v_{i2} = \frac{1}{2} v_{id}$$


$$v_{id} = v_{i1} - v_{i2}$$

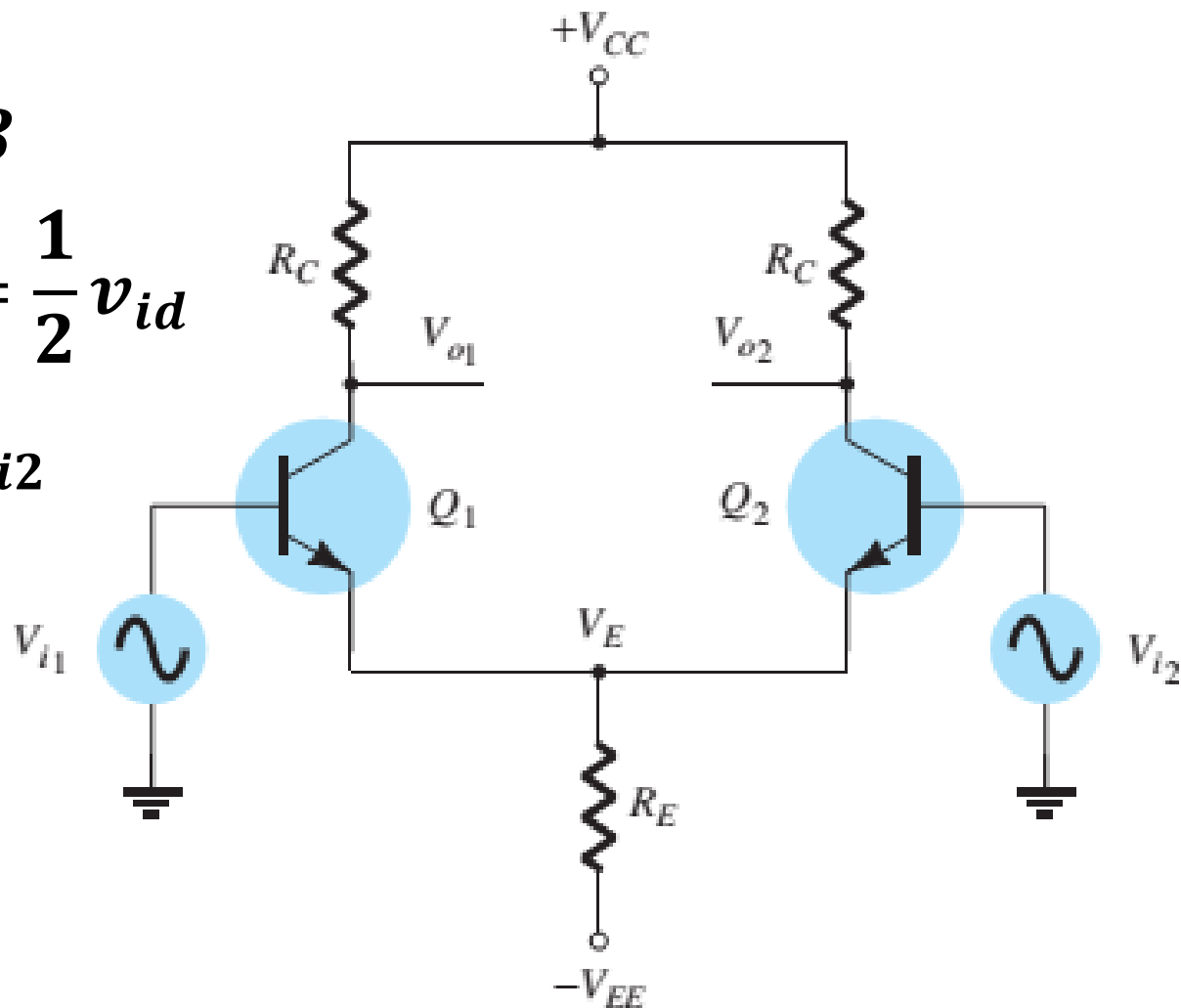



AC Operation of Diff-Amp

Double-Ended AC Voltage Gain

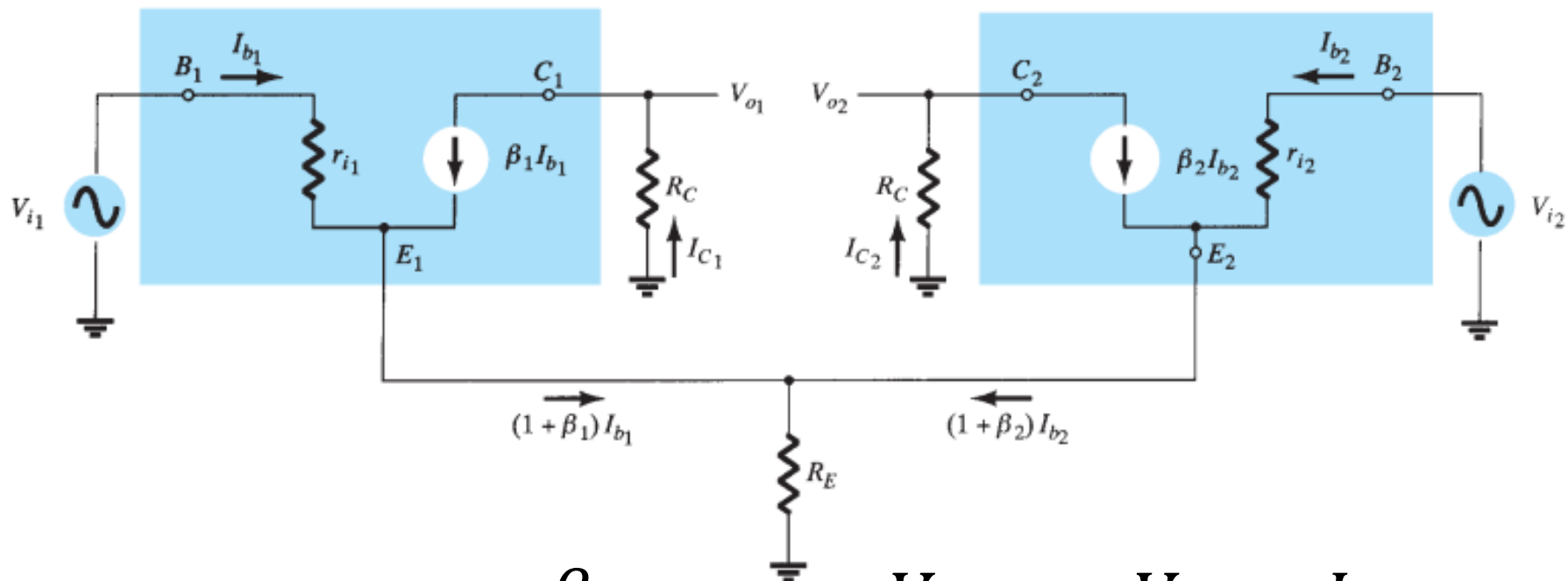

$$r_{i1} = r_{i2} = r_i = \beta r_e$$


$$V_{i1} = -V_{i2} = I_b r_i$$

$$I_{b1} = -I_{b2} = I_b$$

$$V_{id} = 2I_b r_i = 2\beta I_b r_e$$



AC Operation of Diff-Amp

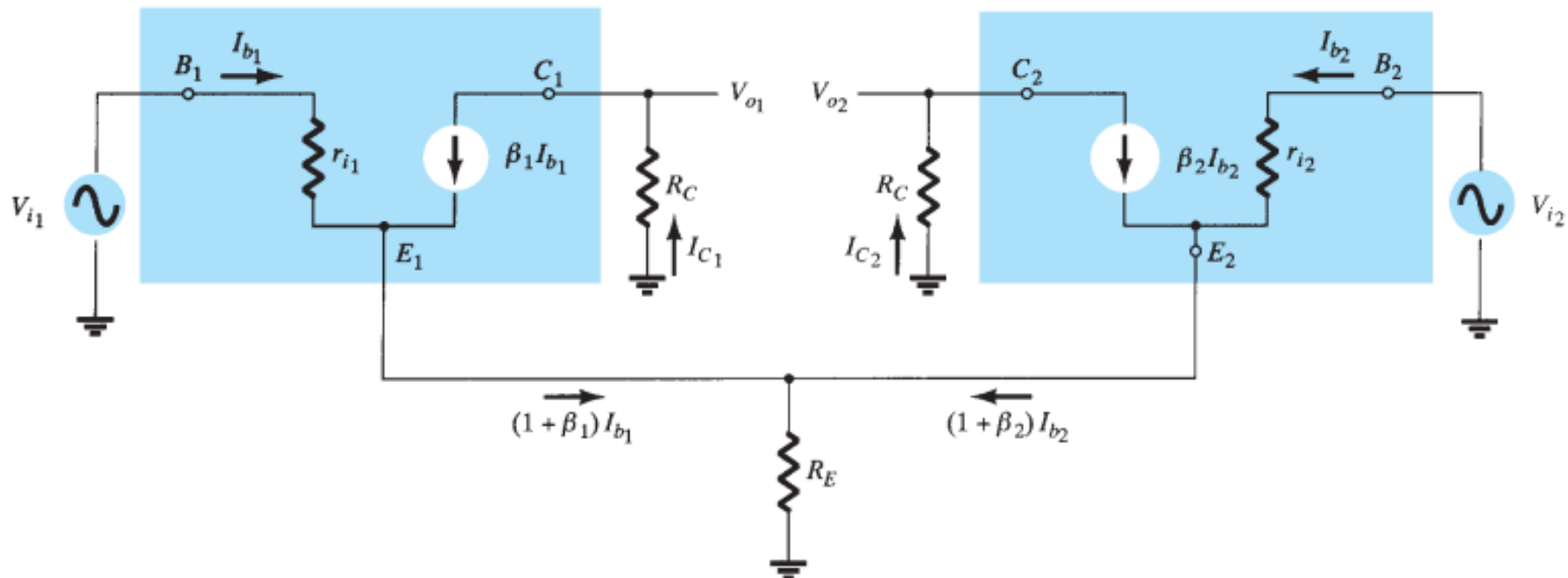

$$V_{o1} = -I_{c1}R_C = -\beta I_b R_C$$


$$V_{o2} = -I_{c2}R_C = \beta I_b R_C$$

$$V_o = V_{o1} - V_{o2} = -2\beta I_b R_C$$

$$A_{vd} = \frac{V_o}{V_{id}} = \frac{-2\beta I_b R_C}{2\beta I_b r_e} = -\frac{R_C}{r_e}$$



AC Operation of Diff-Amp

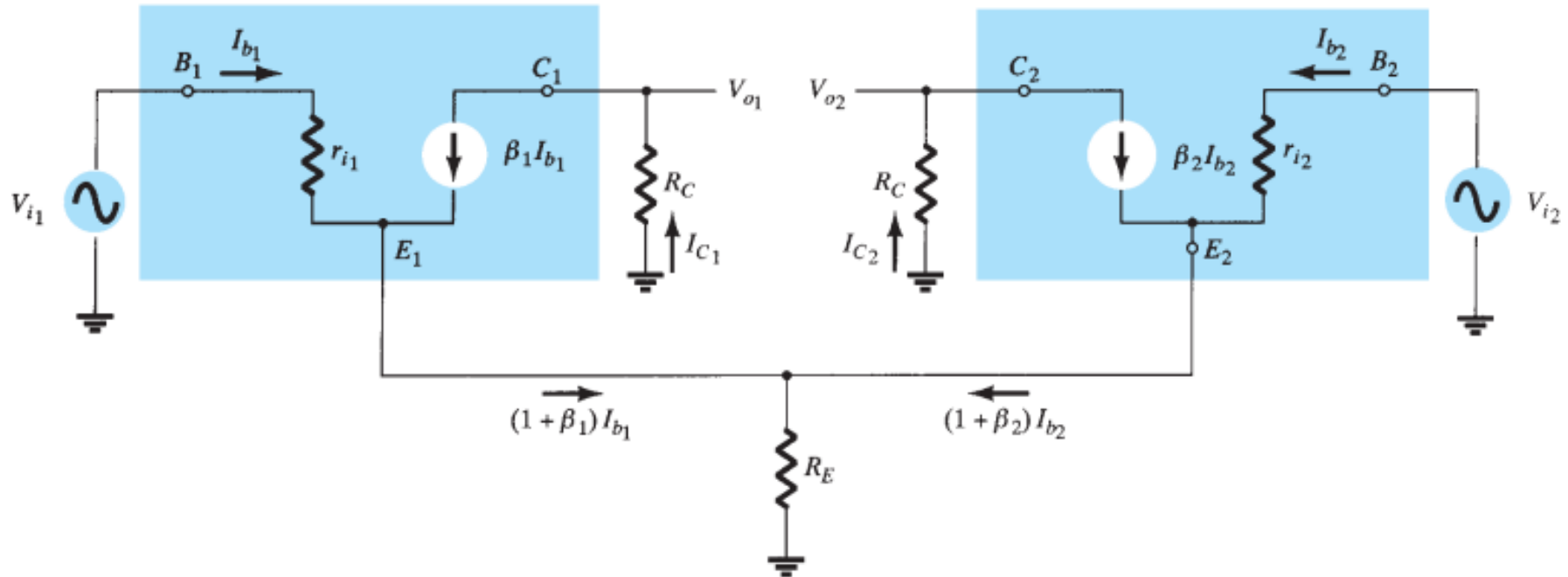

If the output signal is from collector 1 or collector 2 ?


$$A_{v1} = \frac{V_{o1}}{V_{id}} = \frac{-\beta I_b R_C}{2\beta I_b r_e} = -\frac{R_C}{2r_e}$$

$$A_{v2} = \frac{V_{o2}}{V_{id}} = \frac{\beta I_b R_C}{2\beta I_b r_e} = \frac{R_C}{2r_e}$$



AC Operation of Diff-Amp


Single-Ended AC Voltage Gain

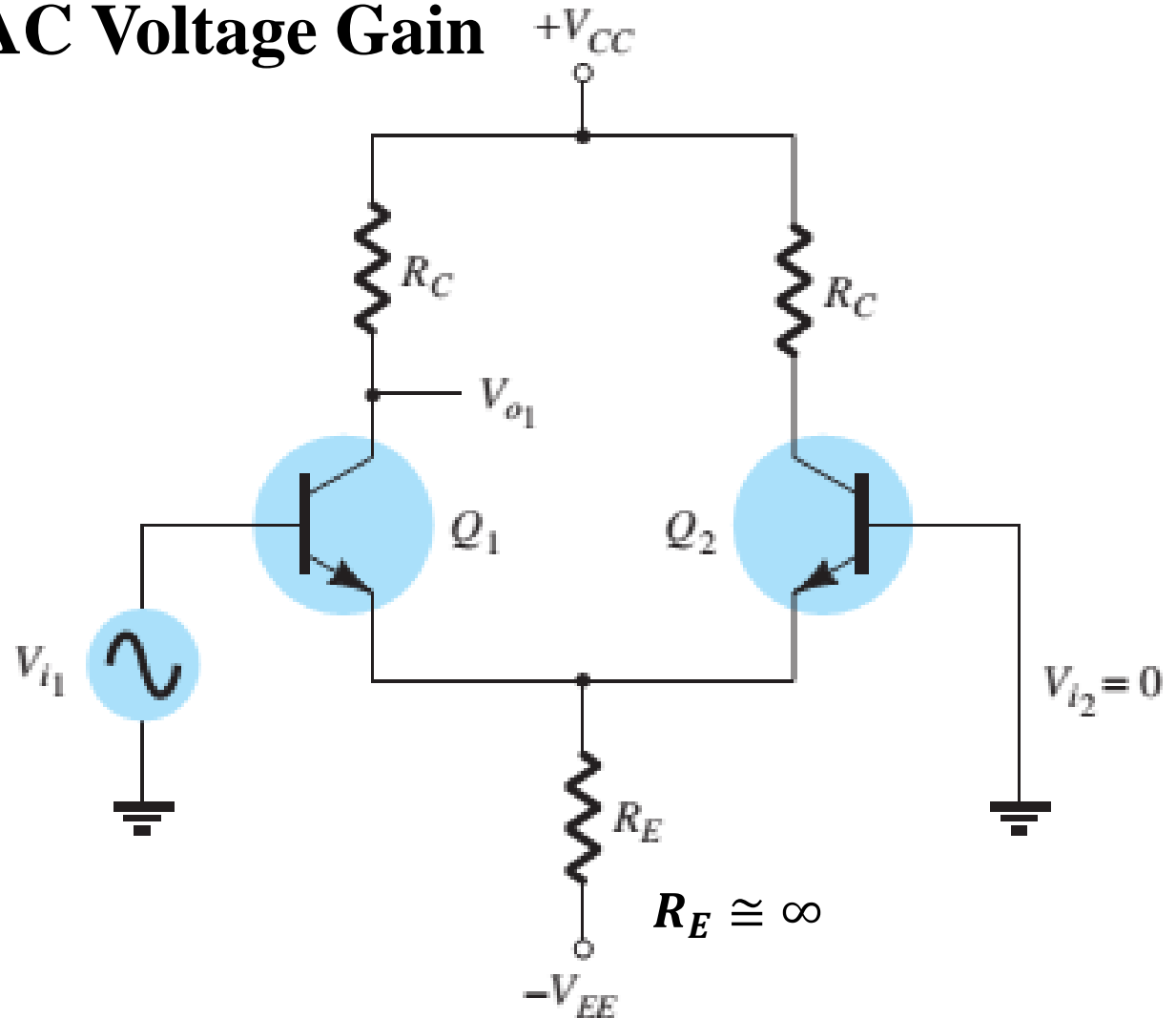



AC Operation of Diff-Amp

Single-Ended AC Voltage Gain

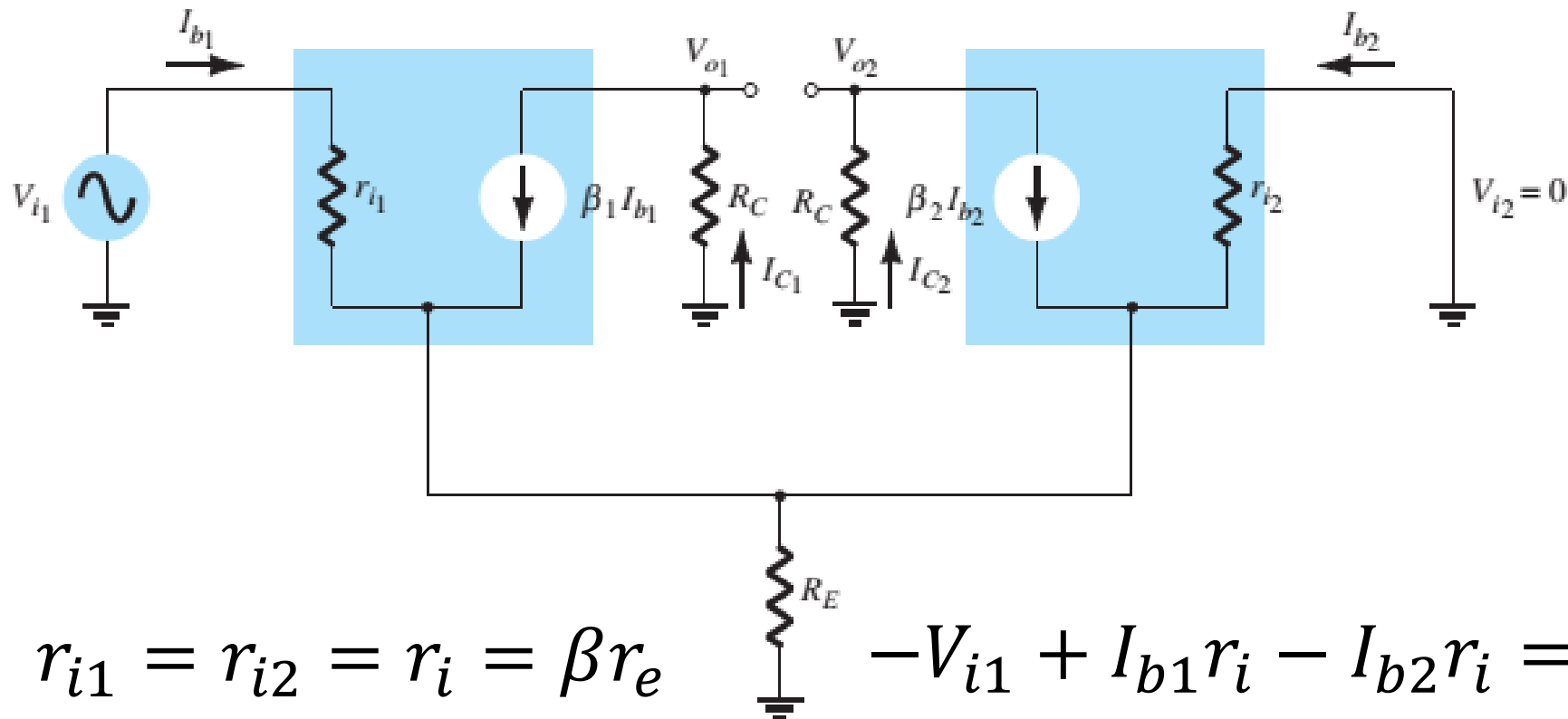


$$-V_{i1} + I_{b1}r_i - I_{b2}r_i = 0$$

$$I_{b1} = -I_{b2} = I_b$$

$$V_{i1} - I_b r_i - I_b r_i = 0$$



AC Operation of Diff-Amp

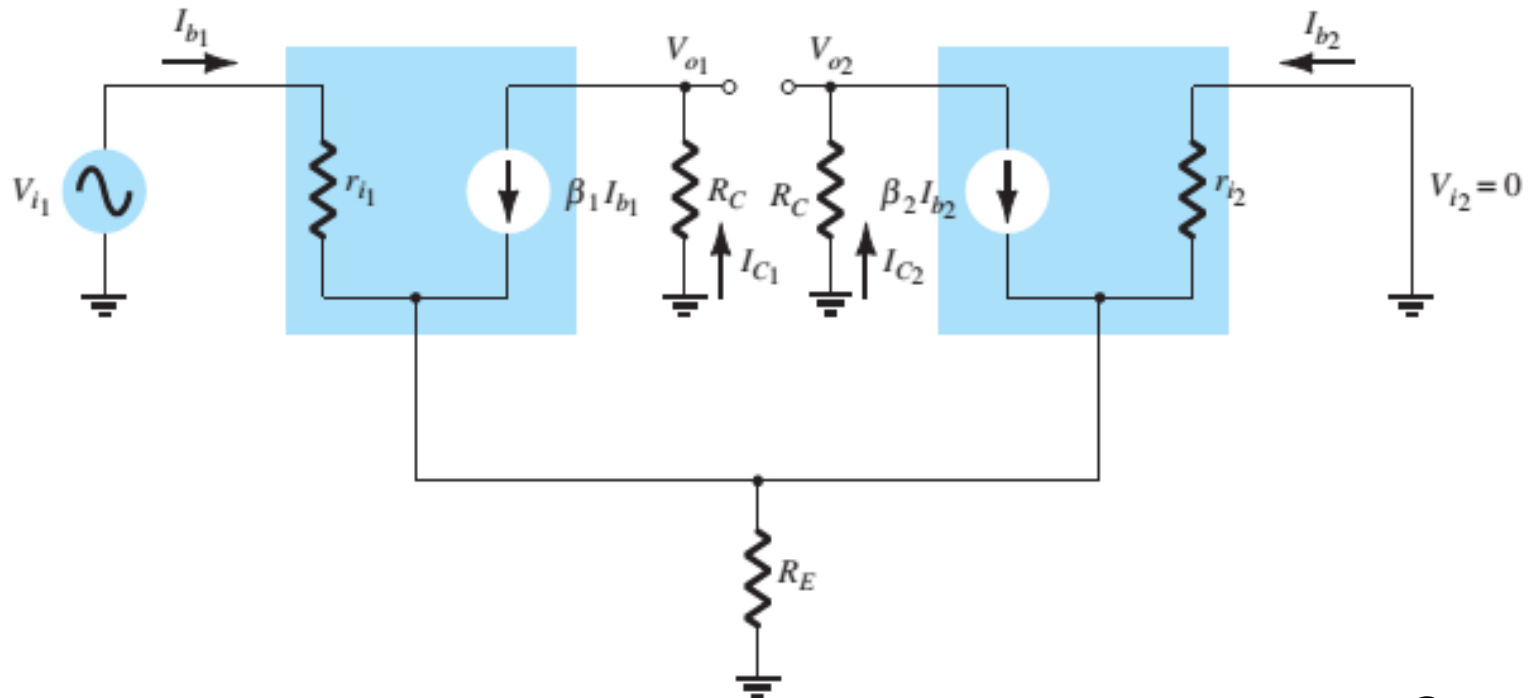

$$V_i = 2I_b r_i = 2\beta I_b r_e$$


$$V_{o1} = -I_{c1} R_C = -\beta I_b R_C$$

$$A_v = \frac{V_{o1}}{V_{i1}} = \frac{-\beta I_b R_C}{2\beta I_b r_e} = -\frac{R_C}{2r_e}$$



AC Operation of Diff-Amp


Example 10.2:

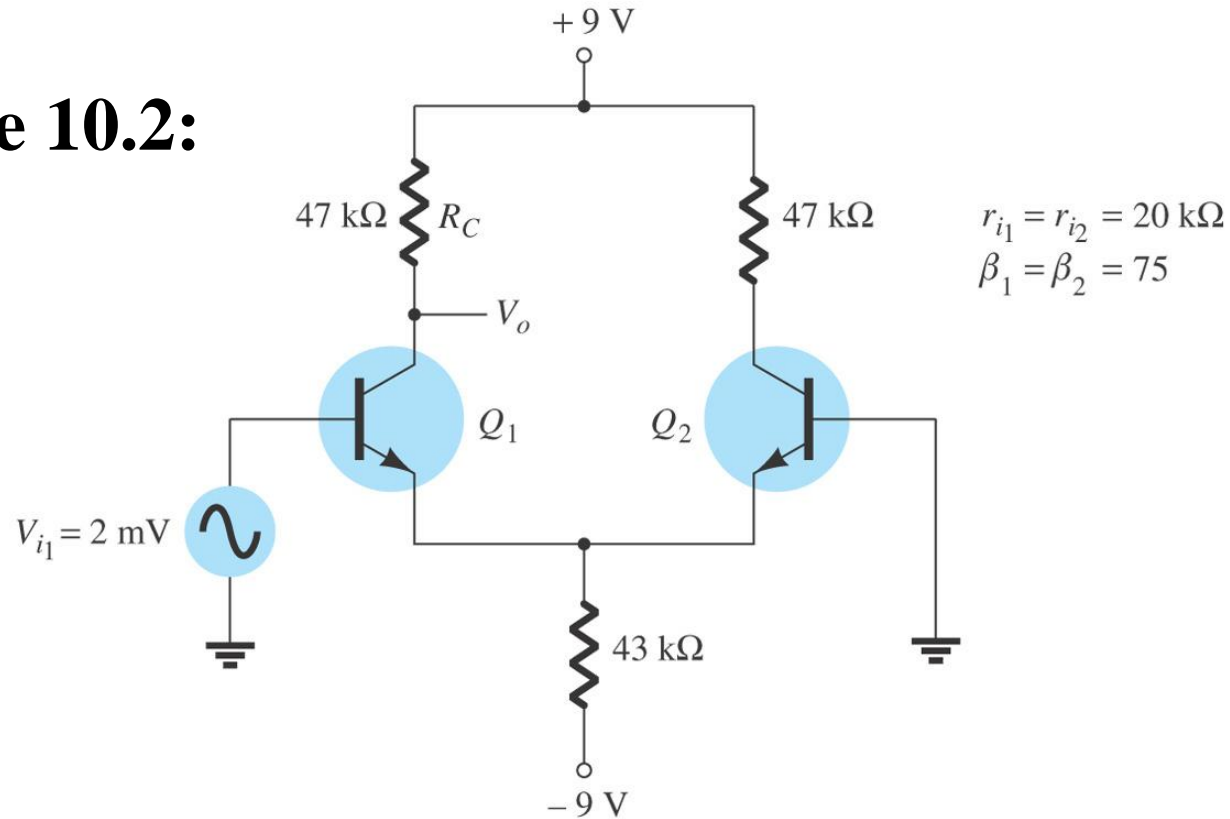

Circuit for Examples 10.2 and 10.3




Common-Mode Operation of Diff-Amp

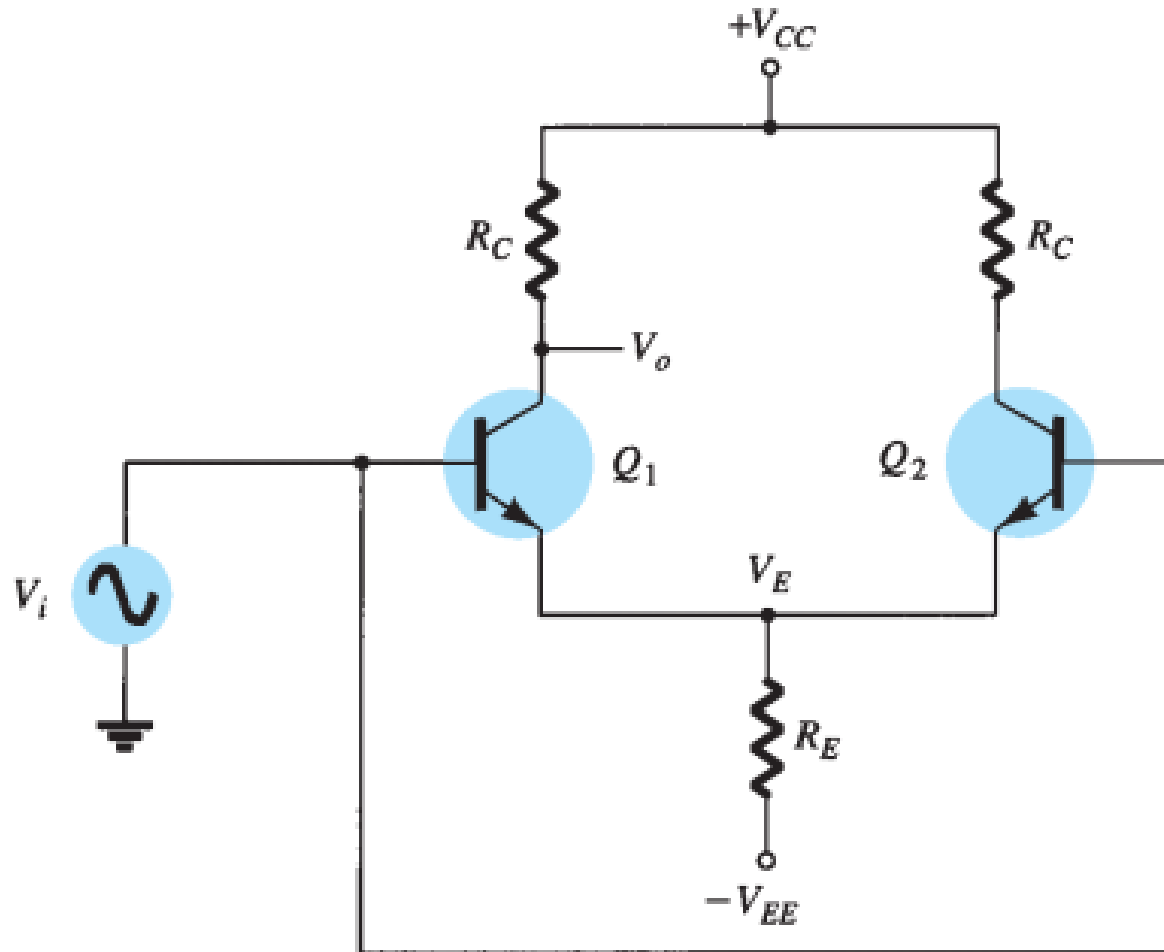



Common-Mode Operation of Diff-Amp

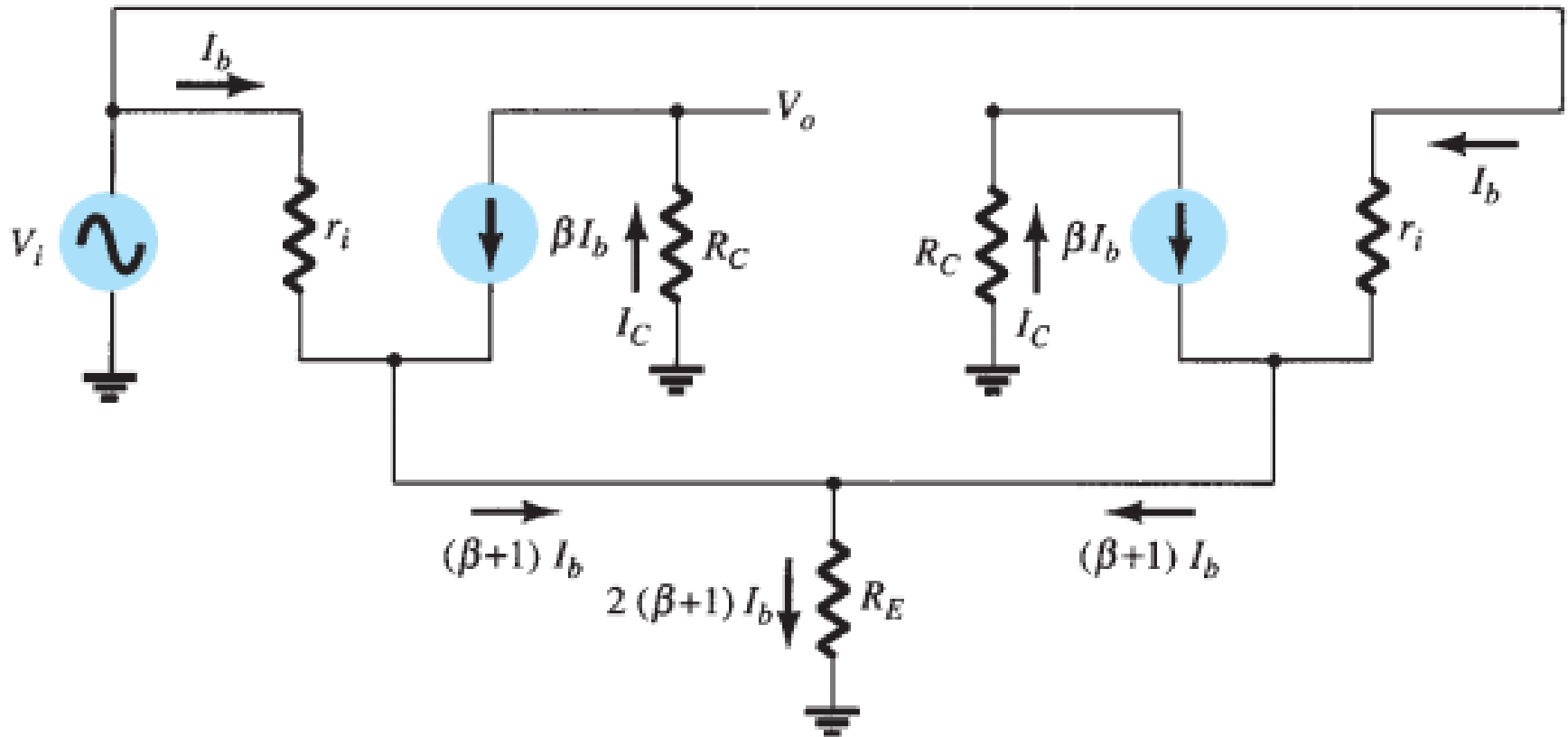


$$A_v = \frac{V_o}{V_i} = \frac{-\beta R_C}{\beta r_e + 2(1 + \beta)R_E}$$



Common-Mode Operation of Diff-Amp

Example 10.3

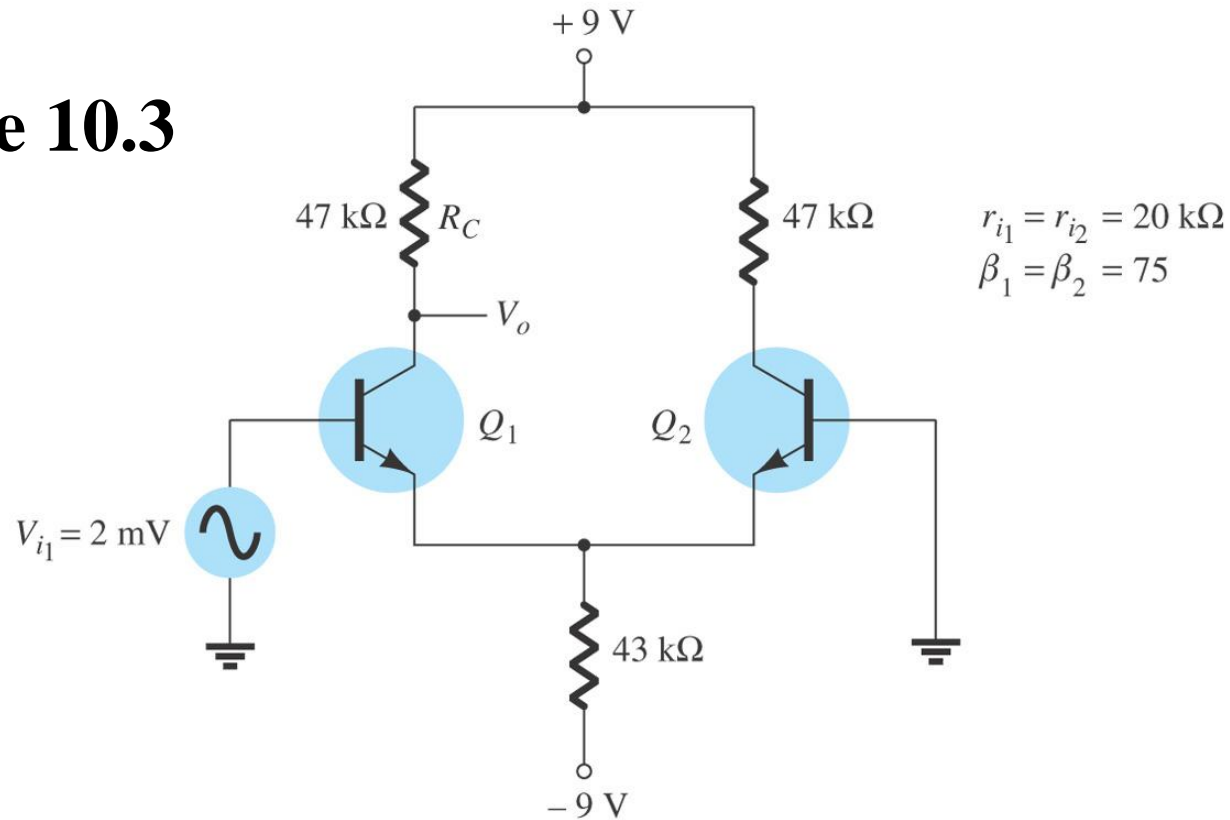

Circuit for Examples 10.2 and 10.3



AC Operation of Diff-Amp

Differential-mode input voltage:

$$V_d = V_{i1} - V_{i2}$$

Common-mode input voltage:

$$V_c = \frac{1}{2} (V_{i1} + V_{i2})$$


Output Voltage:

$$V_o = A_d V_d + A_c V_c$$

Common-mode Rejection Ratio (CMRR):

$$CMRR = \left| \frac{A_d}{A_c} \right|$$

$$CMRR(log) = 20 \log_{10} \left| \frac{A_d}{A_c} \right|$$

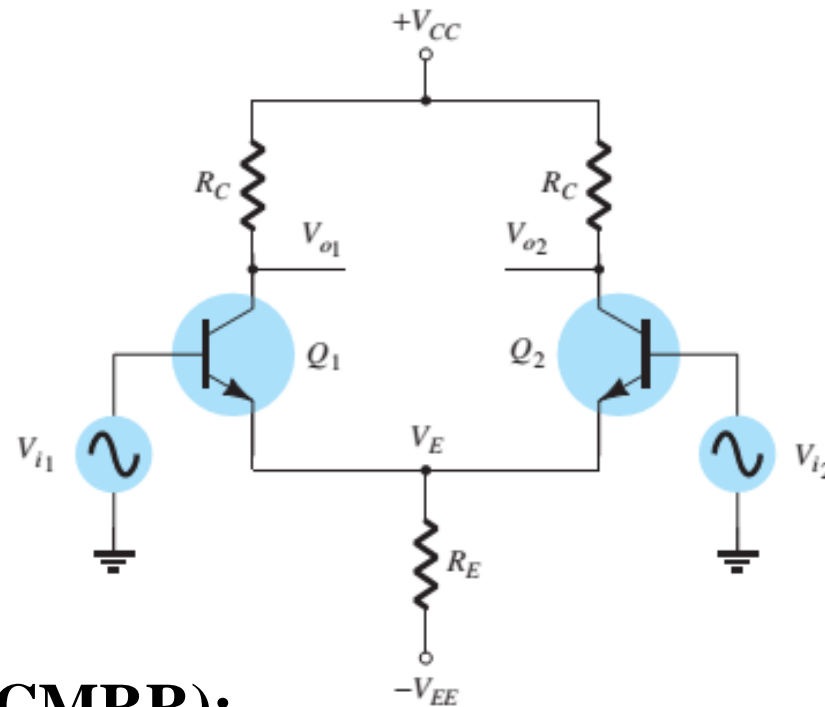



AC Operation of Diff-Amp

Example

1. Find the differential and common-mode components of the input signal applied to a diff-amp for input voltages of

(a) $v_{i1} = 2.1V$, $v_{i2} = 2.12V$; (b) $v_{i1} = 0.25 - 0.002\sin\omega t V$, $v_{i2} = 0.5 + 0.002\sin\omega t V$.

2. Assume the differential-mode gain of a diff-amp is $A_d = 80$, and the common-mode gain is $A_{cm} = -0.2$.


Determine the output voltage for input signals of:

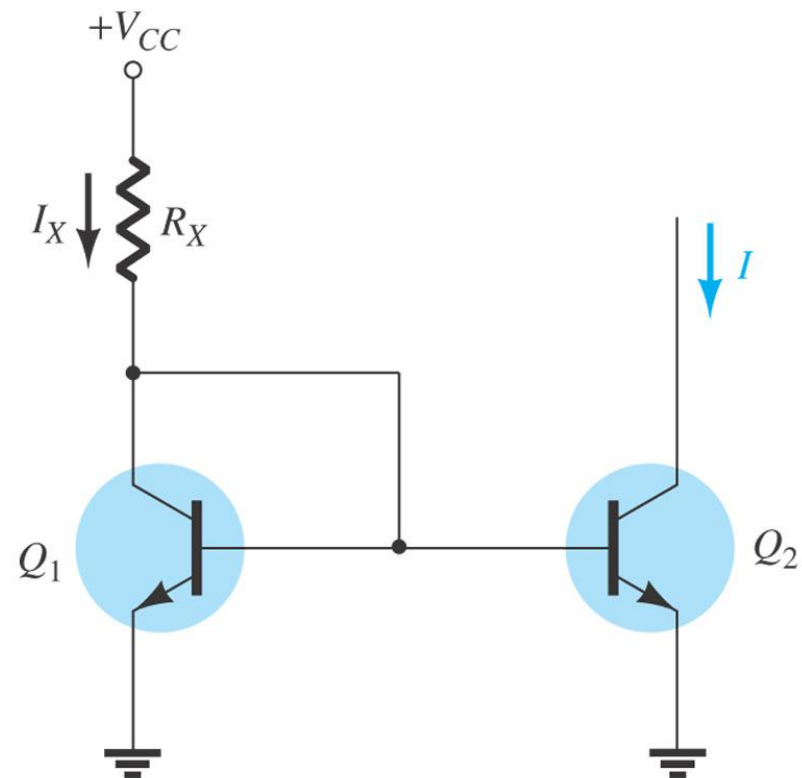(a) $v_1 = 0.995 \sin \omega t V$ and $v_2 = 1.005 \sin \omega t V$; and (b) $v_1 = 2 - 0.005 \sin \omega t V$ and $v_2 = 2 + 0.005 \sin \omega t V$.




Current Mirror Circuits

- A **current mirror circuit** provides a constant current and is used primarily in integrated circuits.
- The **constant current** is obtained from an output current, which is the reflection or mirror of a constant current developed on one side of the circuit.
- The current I_X set by transistor Q_1 and resistor R_X **is mirrored** in the current I through transistor Q_2 .





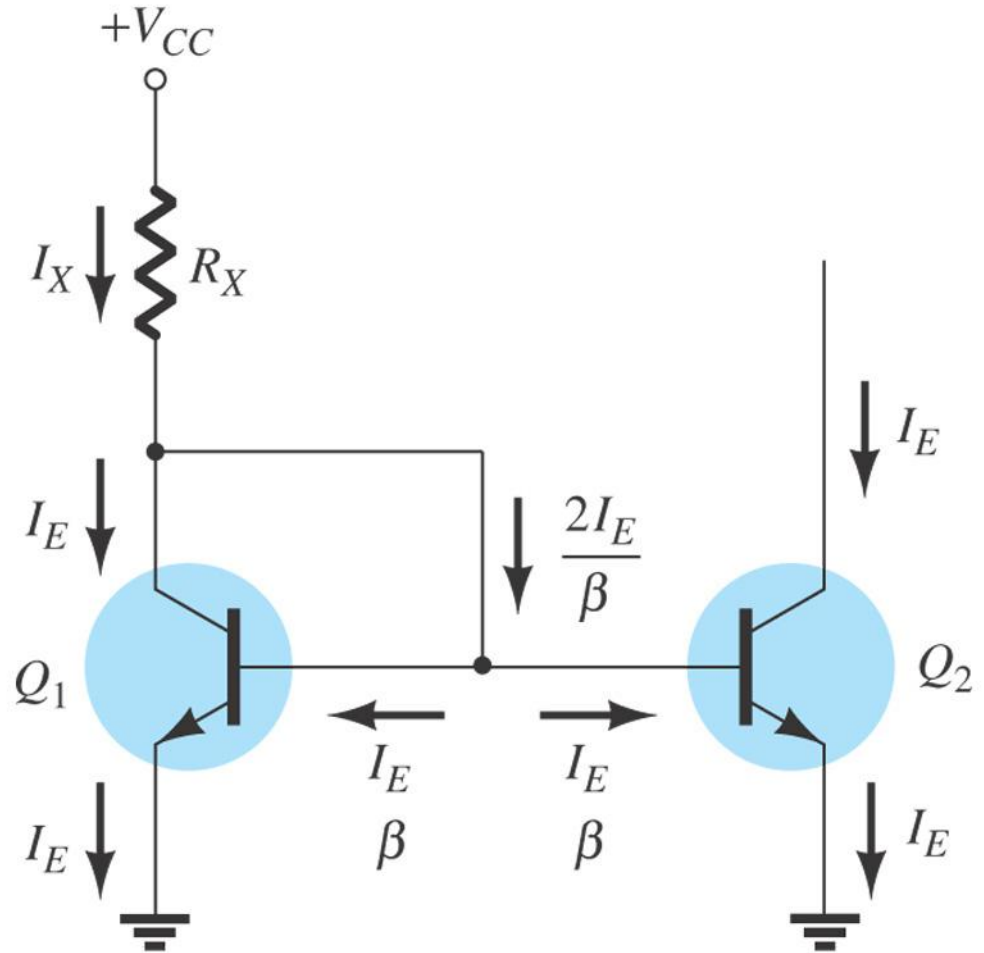
$$\begin{aligned} I_C &\cong I_E \\ I_X &= I_E + \frac{2I_E}{\beta} \\ &= \frac{\beta I_E}{\beta} + \frac{2I_E}{\beta} \\ &= \frac{\beta + 2}{\beta} I_E \approx I_E \\ I_X &= \frac{V_{CC} - V_{BE}}{R_X} \end{aligned}$$






Current Mirror Circuits

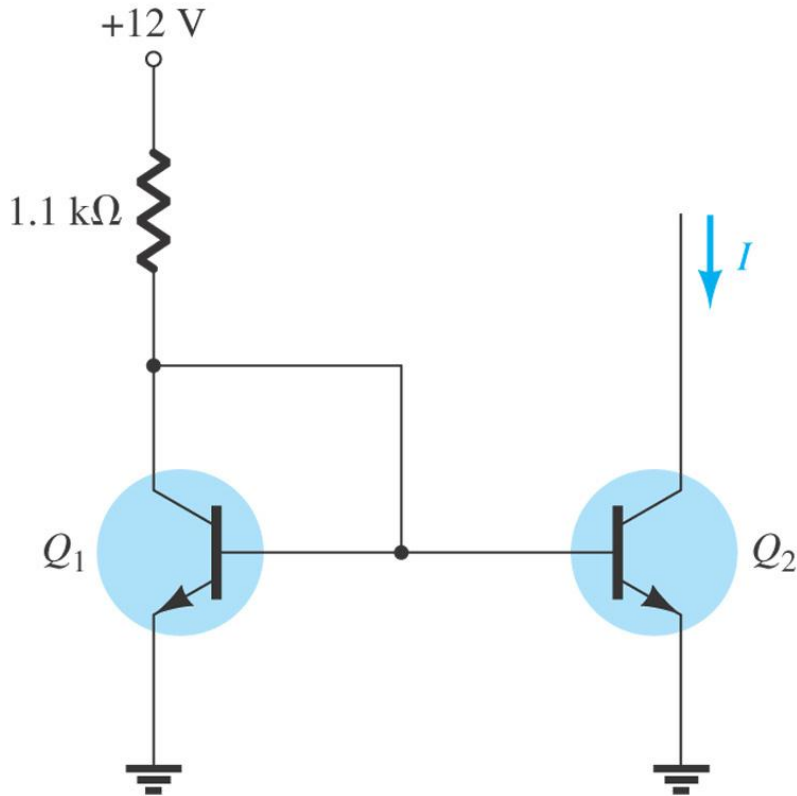


Current mirror circuit for Example 5.27

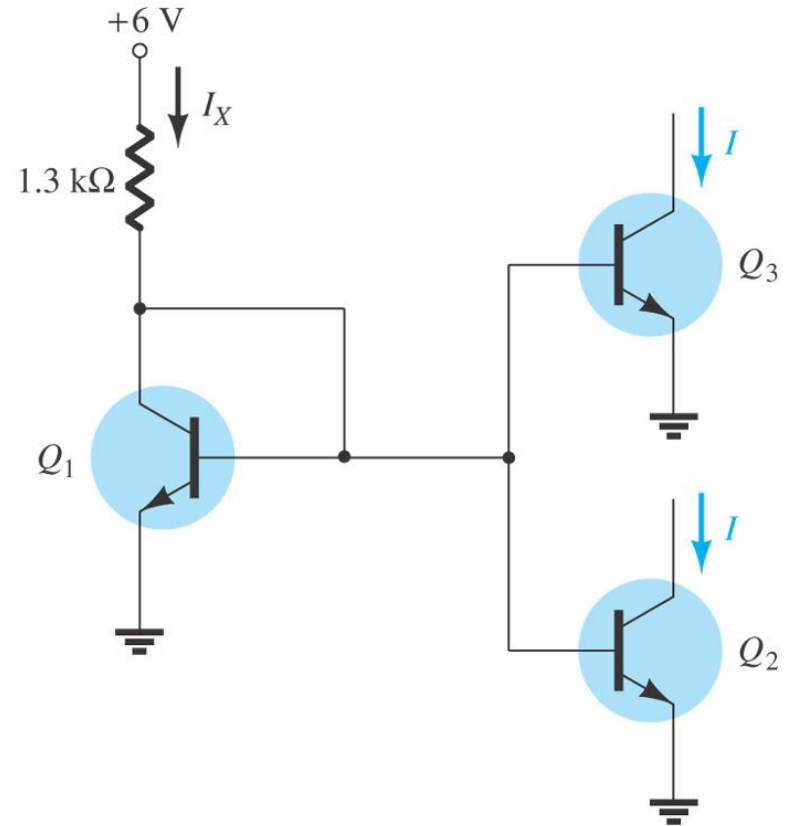


Current mirror circuit for Example 5.28



Circuit Source Circuits

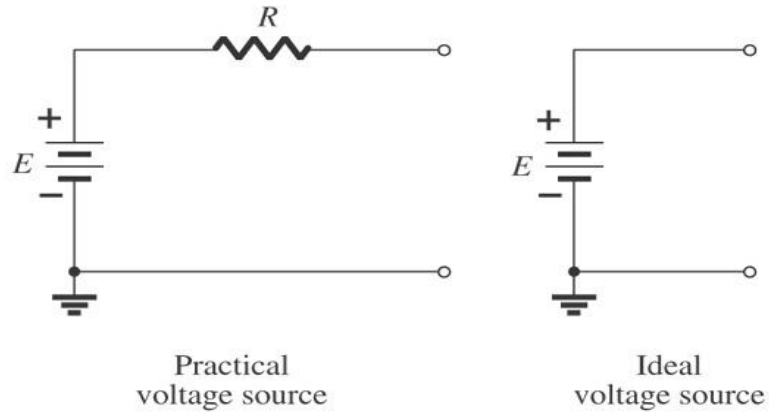

(a)

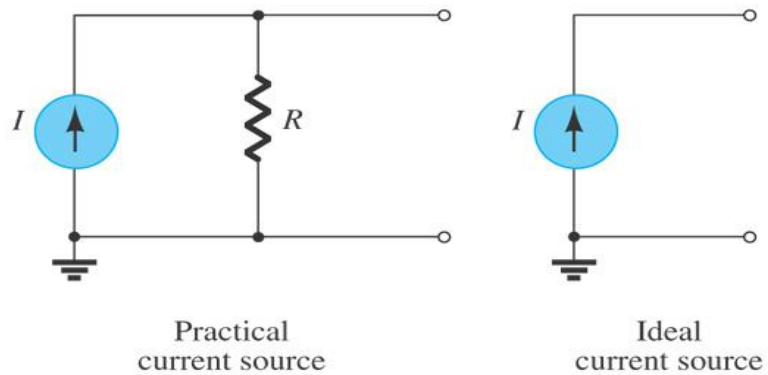

(b)




Circuit Source Circuits

$$V_B = \frac{R_1}{R_1 + R_2} (-V_{EE})$$

$$V_E = V_B - 0.7V$$

$$I_E = \frac{V_E - (-V_{EE})}{R_E} \approx I_C$$

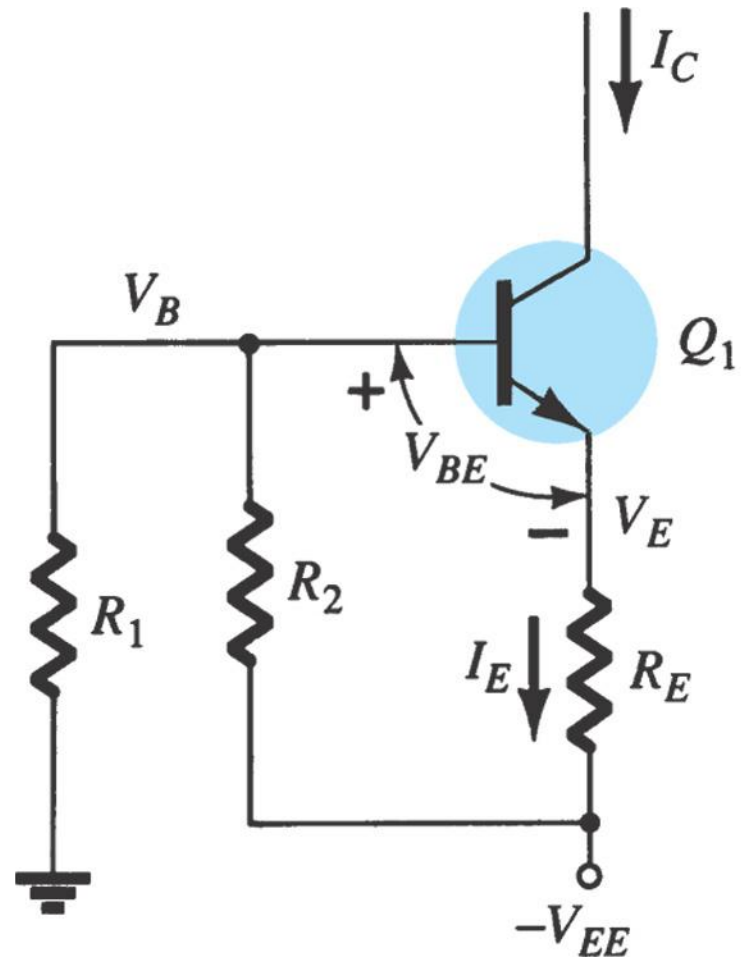I_C Is the constant current provided by the circuit




Discrete constant-current source



Circuit Source Circuits

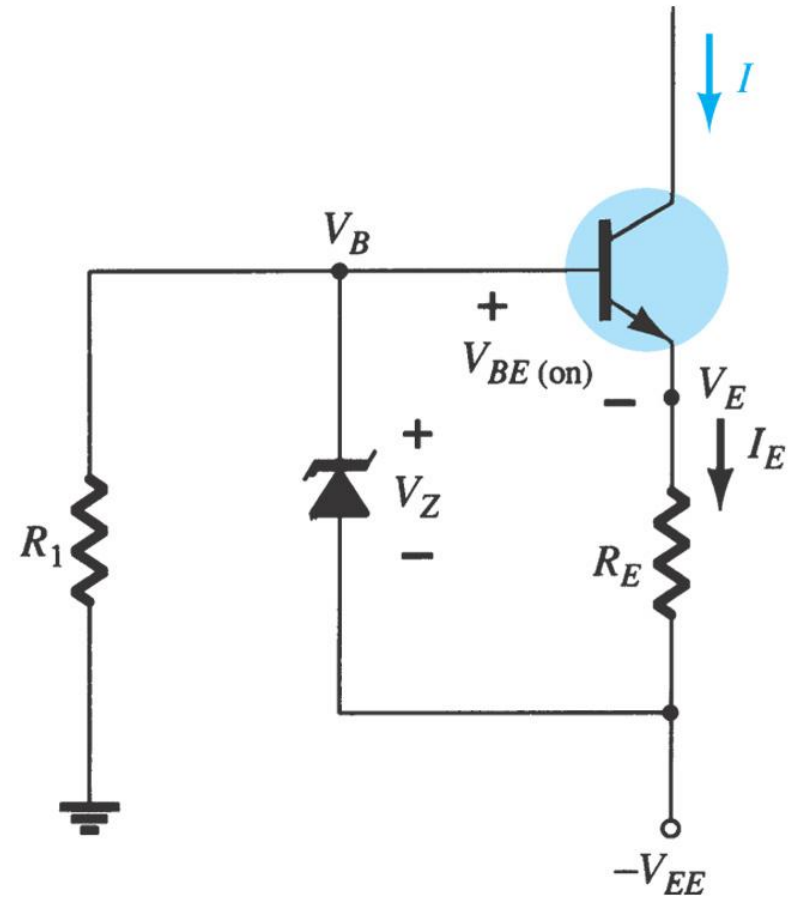
$$I \approx I_E = \frac{V_Z - V_{BE}}{R_E}$$



Constant-current circuit using Zener diode




Use of Constant-Current Source

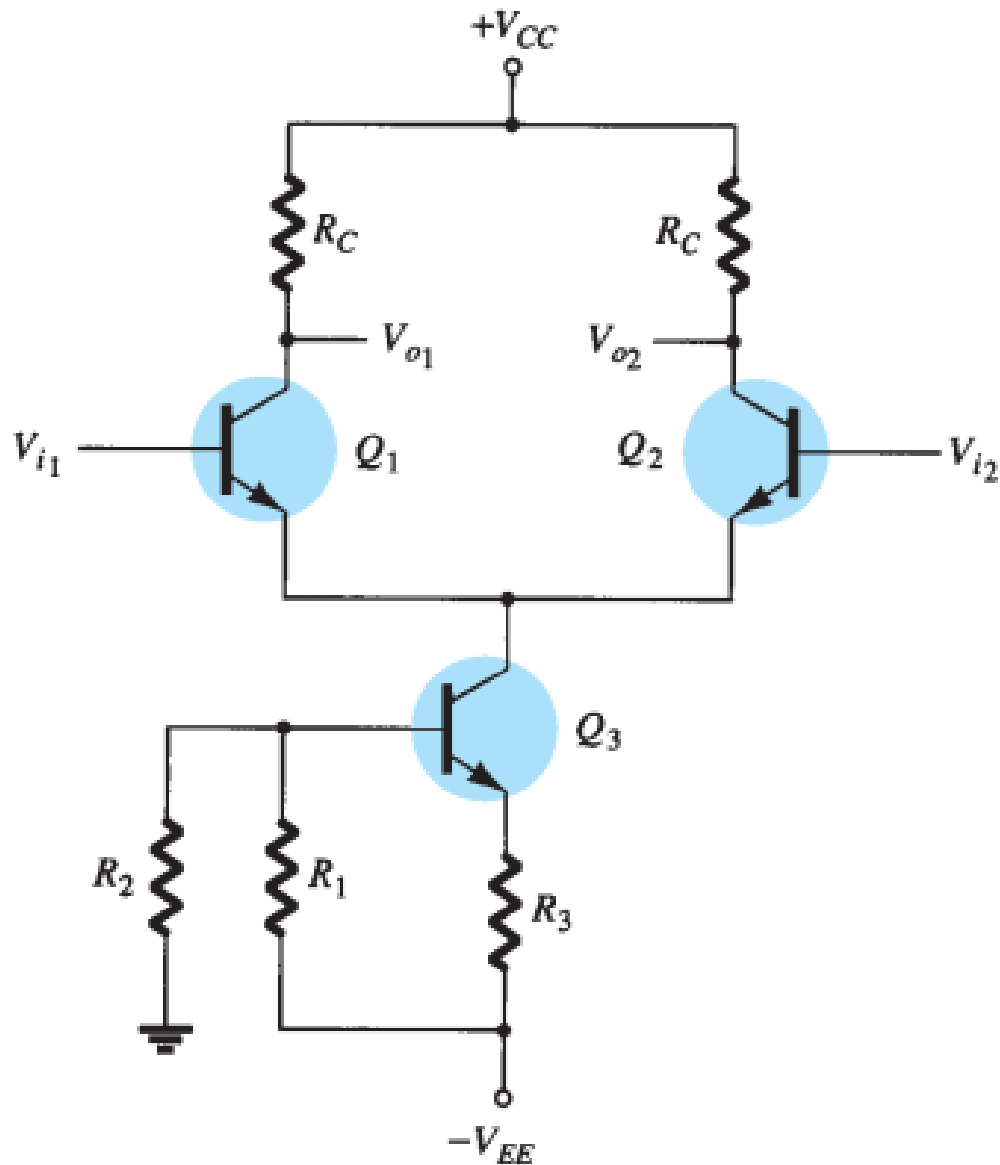



Op-Amp Basics

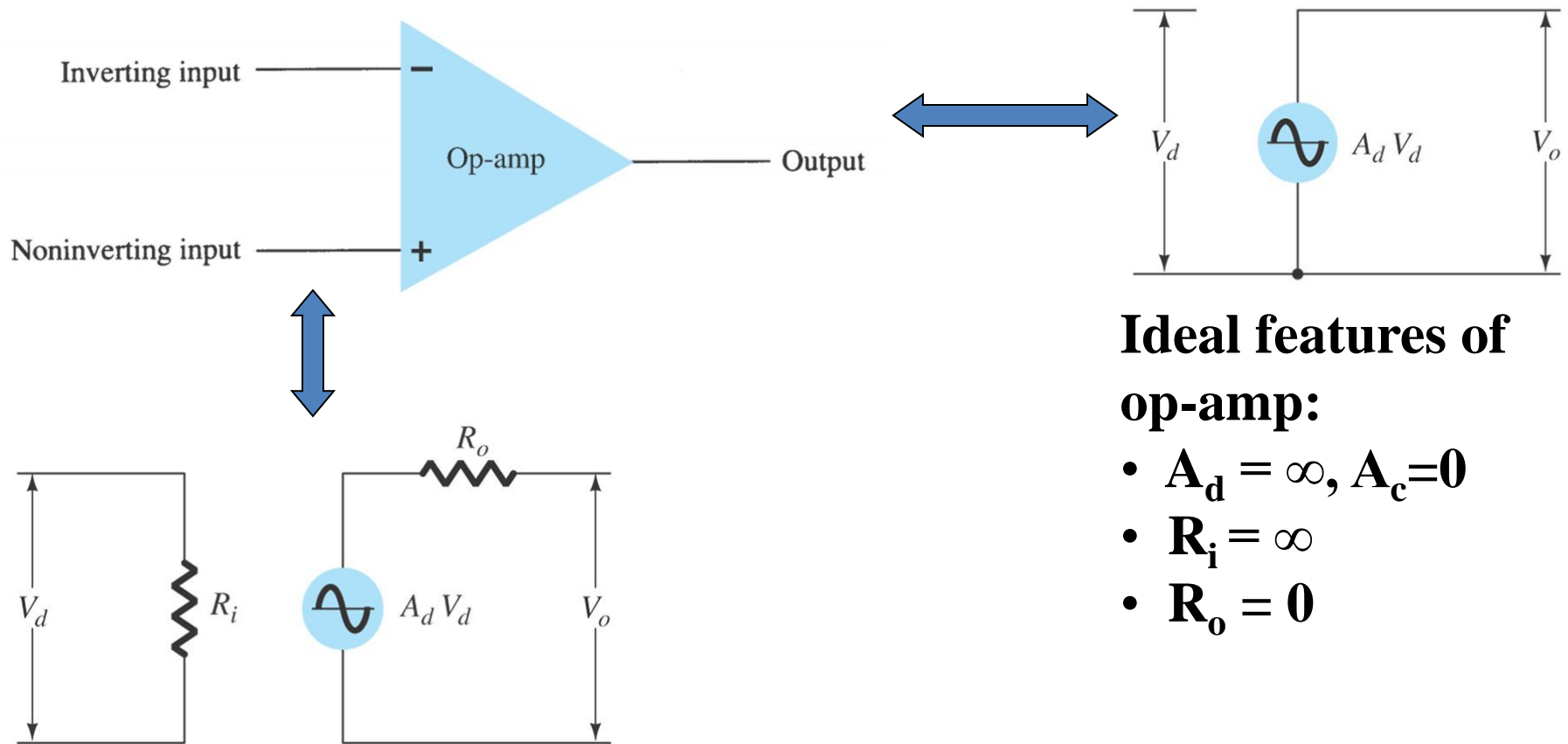

Ideal features of op-amp:



- $A_d = \infty$, $A_c = 0$
- $R_i = \infty$
- $R_o = 0$

Practical features of op-amp:

- very high gain A_d for differential input V_d (Open-Loop differential Gain)
- high input impedance R_i (typically a few meg-Ohms)
- low output impedance R_o (less than 100 Ω).



Op-Amp Basics

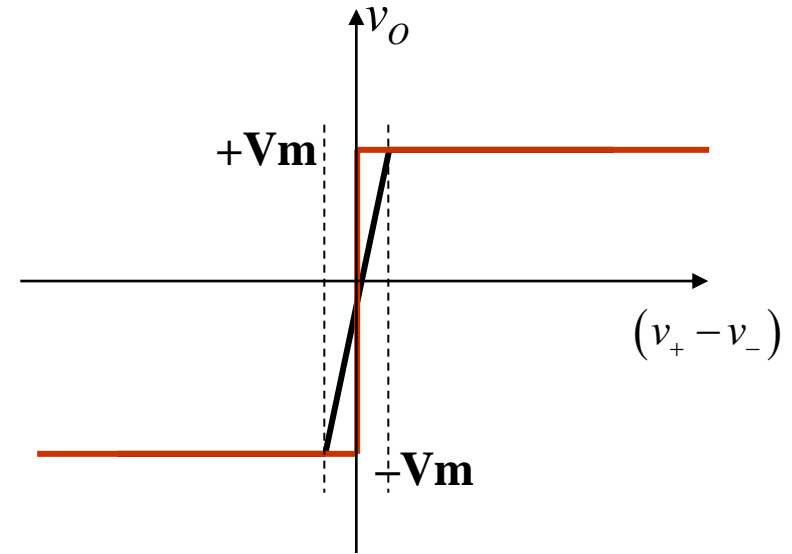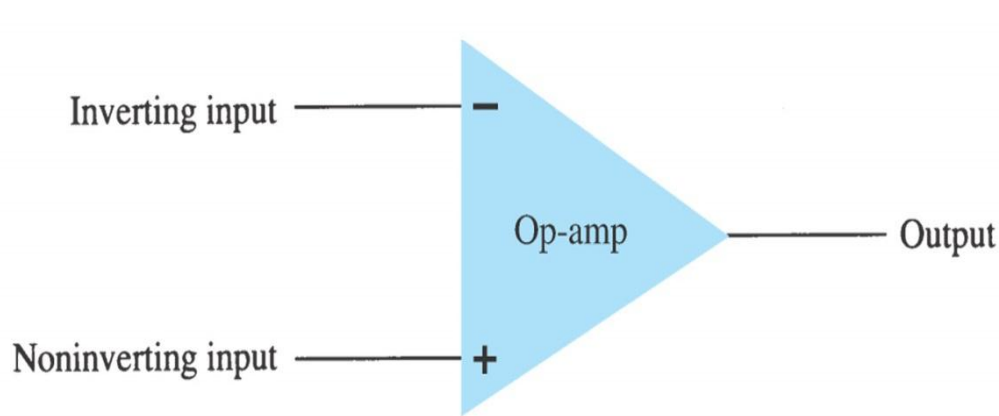

Ideal features of op-amp:

➤ $A_d = \infty, A_c = 0$

➤ $R_i = \infty$

➤ $R_o = 0$

Virtual Short: $V^+ = V^-$


Virtual Open: $I^+ = I^- = 0$

Working at linear region →

circuit with negative feedback



Inverting Amplifier

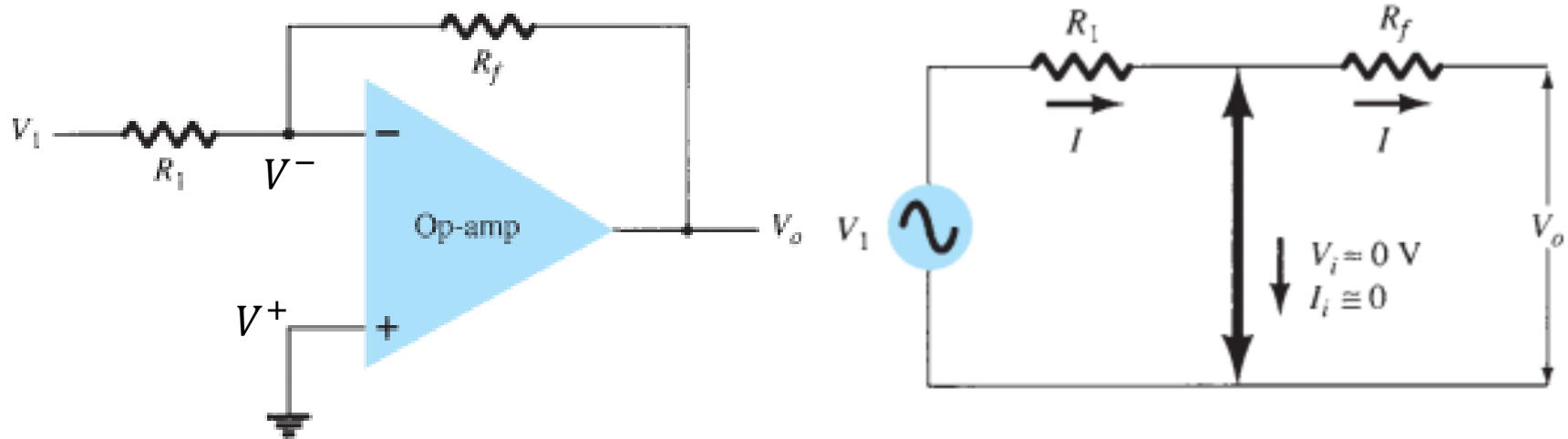

Virtual Open $I^+ = I^- = 0$

Virtual Short $V^+ = V^-$

$V^+ = 0 \quad \Rightarrow \quad V^+ = V^- = 0$ **Virtual Ground**



Inverting Amplifier

$$I = \frac{V_i}{R_1} = \frac{0 - V_o}{R_f} \quad A_v = \frac{V_o}{V_i} = -\frac{R_f}{R_1}$$


The ratio of the overall output to input voltage is dependent only on the values of resistors R_1 and R_f

$$R_i = ? \quad R_i = \frac{V_i}{I_i} = R_1$$

$$\text{If } R_1 = R_f \quad \longrightarrow \quad A_v = -1$$



Amplifier with a T-Network

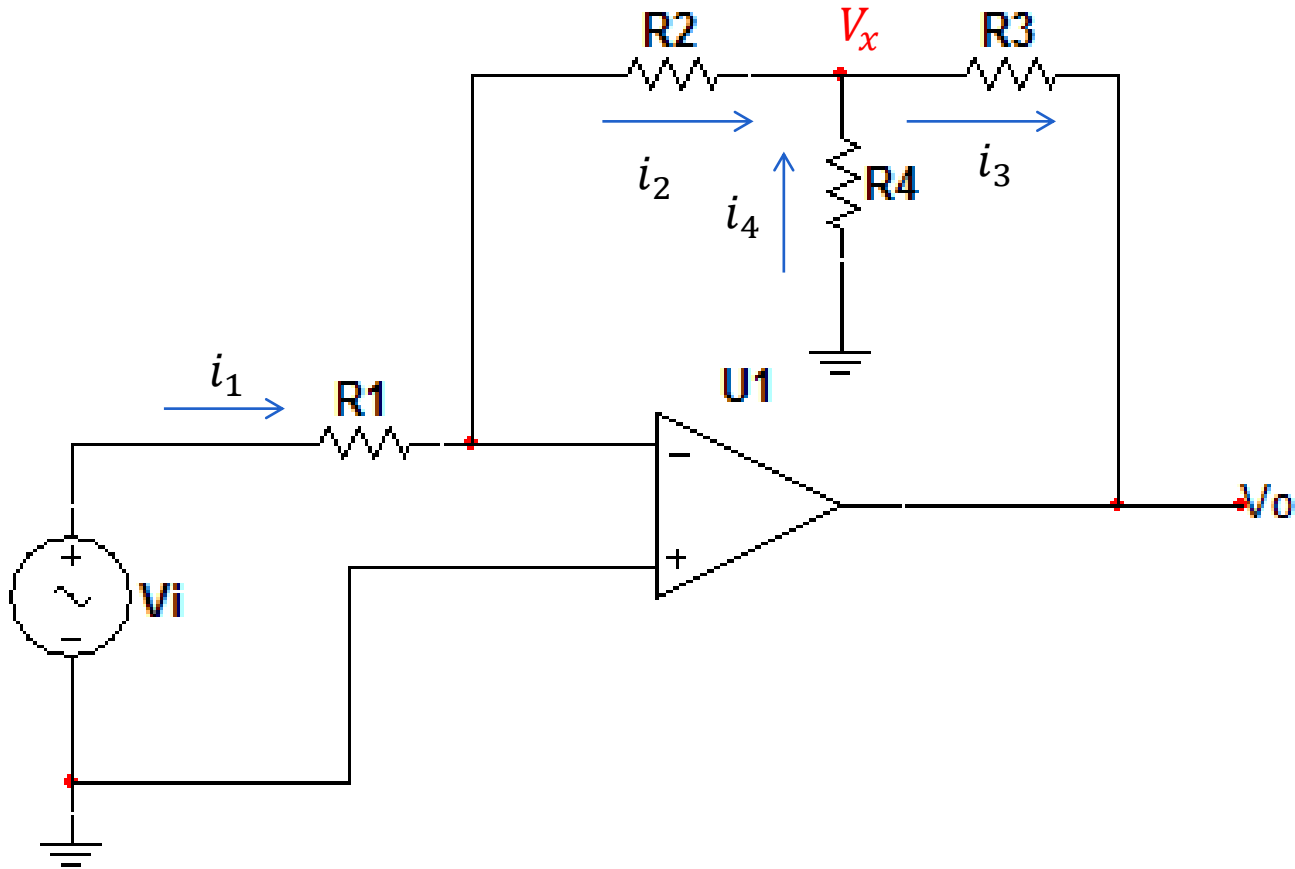



Exercise Problem



Design an ideal inverting op-amp with a T-network that has a closed-loop voltage gain of $A_v = -50$, and an input resistance of $10\text{k}\Omega$.

All resistors must be no larger than $50\text{k}\Omega$.

The amplifier with a T-network allows us to obtain a large gain using reasonably sized resistor.



Noninverting Amplifier

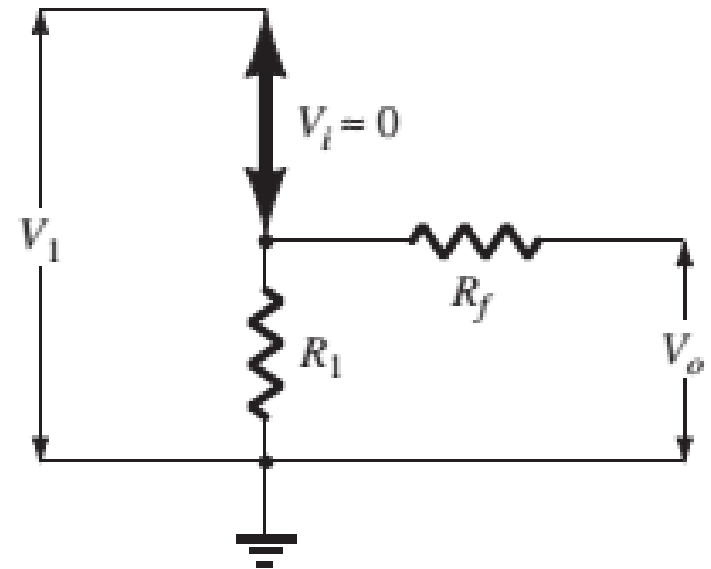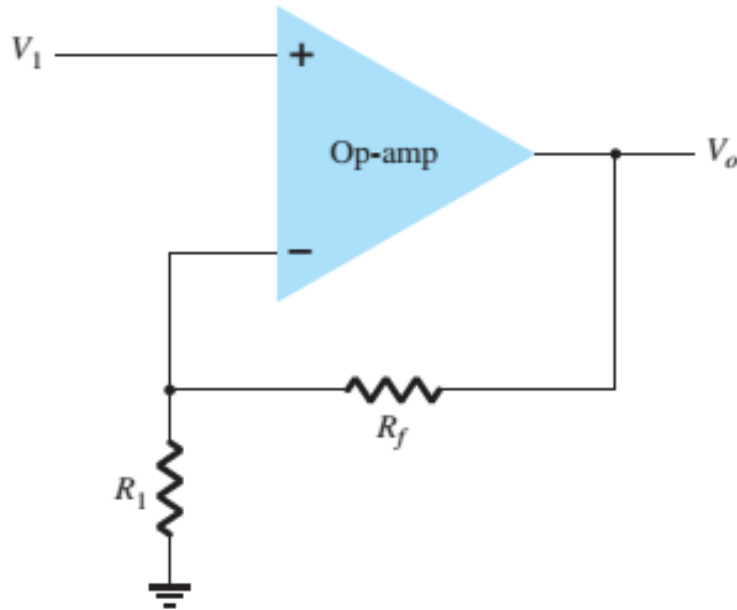

Virtual Open

$$I^+ = I^-$$

Virtual Short


$$V^+ = V^-$$



$$A_V = 1 + \frac{R_f}{R_1}$$



Unity Follower

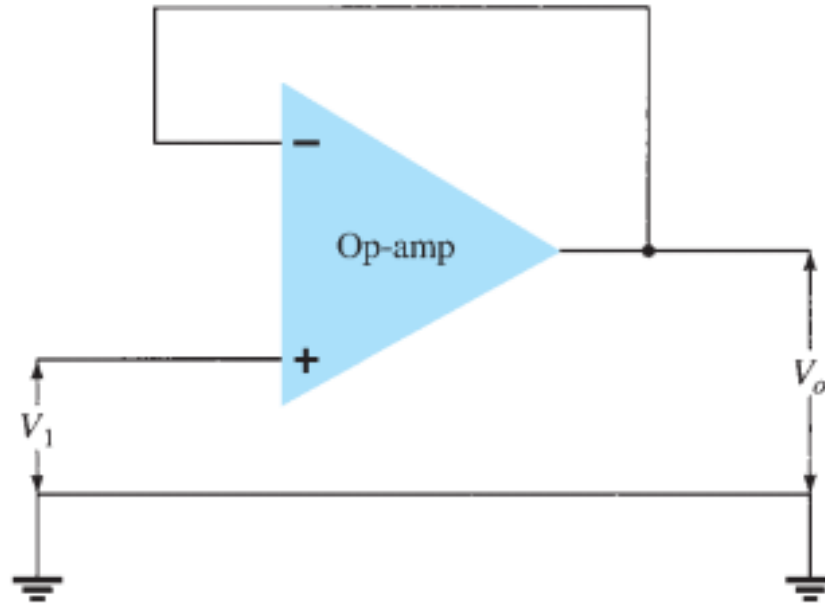

$$V_o = V_i$$




Problem-Solving Technique

1. If the noninverting terminal of the op-amp is at ground potential, the the inverting terminal is at virtual ground. Sum currents at this node, assuming zero current enters the op-amp itself.
2. If the noninverting terminal of the op-amp is not at ground potential, then the inverting terminal voltage is equal to that at the noninverting terminal. Sum currents at the inverting terminal node, assuming zero current enters the op-amp itself.
3. For the ideal op-amp circuit, the output voltage is determined from either step 1 or step 2 above and is independent of any load connected to the output terminal.




Voltage Summing

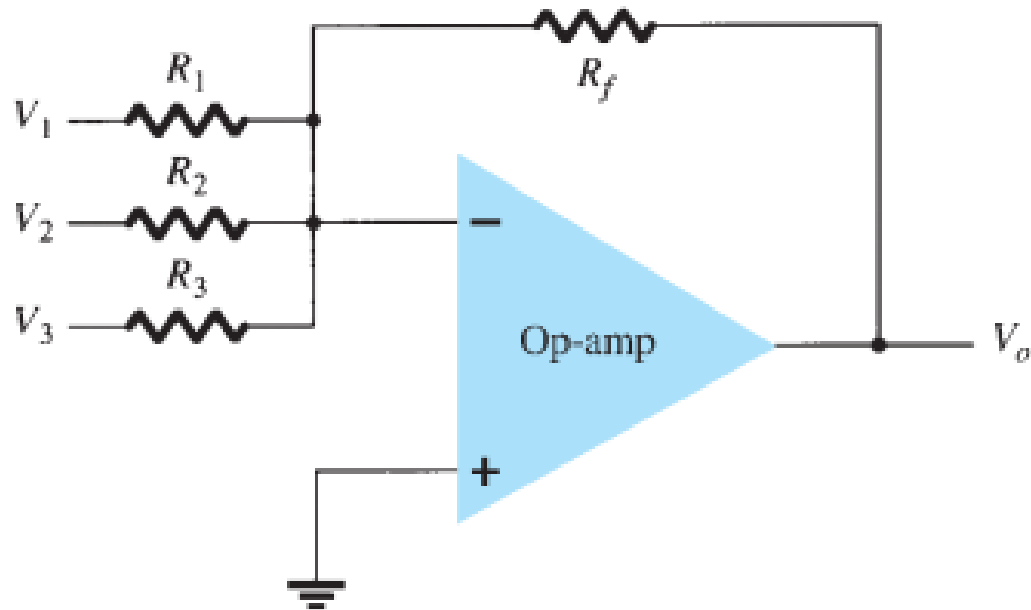

$$V_o = -\left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3\right)$$




Exercise Problem

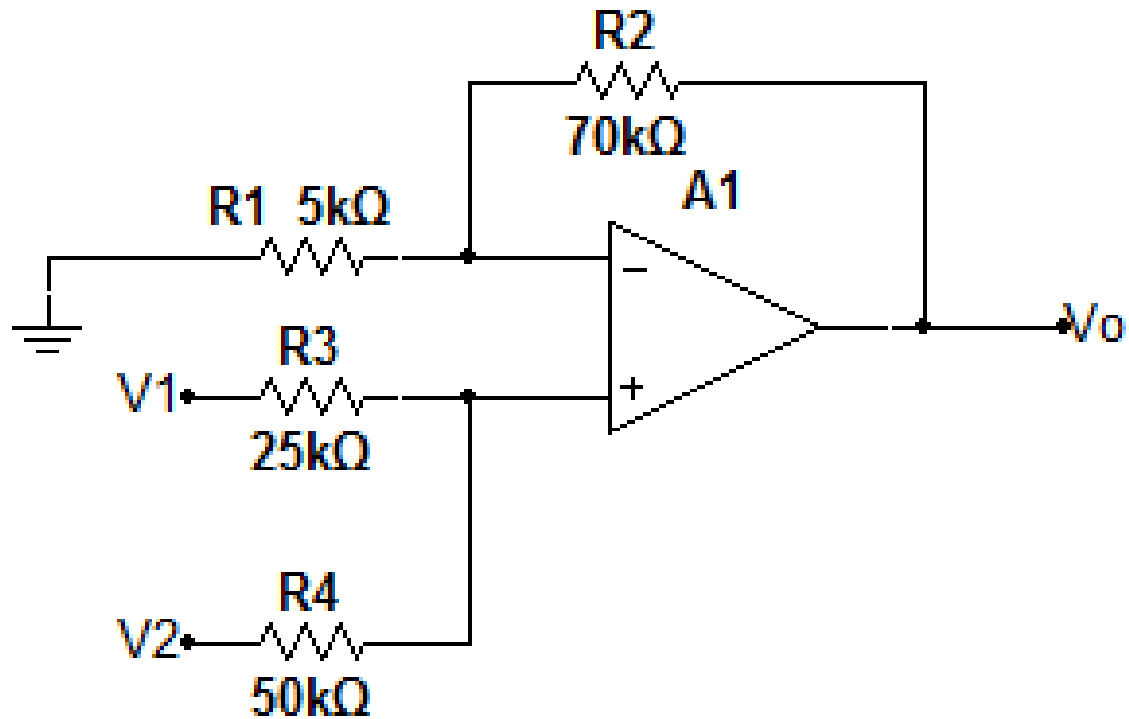




Voltage Subtraction

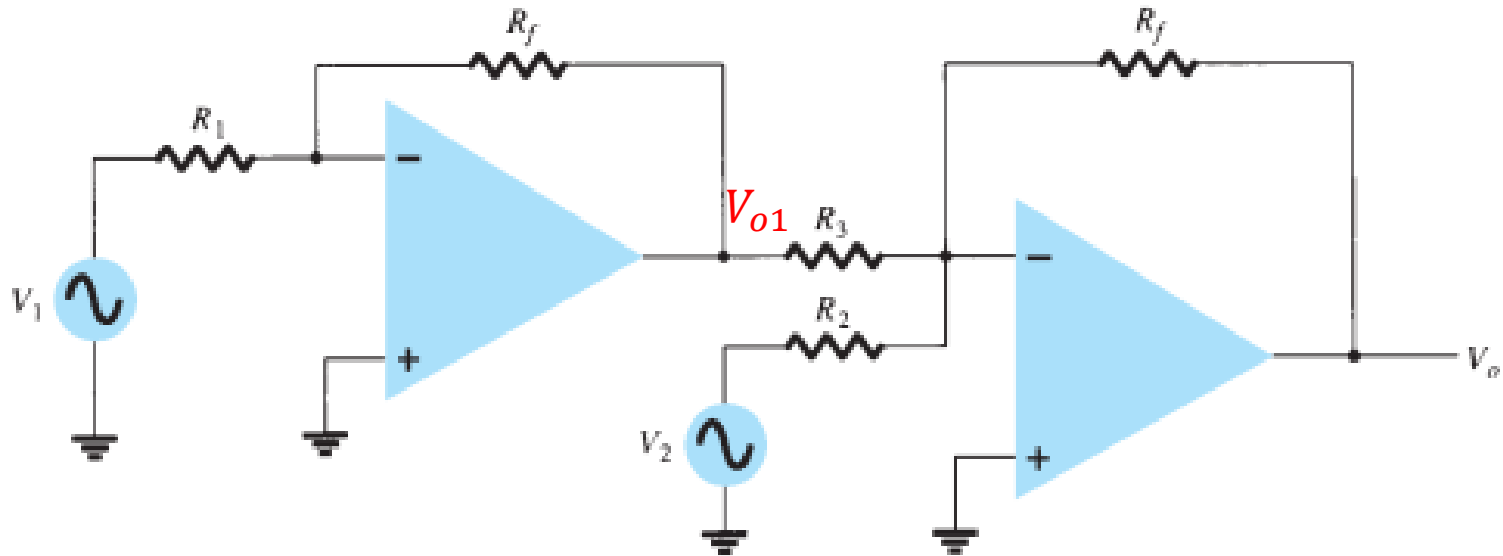

$$V_o = -\left(\frac{R_f}{R_2} V_2 - \frac{R_f}{R_3} \frac{R_f}{R_1} V_1\right)$$




Voltage Subtraction

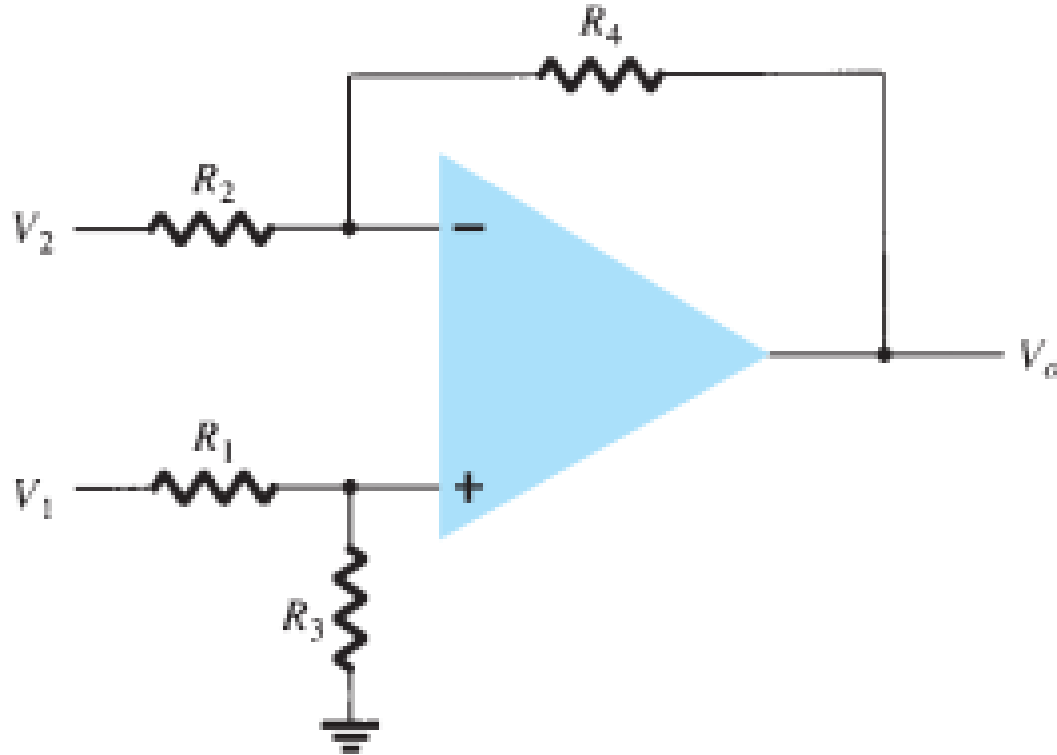

$$V_o = \frac{R_3}{R_1 + R_3} \frac{R_2 + R_4}{R_2} V_1 - \frac{R_4}{R_2} V_2$$




Example 11.3

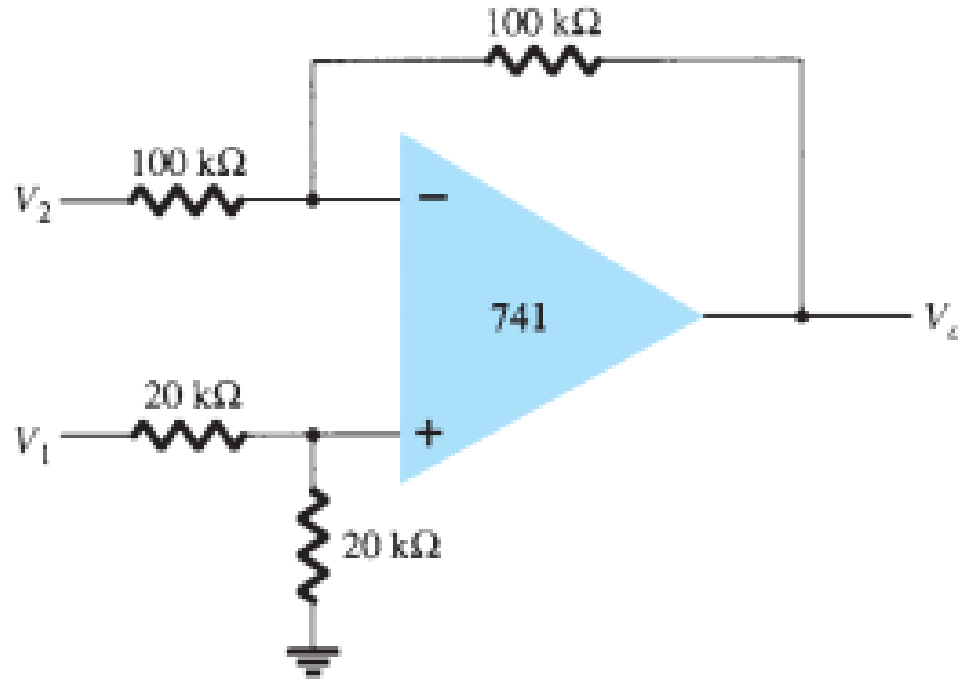

$$V_o = \left(\frac{20K\Omega}{20K\Omega + 20K\Omega} \right) \left(\frac{100K\Omega + 100K\Omega}{100K\Omega} \right) V_1 - \frac{100K\Omega}{100K\Omega} V_2 = V_1 - V_2$$




Integrator

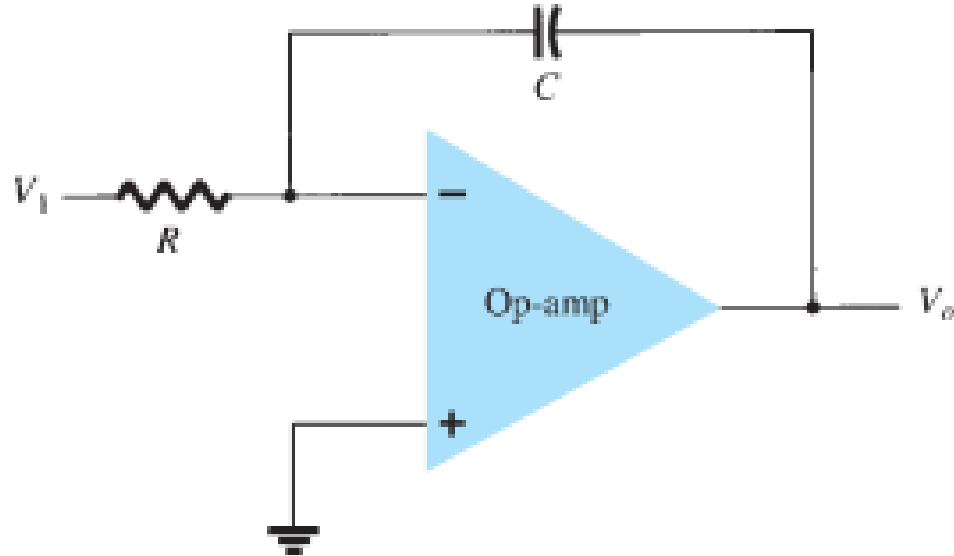

$$v_o(t) = -\frac{1}{RC} \int v_1(t) dt$$




Integrator

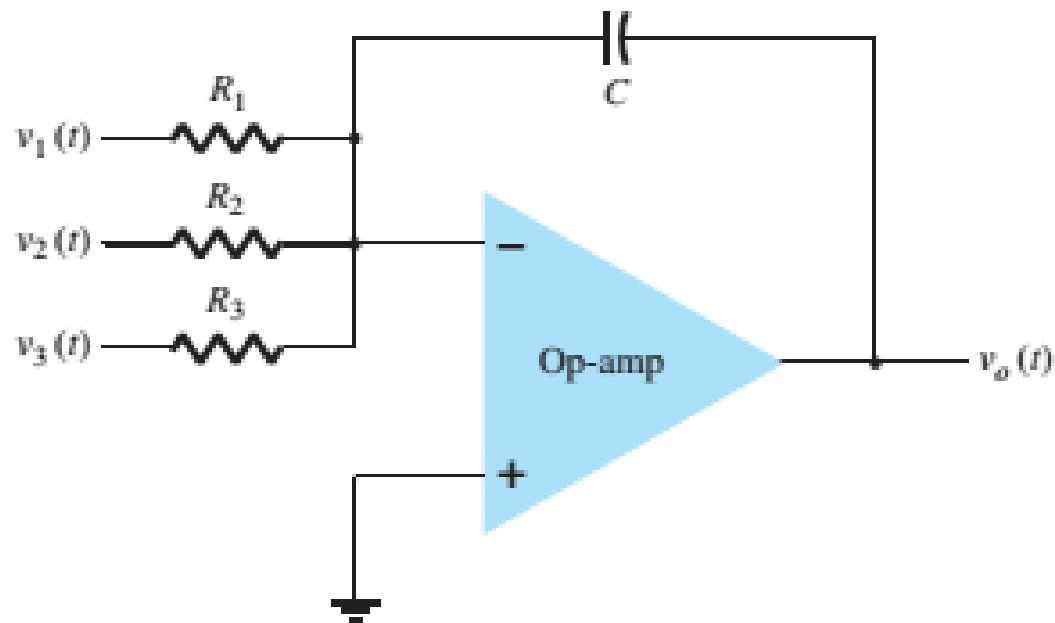


$$v_o(t) = -\left[\frac{1}{R_1 C} \int v_1(t) dt + \frac{1}{R_2 C} \int v_2(t) dt + \frac{1}{R_3 C} \int v_3(t) dt \right]$$




Exercise

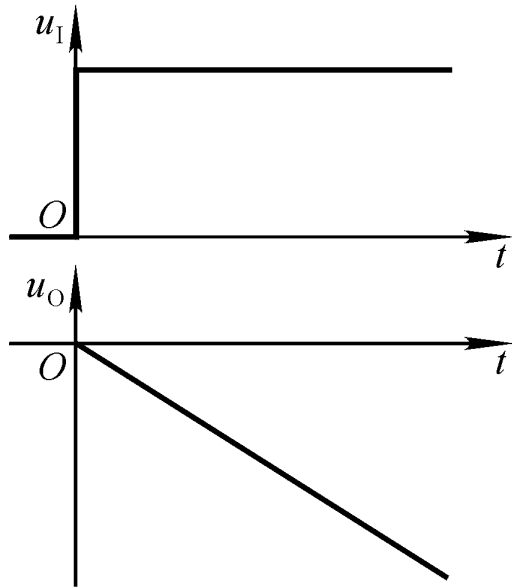

(a)

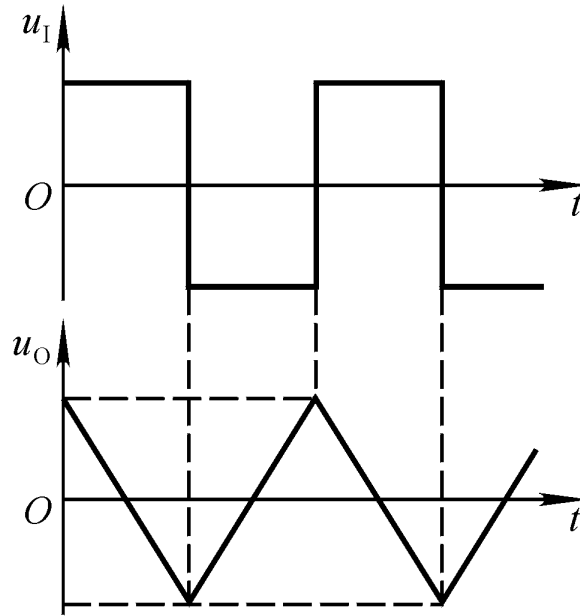


(b)

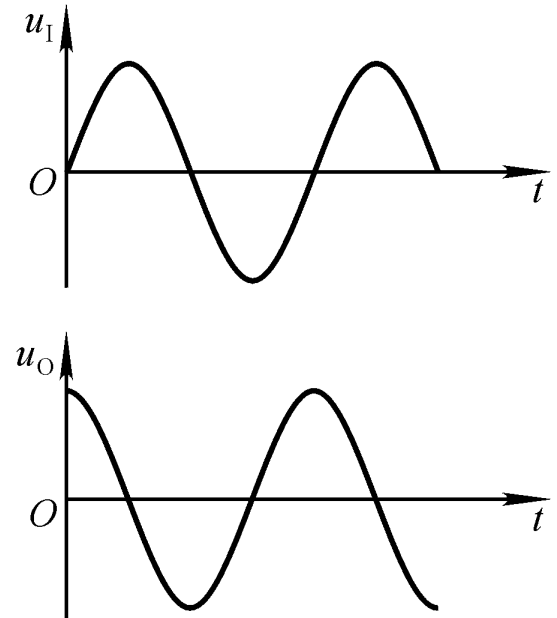

(c)



Differentiator


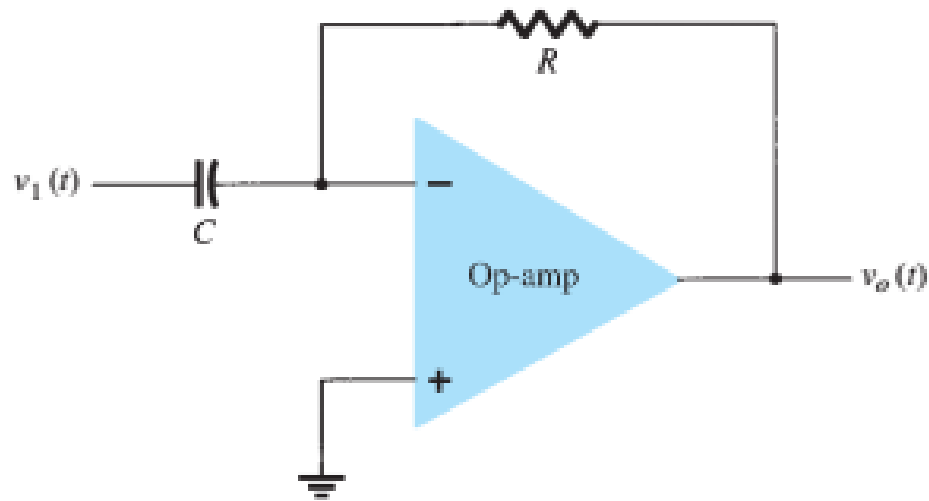


$$v_o(t) = -RC \frac{dv_1(t)}{dt}$$



Active Filter

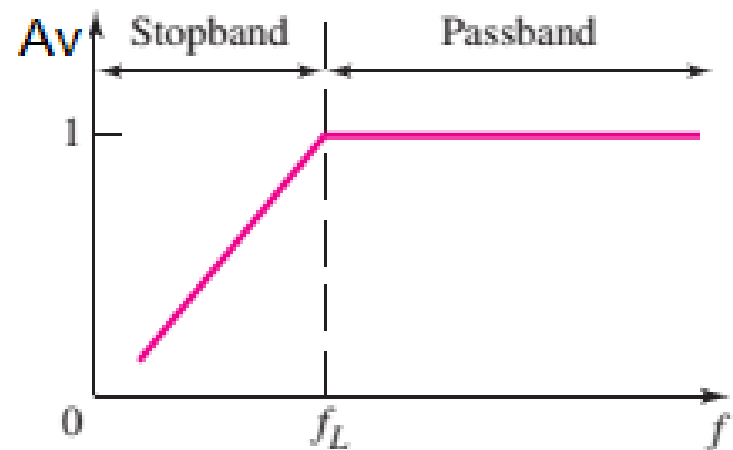
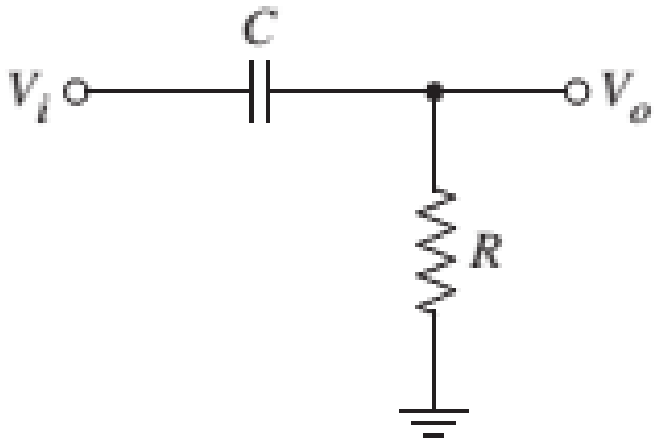
- The word *filter* refers to the process of removing undesired portions of the frequency spectrum.





Active Filter

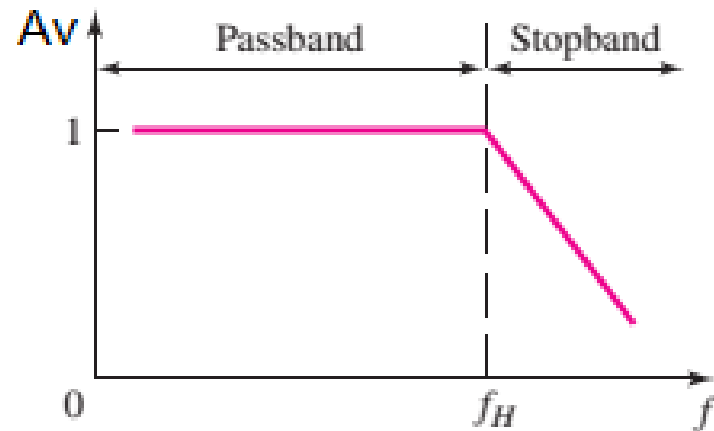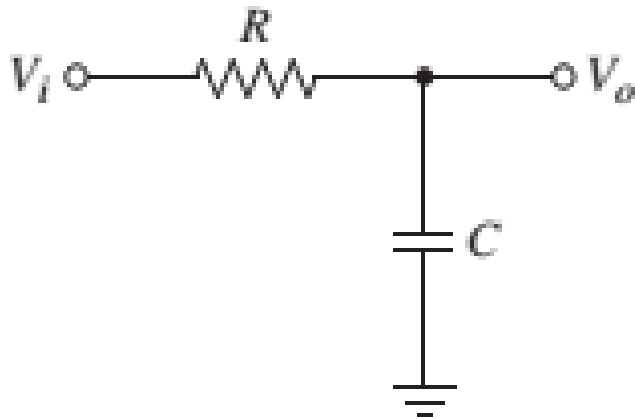- The word *filter* refers to the process of removing undesired portions of the frequency spectrum.
- The word *active* implies the use of one or more active devices, usually an operational amplifier, in the filter circuit.






Active Filter

Two advantages of active filters over passive filters are:

- The maximum gain or the maximum value of the transfer function may be greater than unity.
- The loading effect is minimal, which means that the output response of the filter is essentially independent of the load driven by the filter.




Active Filter

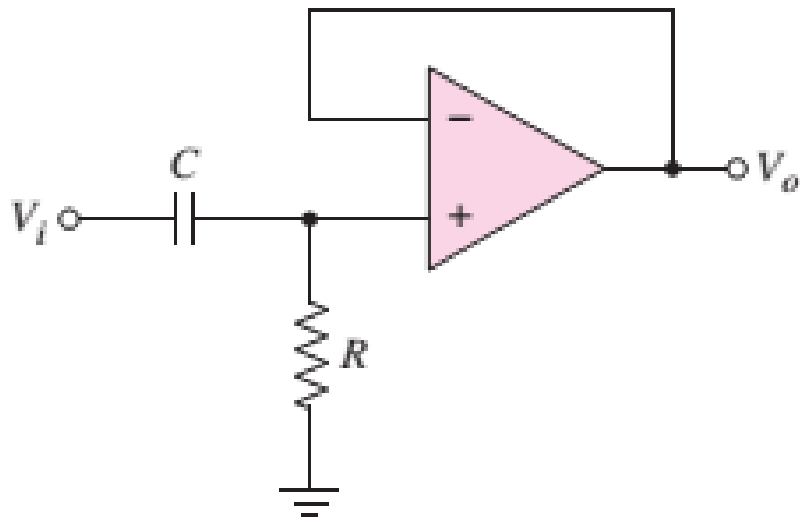

(a)

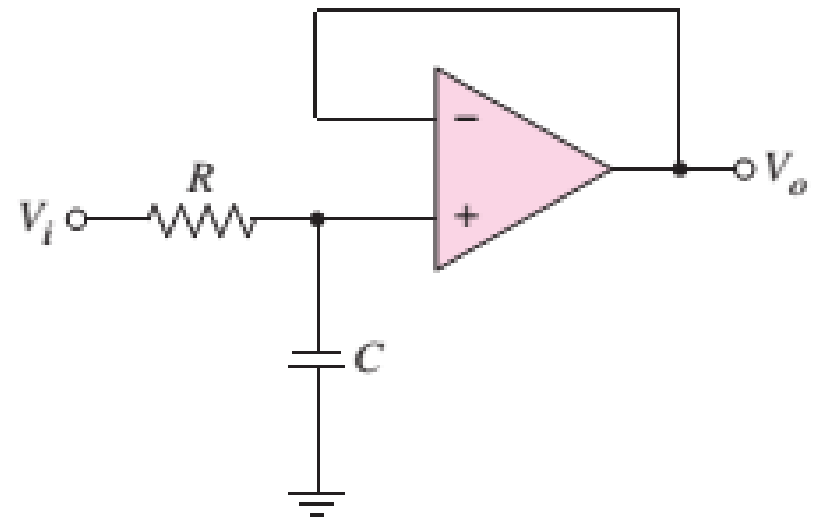(a) High-pass filter with voltage follower



(b)


(b) Low-pass filter with voltage follower

$$f_L = \frac{1}{2\pi RC}$$


$$f_H = \frac{1}{2\pi RC}$$




Active Filter

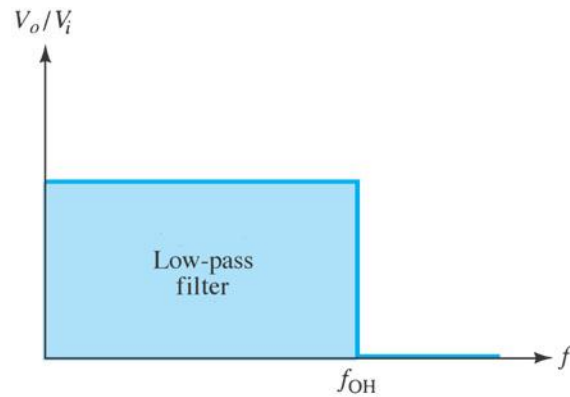

(a)

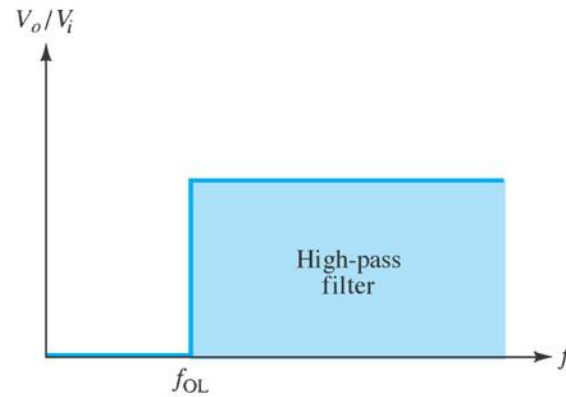

(b)


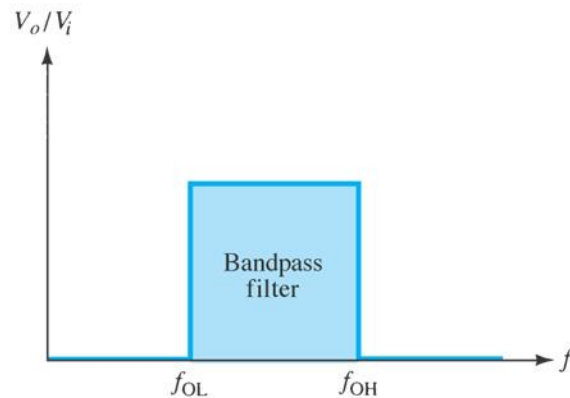


(c)

Ideal filter response: (a) low-pass; (b) high-pass; (c) bandpass.



Active Filter

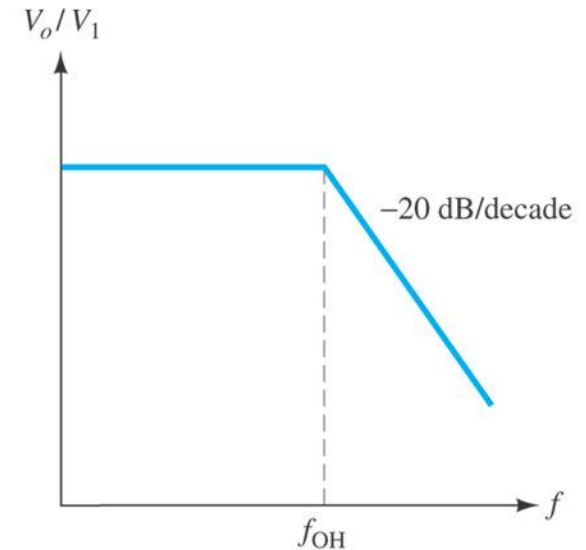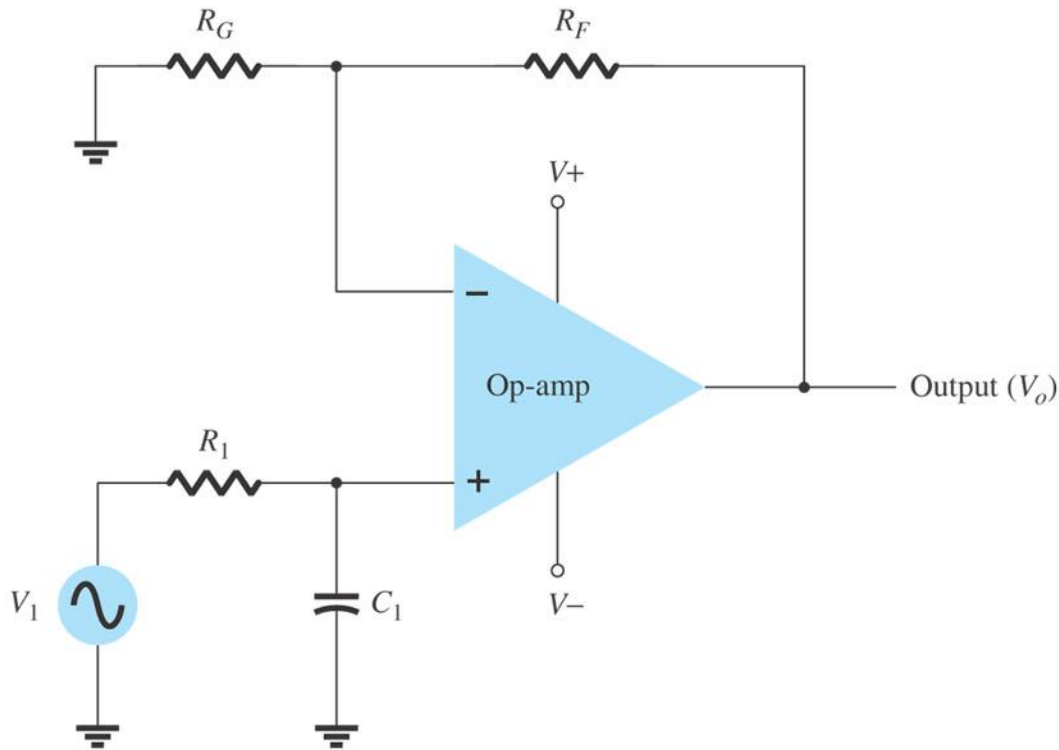

(a) First-order low-pass active filter


(b)

$$f_{OH} = \frac{1}{2\pi R_1 C_1}$$


$$A_v = 1 + \frac{R_F}{R_G}$$



Active Filter

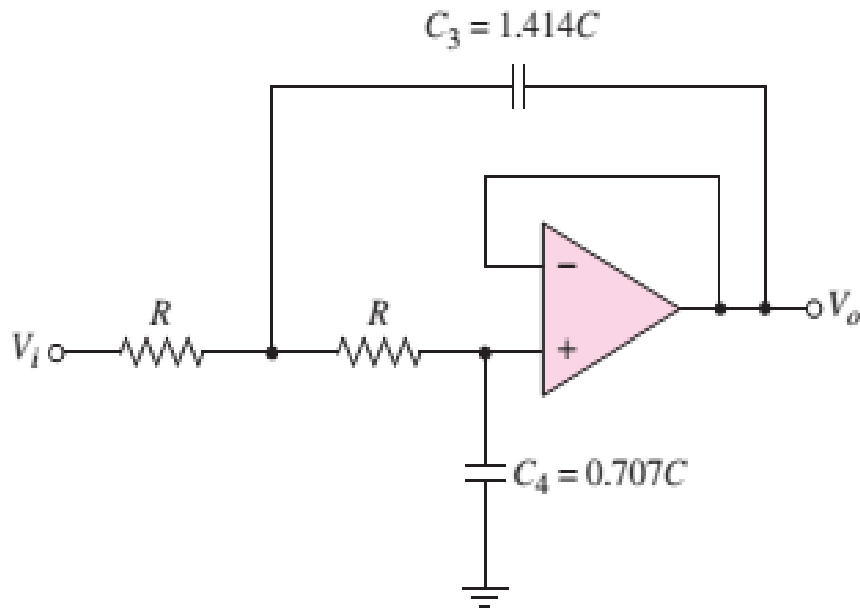

(a)

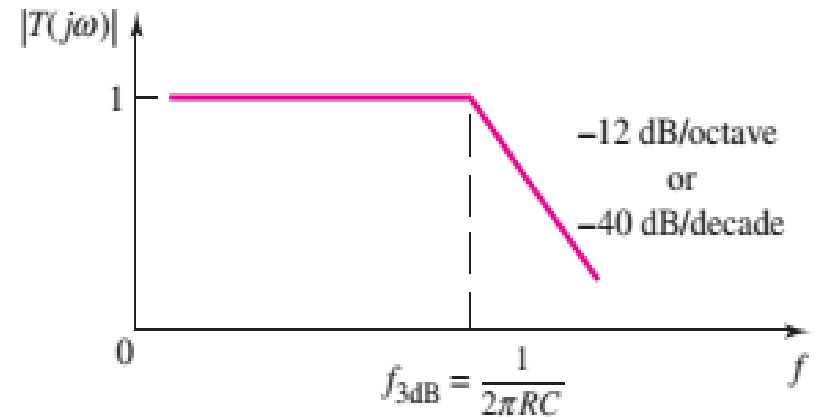



(b)

Second-order low-pass active filter

The roll-off can be made steeper by adding more RC networks.



Active Filter

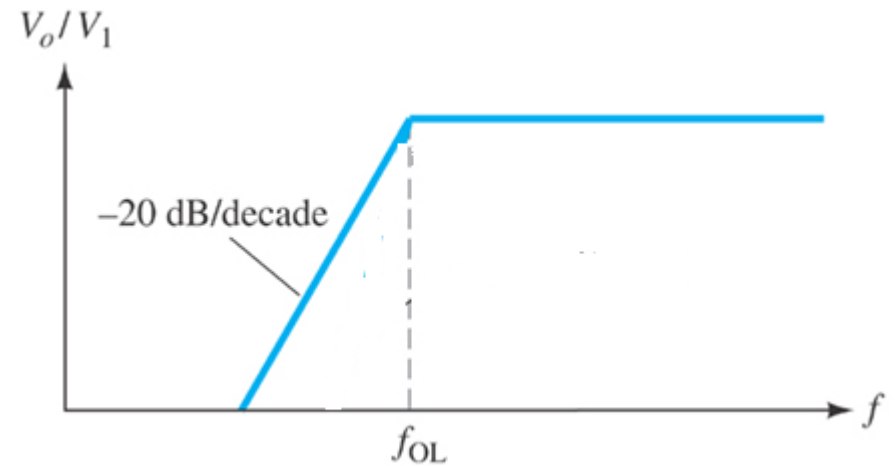
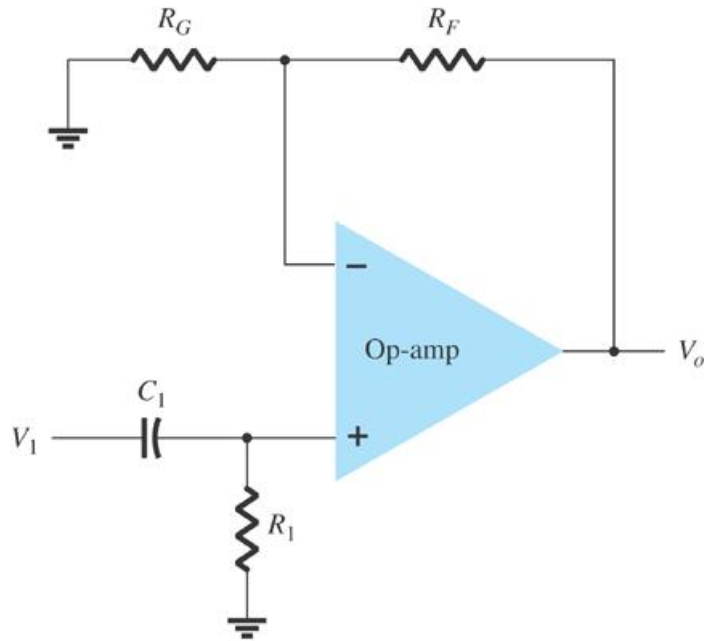


$$f_{OL} = \frac{1}{2\pi R_1 C_1}$$

$$A_v = 1 + \frac{R_F}{R_G}$$



Active Filter

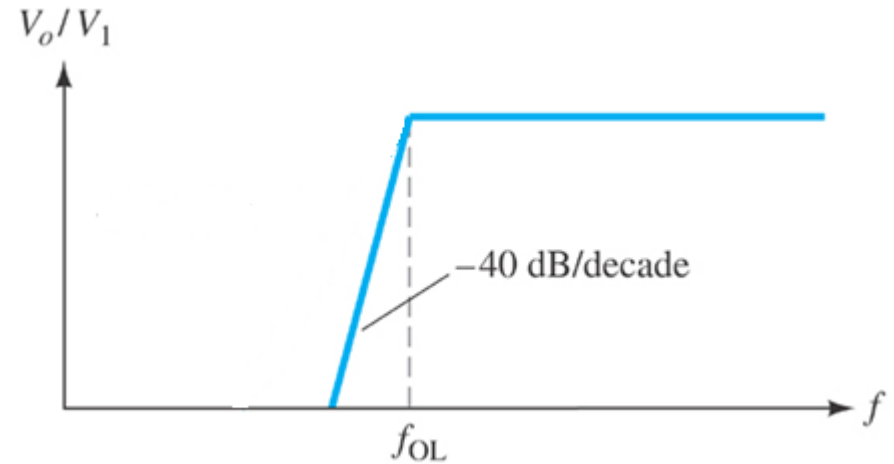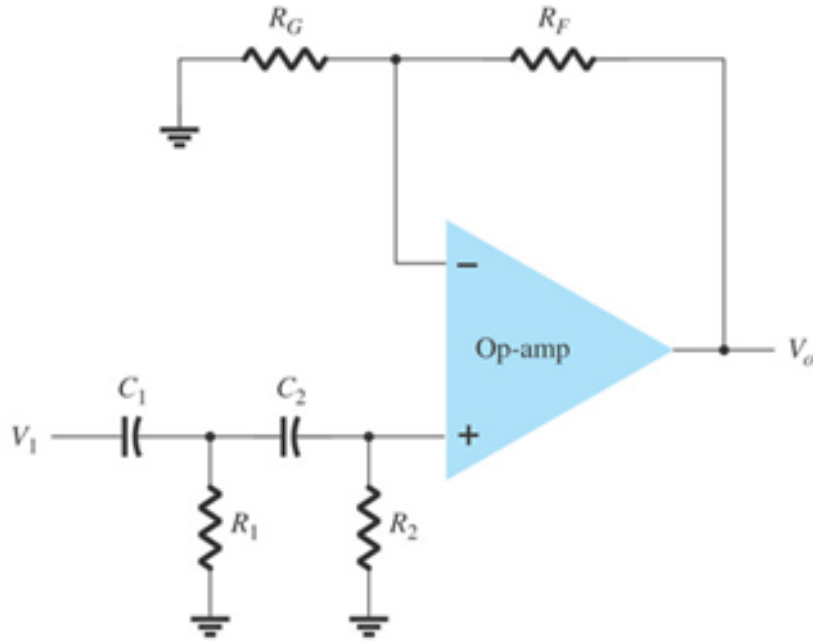


$$R_1 = R_2, C_1 = C_2$$

$$f_{OH} = \frac{1}{2\pi R_1 C_1}$$

$$A_v = 1 + \frac{R_F}{R_G}$$




Active Filter

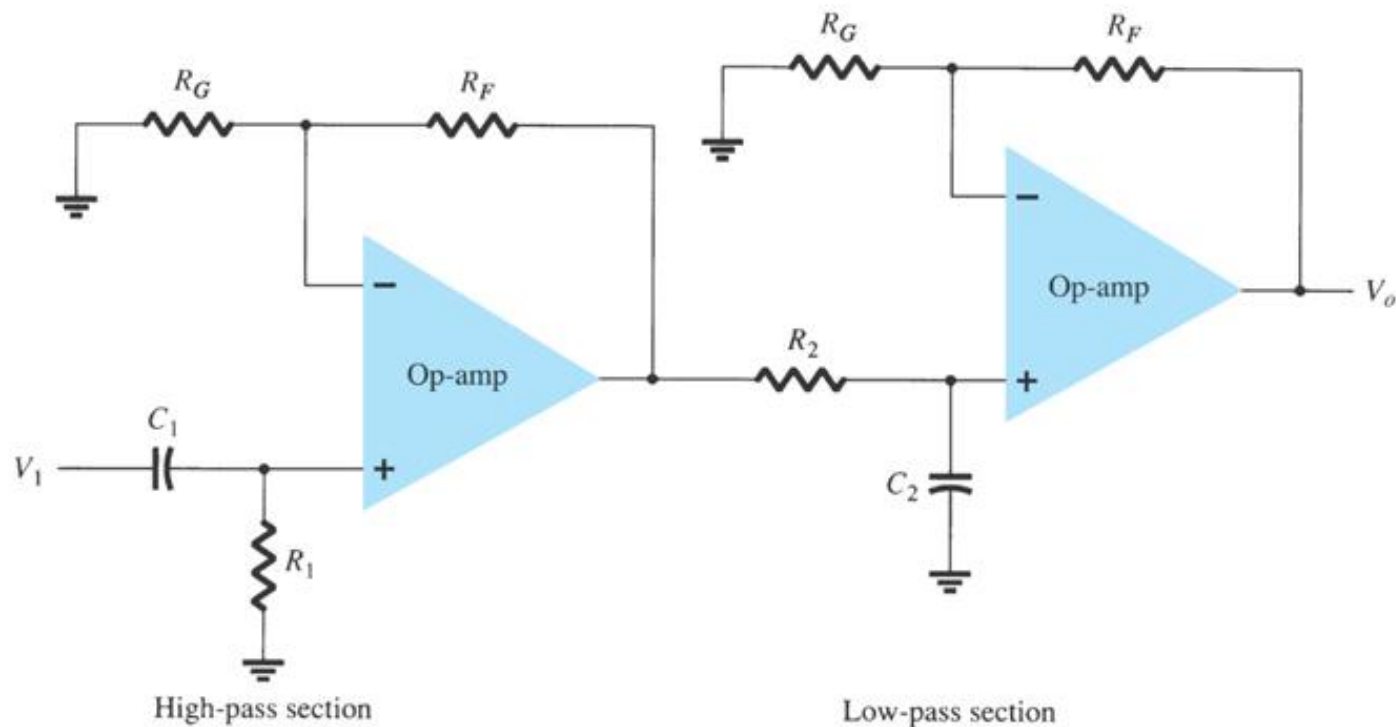


There are two cutoff frequencies: upper and lower. They can be calculated using the same low-pass cutoff and high-pass cutoff frequency formulas in the appropriate sections.



Active Filter

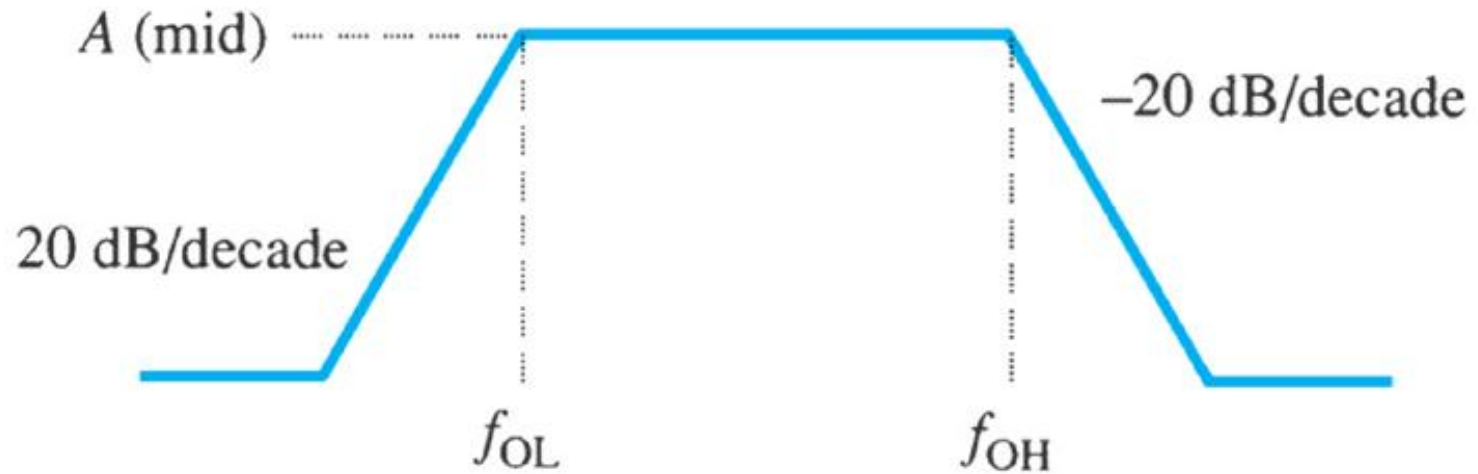

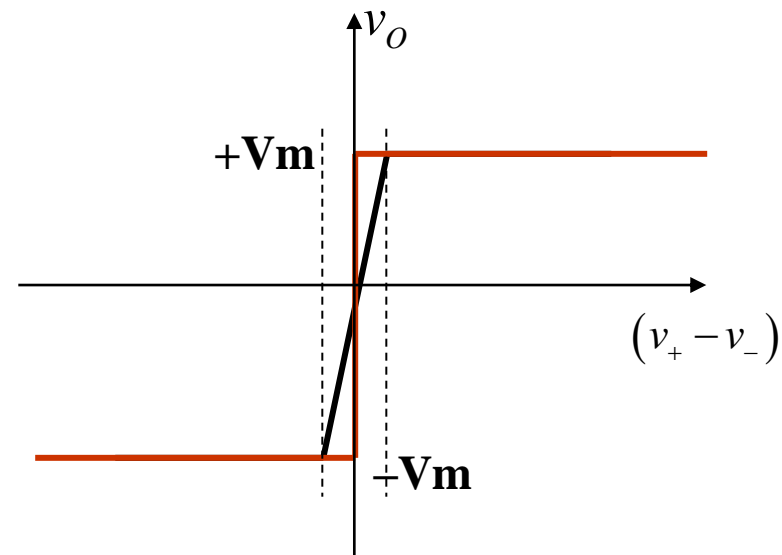

► $\mathbf{A}_d = \infty, \mathbf{A}_c = \mathbf{0}$

➤ $R_i = \infty$

$$v_+ > v_- \quad \longrightarrow \quad v_o = +v_{oM}$$

➤ $\mathbf{R}_0 = \mathbf{0}$

$$v_+ < v_- \quad \longrightarrow \quad v_o = -v_{oM}$$



Schmitt Trigger



Op-Amp Specifications

DC-Offset Parameters

Even when the input voltage is zero, an op-amp can have an output **offset**. The following can cause this offset:

Input offset voltage

Input offset current

Input offset voltage *and* input offset current

Input bias current



Op-Amp Specifications

Frequency Parameters

An op-amp is a wide-bandwidth amplifier. The following factors affect the bandwidth of the op-amp:

Gain


Slew rate



Op-Amp Specifications

Gain and Bandwidth

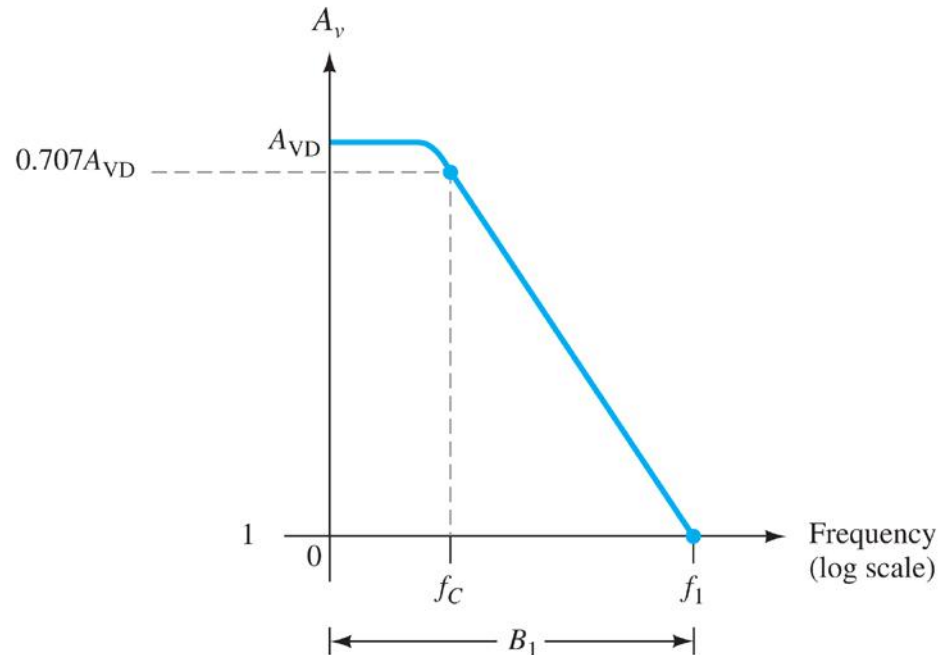The op-amp's high frequency response is limited by its internal circuitry. The plot shown is for an open loop gain (A_{OL} or A_{VD}). This means that the op-amp is operating at the highest possible gain with no feedback resistor.



$$f_1 = A_{VD}f_c$$

In the open loop mode, an op-amp has a narrow bandwidth. The bandwidth widens in closed-loop mode, but the gain is lower.



Op-Amp Specifications

Slew Rate (SR)

Slew rate (SR): The maximum rate at which an op-amp can change output without distortion.

$$SR = \frac{\Delta V_o}{\Delta t} \quad V/\mu s$$

The SR rating is listed in the specification sheets as the V/μs rating.



Op-Amp Specifications