

1. Define the region of operation for the 2N5457 JFET using the range of I_{DSS} and V_P provided. That is, sketch the transfer curve defined by the maximum I_{DSS} and V_P and the transfer curve for the minimum I_{DSS} and V_P . Then, shade in the resulting area between the two curves.

ANSWER:

From Fig. 6.22:

$$-0.5 \text{ V} < V_P < -6 \text{ V}$$

$$1 \text{ mA} < I_{DSS} < 5 \text{ mA}$$

For $I_{DSS} = 5 \text{ mA}$ and $V_P = -6 \text{ V}$:

$$V_{GS} = 0 \text{ V}, I_D = 5 \text{ mA}$$

$$V_{GS} = 0.3V_P = -1.8 \text{ V}, I_D = 2.5 \text{ mA}$$

$$V_{GS} = V_P/2 = -3 \text{ V}, I_D = 1.25 \text{ mA}$$

$$V_{GS} = V_P = -6 \text{ V}, I_D = 0 \text{ mA}$$


For $I_{DSS} = 1 \text{ mA}$ and $V_P = -0.5 \text{ V}$:

$$V_{GS} = 0 \text{ V}, I_D = 1 \text{ mA}$$

$$V_{GS} = 0.3V_P = -0.15 \text{ V}, I_D = 0.5 \text{ mA}$$

$$V_{GS} = V_P/2 = -0.25 \text{ V}, I_D = 0.25 \text{ mA}$$
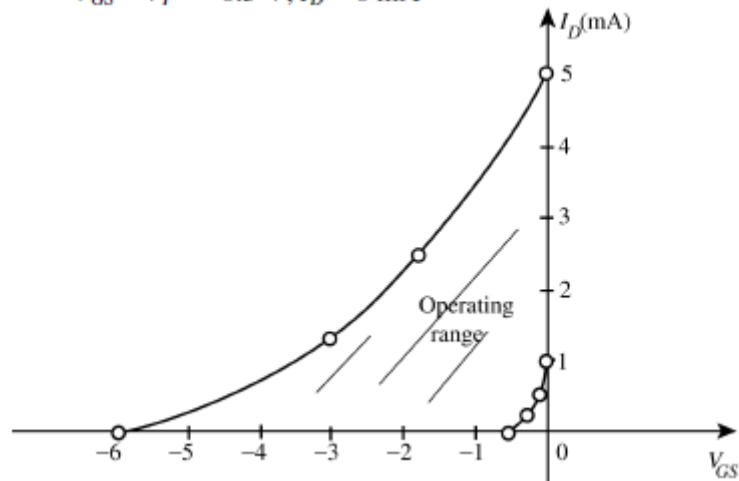
$$V_{GS} = V_P = -0.5 \text{ V}, I_D = 0 \text{ mA}$$



2. For the 2N5457 JFET, what is the power rating at a typical operating temperature of 45°C using the $5.0 \text{ mW}/^\circ\text{C}$ derating factor.

ANSWER

$$\text{At } 25^\circ\text{C}, P_D = 625 \text{ mW}$$

$$45^\circ\text{C} - 25^\circ\text{C} = 20^\circ\text{C}$$


$$20^\circ\text{C} \times \frac{5 \text{ mW}}{^\circ\text{C}} = 100 \text{ mW}$$

$$P_D' = 625 \text{ mW} - 100 \text{ mW} \\ = 525 \text{ mW}$$


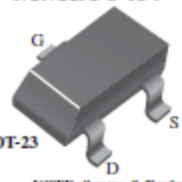
:

ABSOLUTE MAXIMUM RATINGS

| Symbol | Parameter | Value | Units |
|----------------|--|-------------|-------|
| V_{DS} | Drain-Source Voltage | 25 | V |
| V_{DG} | Drain-Gate Voltage | 25 | V |
| V_{GS} | Gate-Source Voltage | -25 | V |
| I_{GF} | Forward Gate Current | 10 | mA |
| T_J, T_{stg} | Operating and Storage Junction Temperature Range | -55 to +150 | °C |



2N5457 **MMBF5457**

TO-92 SOT-23

NOTE: Source & Drain are interchangeable

N-Channel General Purpose Amplifier
This device is a low-level audio amplifier and switching transistor, and can be used for analog switching applications.

THERMAL CHARACTERISTICS

| Symbol | Characteristic | Max | | Units |
|-----------------|---|--------|-----------|-------|
| | | 2N5457 | *MMBF5457 | |
| P_D | Total Device Dissipation Derate above 25°C | 625 | 350 | mW |
| | | 5.0 | 2.8 | mW/°C |
| $R_{\theta JC}$ | Thermal Resistance, Junction to Case | 125 | | °C/W |
| $R_{\theta JA}$ | Thermal Resistance, Junction to Ambient | 357 | 556 | °C/W |

ELECTRICAL CHARACTERISTICS $T_A = 25^\circ\text{C}$ unless otherwise noted

| Symbol | Parameter | Test Conditions | Min | Typ | Max | Units |
|--------|-----------|-----------------|-----|-----|-----|-------|
|--------|-----------|-----------------|-----|-----|-----|-------|

OFF CHARACTERISTICS

| | | | | | | |
|---------------|-------------------------------|---|-----------|------|------|----|
| $V_{(BR)GSS}$ | Gate-Source Breakdown Voltage | $I_G = 10 \mu\text{A}, V_{DS} = 0$ | -25 | | | V |
| I_{GSS} | Gate Reverse Current | $V_{GS} = -15 \text{ V}, V_{DS} = 0$ | | | -1.0 | nA |
| | | $V_{GS} = -15 \text{ V}, V_{DS} = 0, T_A = 100^\circ\text{C}$ | | | -200 | nA |
| $V_{GS(off)}$ | Gate-Source Cutoff Voltage | $V_{DS} = 15 \text{ V}, I_D = 10 \text{ nA}$ | 5457 -0.5 | | -6.0 | V |
| V_{GS} | Gate-Source Voltage | $V_{DS} = 15 \text{ V}, I_D = 100 \mu\text{A}$ | 5457 | -2.5 | | V |


ON CHARACTERISTICS

| | | | | | | | |
|-----------|---------------------------------|-------------------------------------|------|-----|-----|-----|----|
| I_{DSS} | Zero-Gate Voltage Drain Current | $V_{DS} = 15 \text{ V}, V_{GS} = 0$ | 5457 | 1.0 | 3.0 | 5.0 | mA |
|-----------|---------------------------------|-------------------------------------|------|-----|-----|-----|----|

SMALL SIGNAL CHARACTERISTICS

| | | | | | | | |
|-----------|------------------------------|---|------|------|-----|------|------------------|
| g_{fs} | Forward Transfer Conductance | $V_{DS} = 15 \text{ V}, V_{GS} = 0, f = 1.0 \text{ kHz}$ | 5457 | 1000 | | 5000 | μmhos |
| g_{os} | Output Conductance | $V_{DS} = 15 \text{ V}, V_{GS} = 0, f = 1.0 \text{ MHz}$ | | | 10 | 50 | μmhos |
| C_{iss} | Input Capacitance | $V_{DS} = 15 \text{ V}, V_{GS} = 0, f = 1.0 \text{ MHz}$ | | | 4.5 | 7.0 | pF |
| C_{rss} | Reverse Transfer Capacitance | $V_{DS} = 15 \text{ V}, V_{GS} = 0, f = 1.0 \text{ MHz}$ | | | 1.5 | 3.0 | pF |
| NF | Noise Figure | $V_{DS} = 15 \text{ V}, V_{GS} = 0, f = 1.0 \text{ kHz}, R_G = 1.0 \text{ megohm}, BW = 1.0 \text{ Hz}$ | | | | 3.0 | dB |

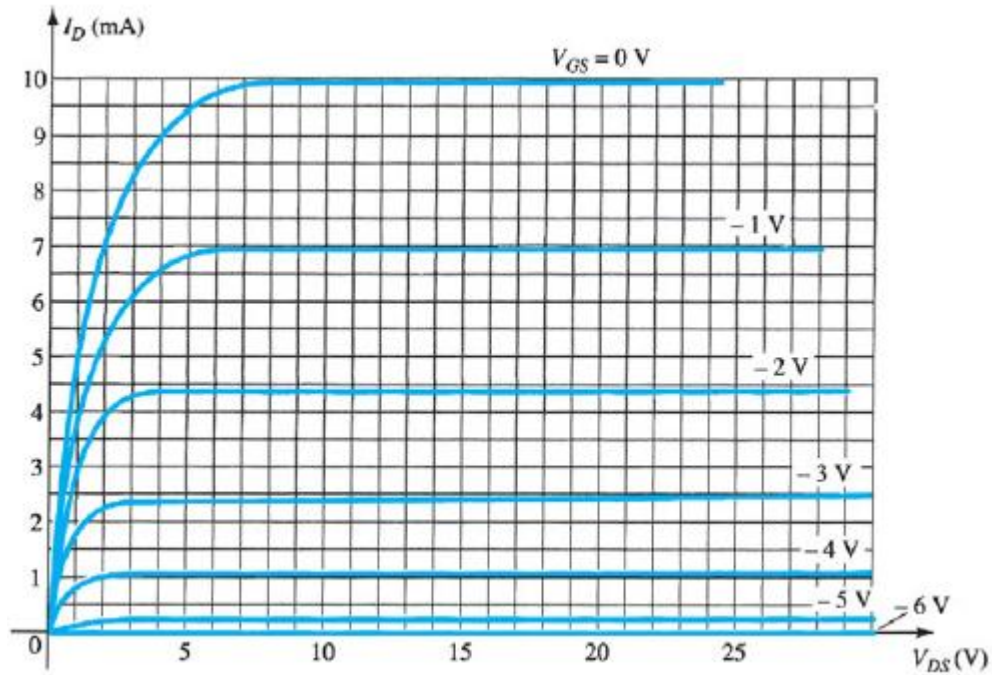- Define the region of operation for the JFET below, if $V_{DS\text{max}} = 30 \text{ V}$ and $P_{D\text{max}} = 100 \text{ mW}$.




ANSWER:

$$V_{DS} = V_{DS_{\max}} = 25 \text{ V}, I_D = \frac{P_{D_{\max}}}{V_{DS_{\max}}} = \frac{100 \text{ mW}}{25 \text{ V}} = 4 \text{ mA}$$

$$I_D = I_{DSS} = 10 \text{ mA}, V_{DS} = \frac{P_{D_{\max}}}{I_{DSS}} = \frac{100 \text{ mW}}{10 \text{ mA}} = 10 \text{ V}$$

$$V_D = 20 \text{ V}, I_D = 6.67 \text{ mA}$$
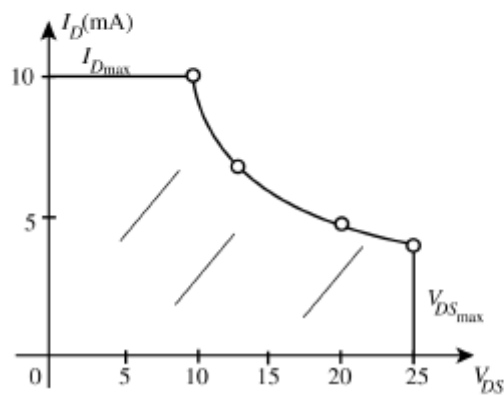
$$V_D = 15 \text{ V}, I_D = 5 \text{ mA}$$



4.

a. Given $V_{GS(Th)} = 4 \text{ V}$ and $I_{D(on)} = 4 \text{ mA}$ at $V_{GS(on)} = 6 \text{ V}$, determine k and write the general expression for I_D in the format of

$$I_D = k(V_{GS} - V_T)^2$$

b. Sketch the transfer characteristics for the device of part (a).

c. Determine I_D for the device of part (a) at $V_{GS} = 2, 5, \text{ and } 10 \text{ V}$.

ANSWER:


$$(a) \quad k = \frac{I_{D(on)}}{(V_{GS(on)} - V_T)^2} = \frac{4 \text{ mA}}{(6 \text{ V} - 4 \text{ V})^2} = 1 \text{ mA/V}^2$$

$$I_D = k(V_{GS} - V_T)^2 = 1 \times 10^{-3}(V_{GS} - 4 \text{ V})^2$$

| (b) | V_{GS} | I_D | For $V_{GS} < V_T = 4 \text{ V}$, $I_D = 0 \text{ mA}$ |
|-----|----------|-------|---|
| | 4 V | 0 mA | |
| | 5 V | 1 mA | |
| | 6 V | 4 mA | |
| | 7 V | 9 mA | |
| | 8 V | 16 mA | |

| (c) | V_{GS} | I_D | ($V_{GS} < V_T$) |
|-----|----------|-------|--------------------|
| | 2 V | 0 mA | |
| | 5 V | 1 mA | |
| | 10 V | 36 mA | |

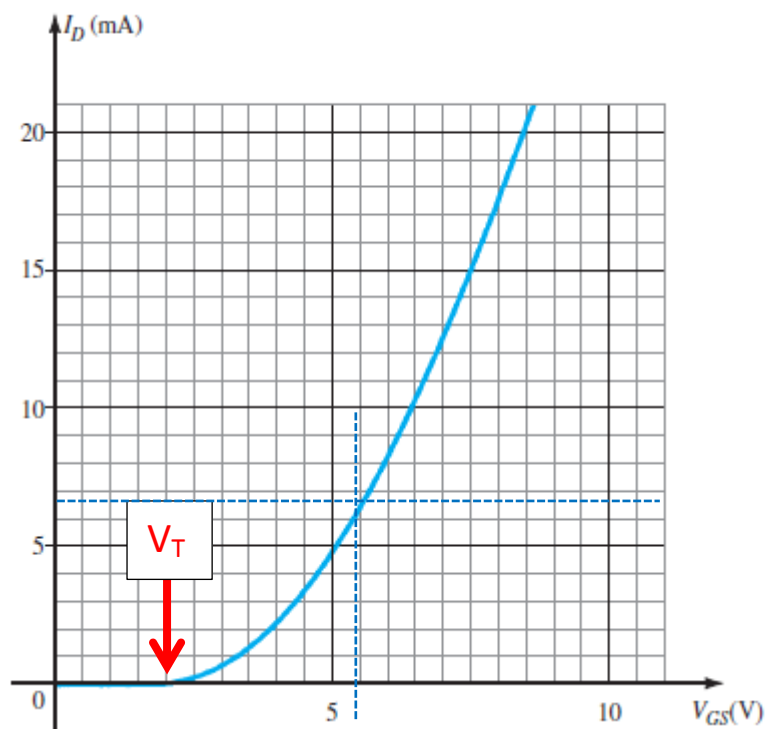5. Given the transfer characteristics of Fig. 6.55, determine V_T and k and write the general equation for I_D .



6:38

ANSWER

From Fig. 6.58, $V_T = 2.0 \text{ V}$

At $I_D = 6.5 \text{ mA}$, $V_{GS} = 5.5 \text{ V}$:

Choose the I_D in the linear region

$$I_D = 5.31 \times 10^{-4}(V_{GS} - 2)^2$$


$$I_D = k(V_{GS} - V_T)^2$$

$$6.5 \text{ mA} = k(5.5 \text{ V} - 2 \text{ V})^2$$

$$k = 5.31 \times 10^{-4}$$

6. For the network determine:

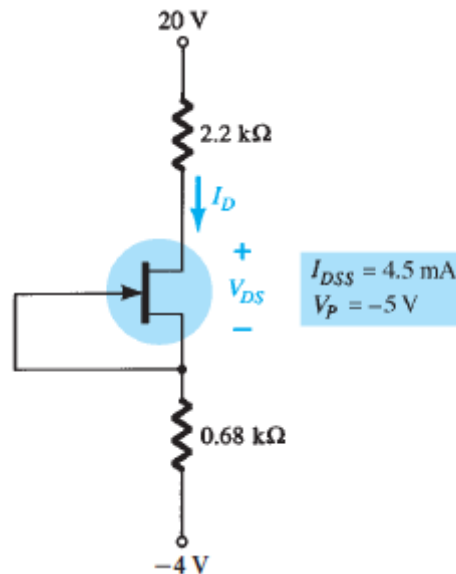- a. I_D .
- b. V_{DS} .
- c. V_D .
- d. V_S .



ANSWER

- (a) $V_{GS} = 0 \text{ V}$
 $\therefore I_D = I_{DSS} = 4.5 \text{ mA}$
- (b) $V_{DS} = V_{DD} - I_D(R_D + R_S)$
 $= 20 \text{ V} + 4 \text{ V} - (4.5 \text{ mA})(2.2 \text{ k}\Omega + 0.68 \text{ k}\Omega)$
 $= 24 \text{ V} - 12.96$
 $= 11.04 \text{ V}$
- (c) $V_D = V_{DD} - I_D R_D$
 $= 20 \text{ V} - (4.5 \text{ mA})(2.2 \text{ k}\Omega)$
 $= 10.1 \text{ V}$
- (d) $-4 \text{ V} + I_S R_S - V_S = 0$
 $V_S = I_S R_S - 4 \text{ V} = I_D R_S - 4 \text{ V} = (4.5 \text{ mA})(0.68 \text{ k}\Omega) - 4 \text{ V}$
 $= 3.06 \text{ V} - 4 \text{ V}$
 $= -0.94 \text{ V}$

7. Determine the value of R_S for the network to establish $V_D = 10 \text{ V}$.

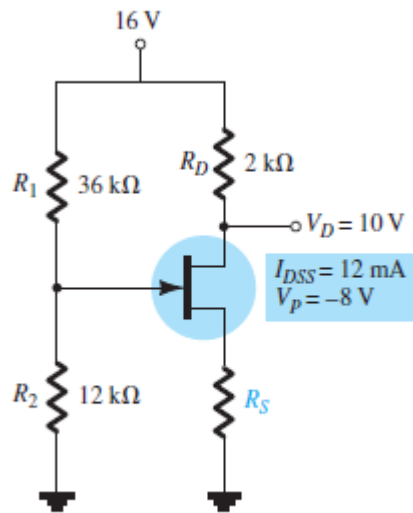



FIG. 7.87

ANSWER

$$I_{D_Q} = \frac{16 \text{ V} - 10 \text{ V}}{2 \text{ k}\Omega} = \frac{6 \text{ V}}{2 \text{ k}\Omega} = 3 \text{ mA}$$


$$V_G = \frac{12 \text{ k}\Omega (16 \text{ V})}{12 \text{ k}\Omega + 36 \text{ k}\Omega} = 4 \text{ V}$$
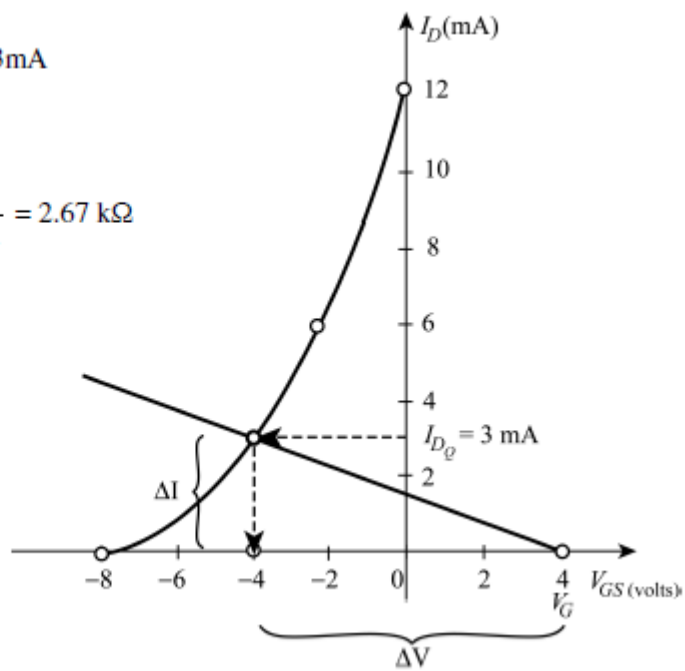
$$R_S = \frac{\Delta V}{\Delta I} = \frac{4 \text{ V} + 4 \text{ V}}{3 \text{ mA}} = \frac{8 \text{ V}}{3 \text{ mA}} = 2.67 \text{ k}\Omega$$



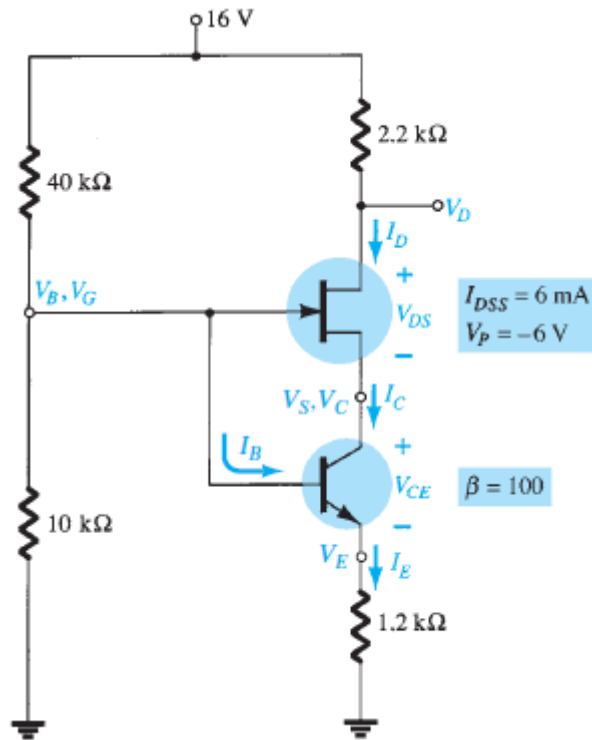8. For the combination network of, determine:

- V_B and V_G .
- V_E .
- I_E , I_C , and I_D .
- I_B .
- V_C , V_S , and V_D .
- V_{CE} .
- V_{DS} .



ANSWER:

Testing:

$$\begin{aligned}\beta R_E &\geq 10R_2 \\ (100)(1.2 \text{ k}\Omega) &\geq 10(10 \text{ k}\Omega) \\ 120 \text{ k}\Omega &> 100 \text{ k}\Omega \text{ (satisfied)}\end{aligned}$$

$$\begin{aligned}\text{(a)} \quad V_B = V_G &= \frac{R_2 V_{DD}}{R_1 + R_2} = \frac{10 \text{ k}\Omega (16 \text{ V})}{40 \text{ k}\Omega + 10 \text{ k}\Omega} \\ &= 3.2 \text{ V}\end{aligned}$$

$$\text{(b)} \quad V_E = V_B - V_{BE} = 3.2 \text{ V} - 0.7 \text{ V} = 2.5 \text{ V}$$

$$\begin{aligned}\text{(c)} \quad I_E &= \frac{V_E}{R_E} = \frac{2.5 \text{ V}}{1.2 \text{ k}\Omega} = 2.08 \text{ mA} \\ I_C &\cong I_E = 2.08 \text{ mA} \\ I_D &= I_C = 2.08 \text{ mA}\end{aligned}$$

$$(d) \quad I_B = \frac{I_C}{\beta} = \frac{2.08 \text{ mA}}{100} = \mathbf{20.8 \mu A}$$

$$\begin{aligned}
 (e) \quad V_C &= V_G - V_{GS} \\
 V_{GS} &= V_P \left(1 - \sqrt{\frac{I_D}{I_{DSS}}} \right) \\
 &= (-6 \text{ V}) \left(1 - \sqrt{\frac{2.08 \text{ mA}}{6 \text{ mA}}} \right) \\
 &= -2.47 \text{ V} \\
 V_C &= 3.2 - (-2.47 \text{ V}) \\
 &= \mathbf{5.67 \text{ V}} \\
 V_S &= V_C = \mathbf{5.67 \text{ V}} \\
 V_D &= V_{DD} - I_D R_D \\
 &= 16 \text{ V} - (2.08 \text{ mA})(2.2 \text{ k}\Omega) \\
 &= \mathbf{11.42 \text{ V}}
 \end{aligned}$$

$$(f) \quad V_{CE} = V_C - V_E = 5.67 \text{ V} - 2.5 \text{ V} = \mathbf{3.17 \text{ V}}$$

$$(g) \quad V_{DS} = V_D - V_S = 11.42 \text{ V} - 5.67 \text{ V} = \mathbf{5.75 \text{ V}}$$