
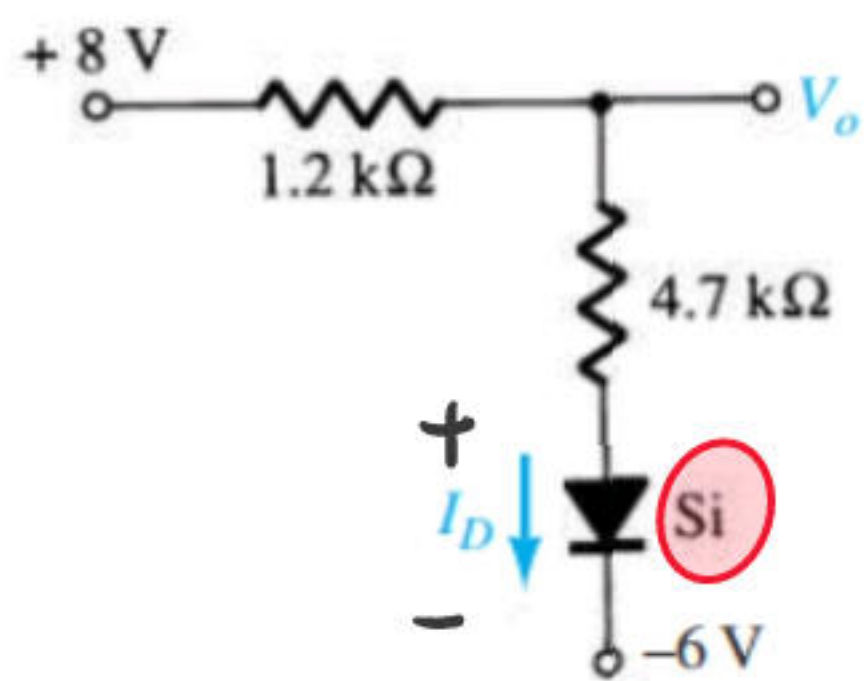


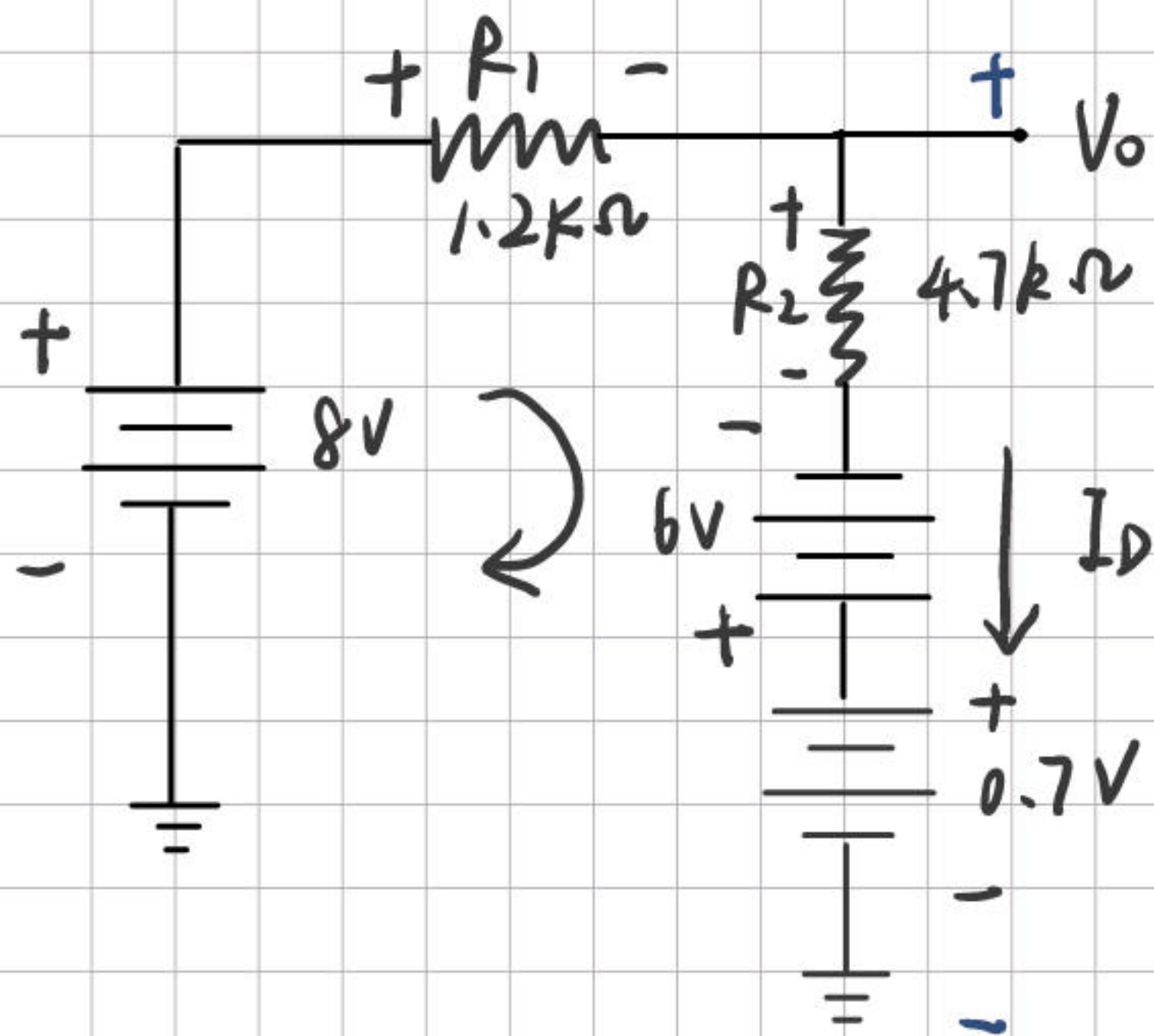Determine the level of V_o for the network below.



Solution: The diode is on, the equivalent circuit is,



KVL:

$$R_1 \cdot I_D + R_2 \cdot I_D - 6 - 8 + 0.7 = 0$$

$$I_D \cdot (1.2k + 4.7k) = 13.3$$

$$I_D = \frac{13.3}{1.2k + 4.7k} \approx 2.25 \text{ mA}$$


$$\therefore V_{R2} = I_D R_2 \approx 10.56 \text{ V}$$

KVL:


$$V_o - 0.7 + 6 - 10.56 = 0$$

$$V_o = 5.26 \text{ V}$$

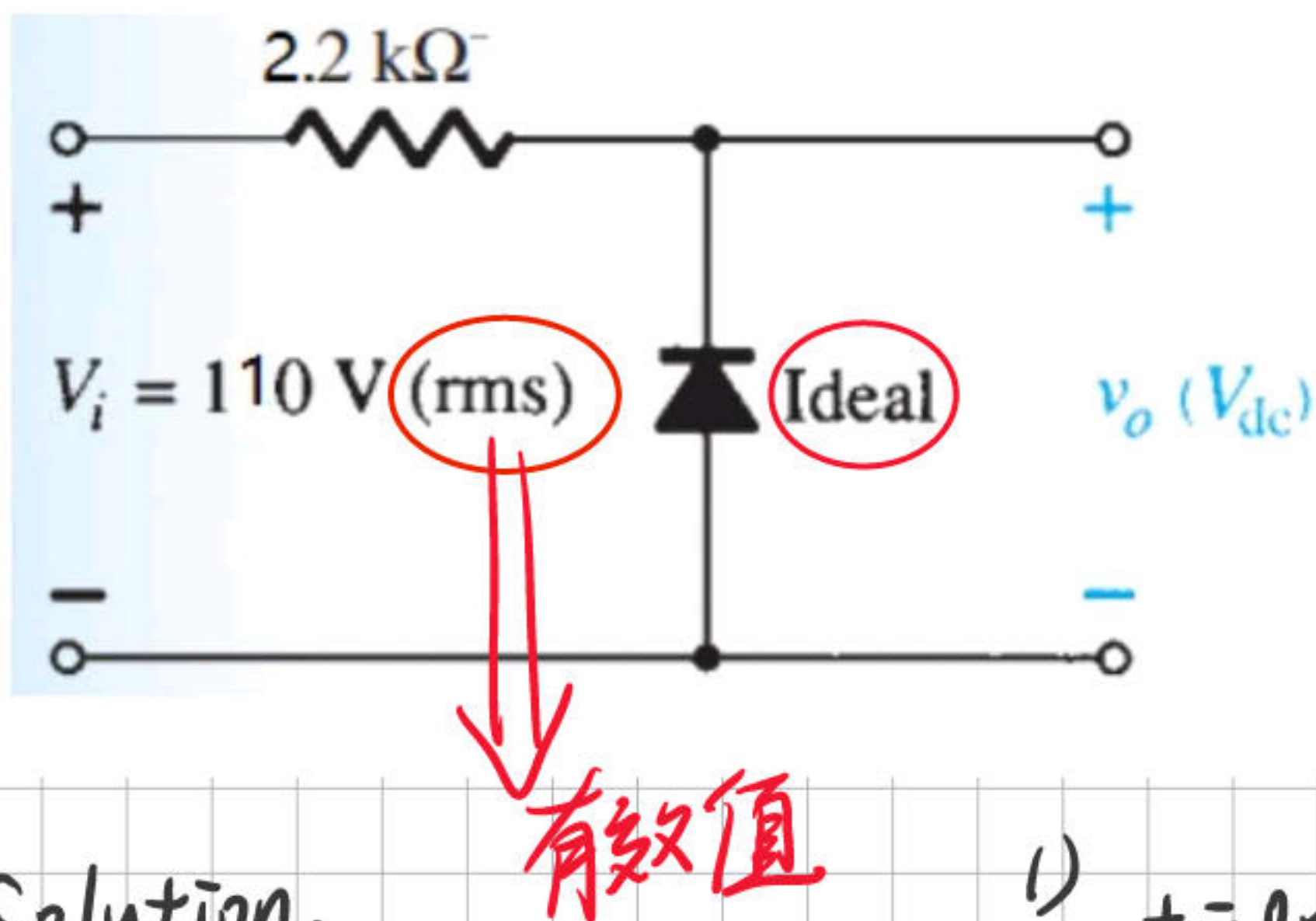
For the network of Fig.2.111, sketch v_o and determine V_{dc} .




Solution:

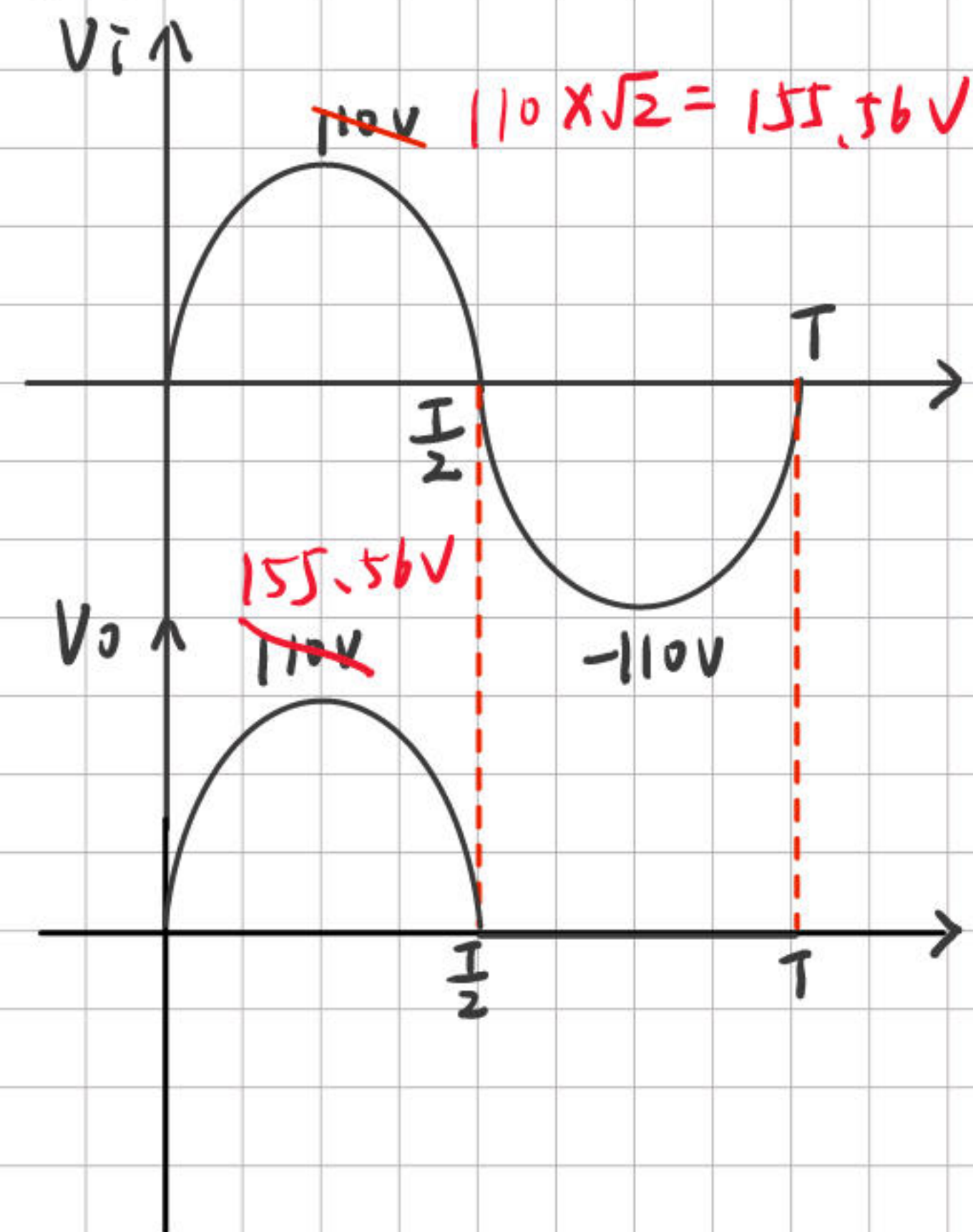

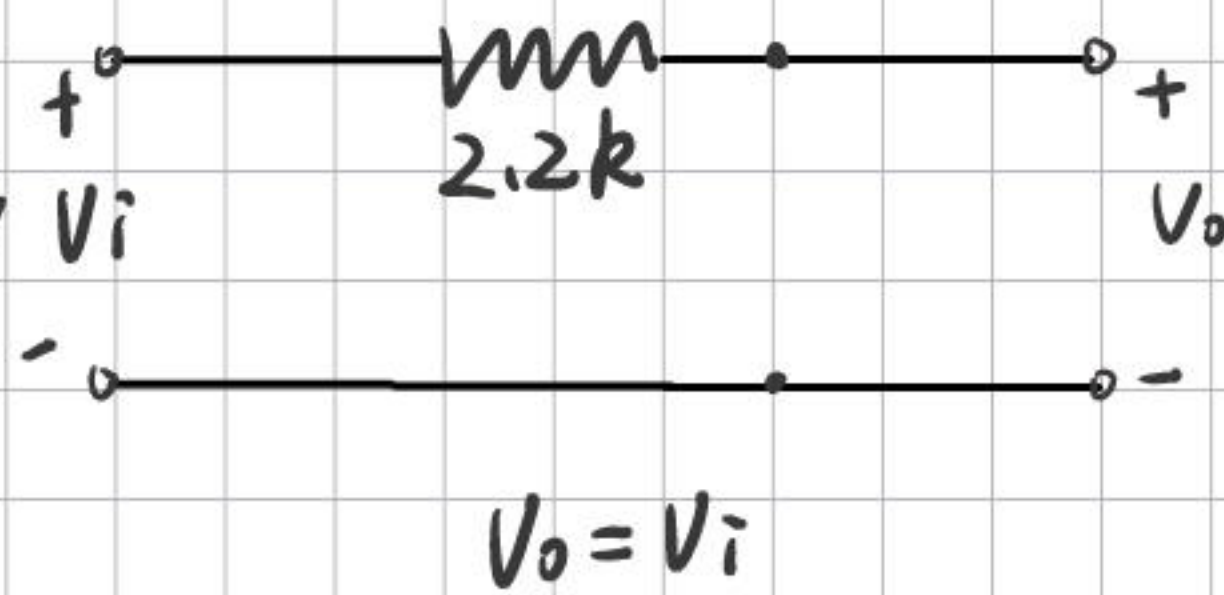1) $t = 0 \sim \frac{T}{2}$, D is off,
the equivalent circuit is,



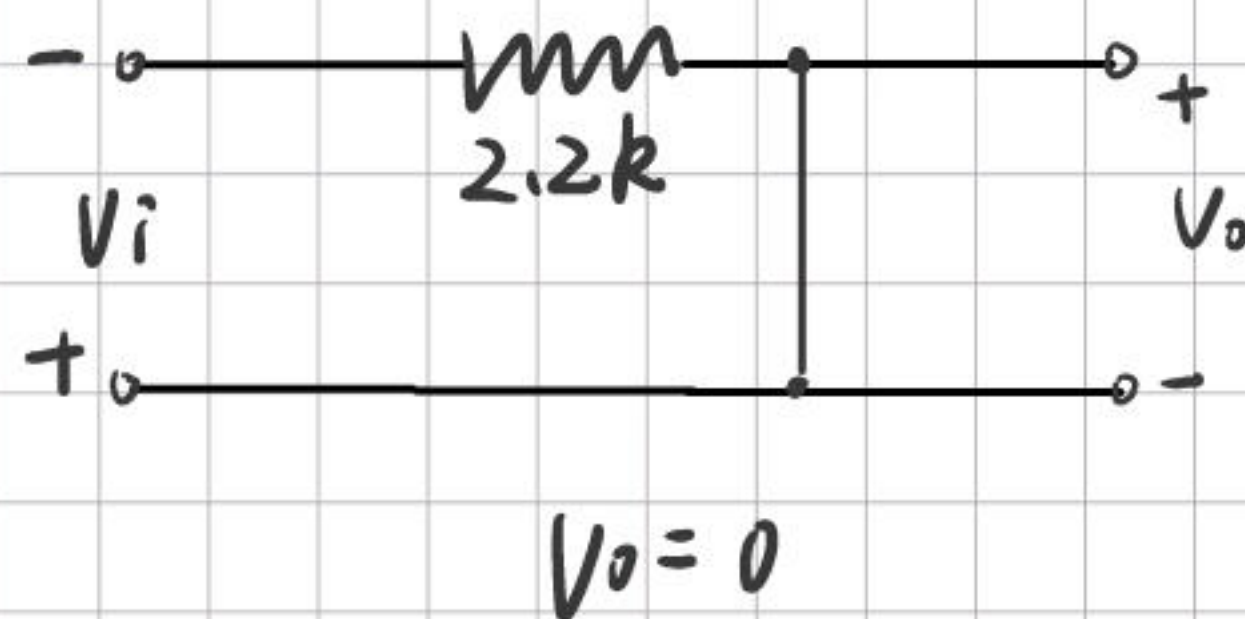2) $t = \frac{T}{2} \sim T$, D is on,
the equivalent circuit is,





$$\therefore V_{dc} = 0.318 \text{ V/m}$$


$$= 155.56 \times 0.318$$

$$\approx 49.47 \text{ V}$$

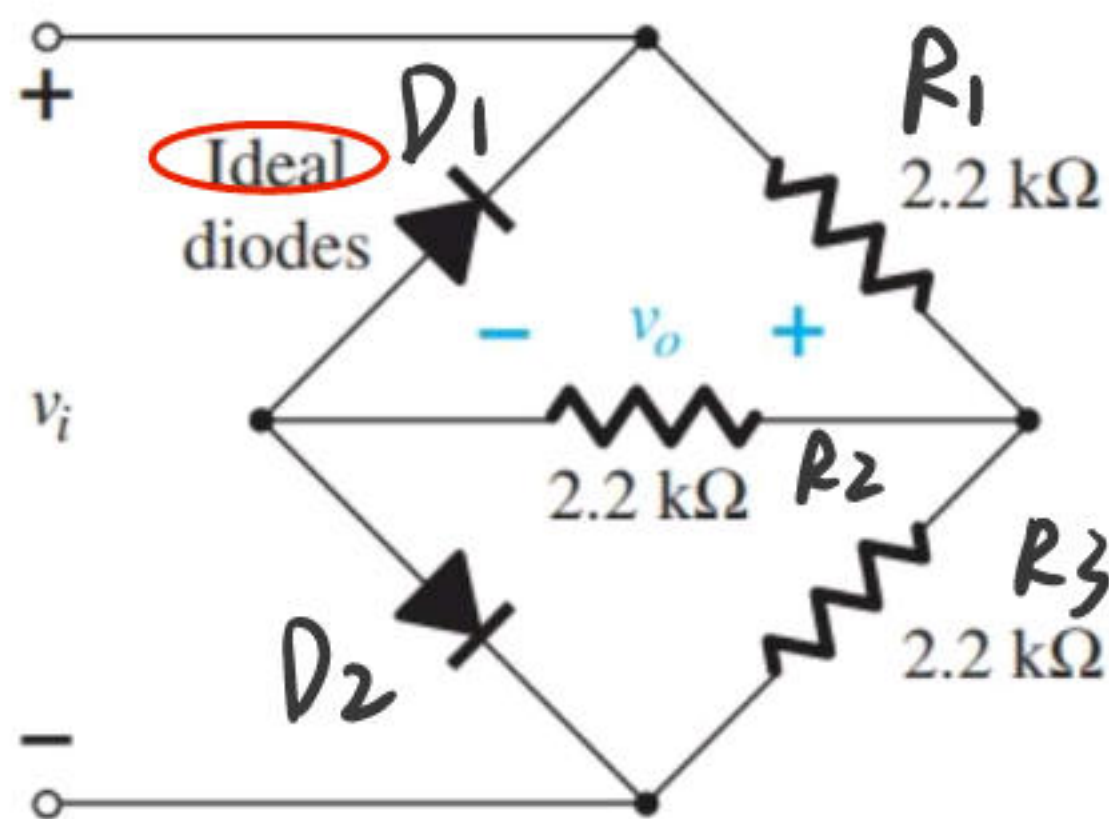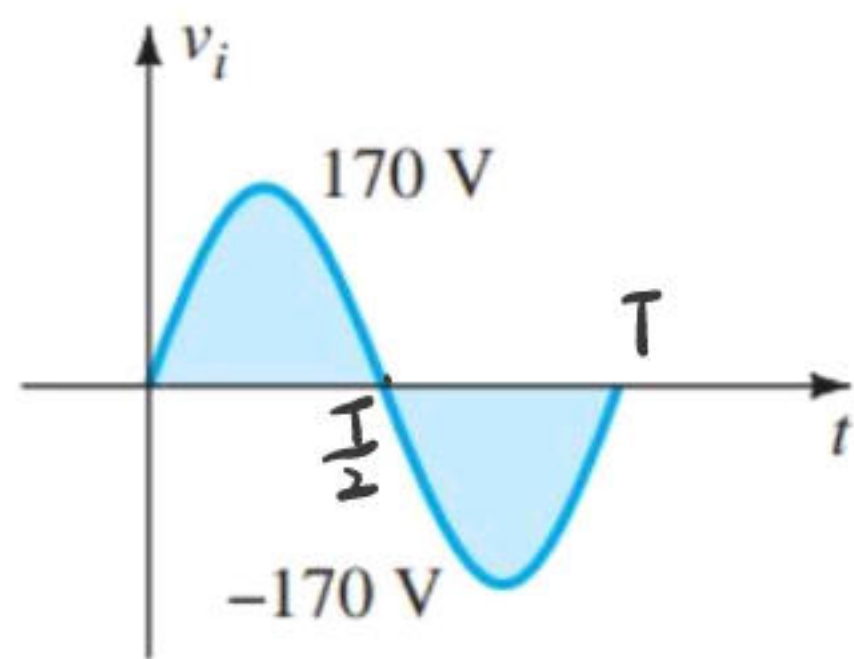Determine v_o for the network of Fig. 2.116 and determine the dc voltage available.



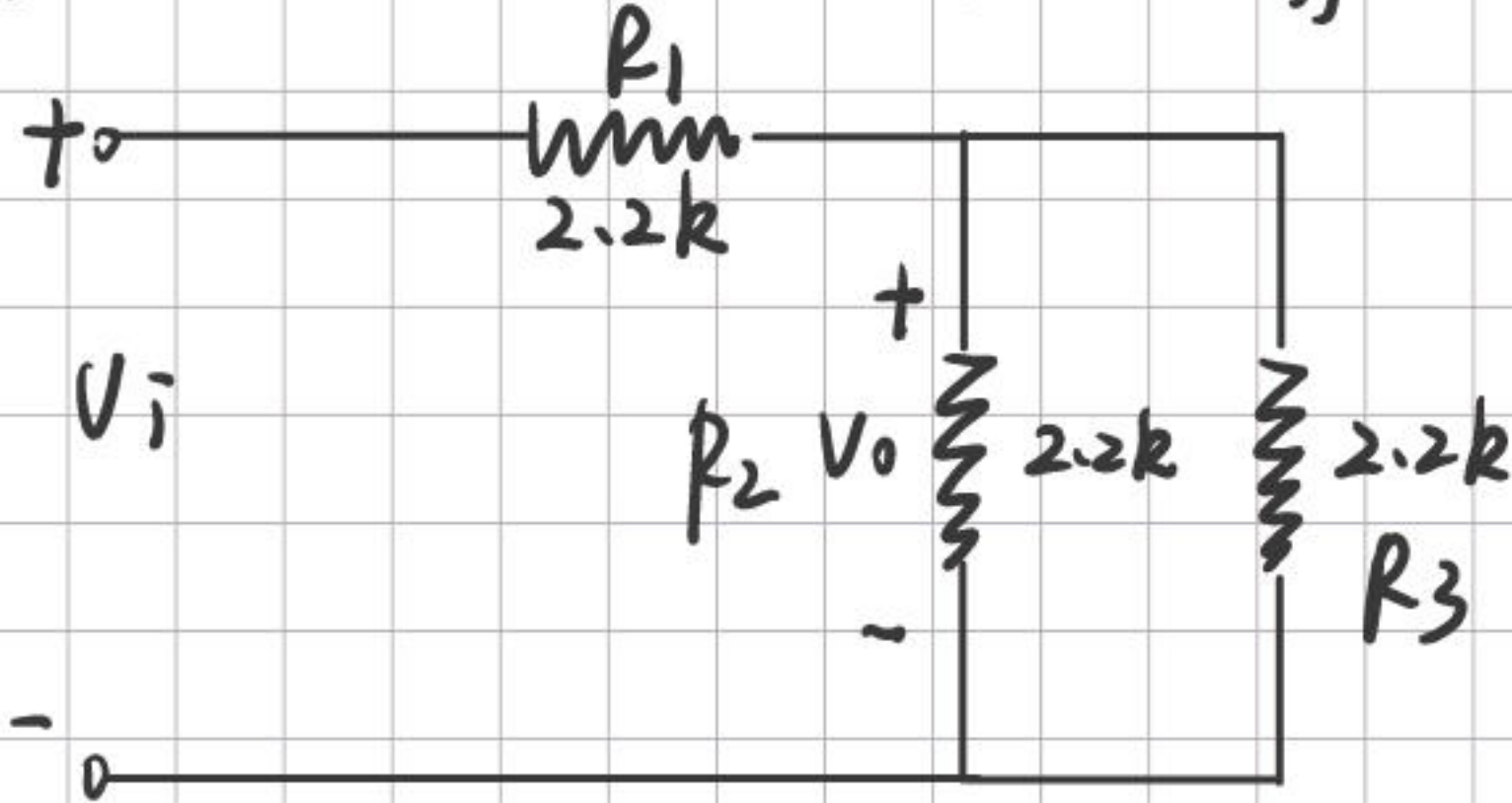
Solution: 1) $t = 0 \sim \frac{T}{2}$, D_1 is off, D_2 is on, the equivalent circuit is,



$$R_p = \frac{2.2k \cdot 2.2k}{2.2k + 2.2k} = 1.1k\Omega$$

$$V_o = \frac{R_p}{R_1 + R_p} V_i = \frac{1.1k}{3.3k} \cdot V_i = \frac{1}{3} V_i$$

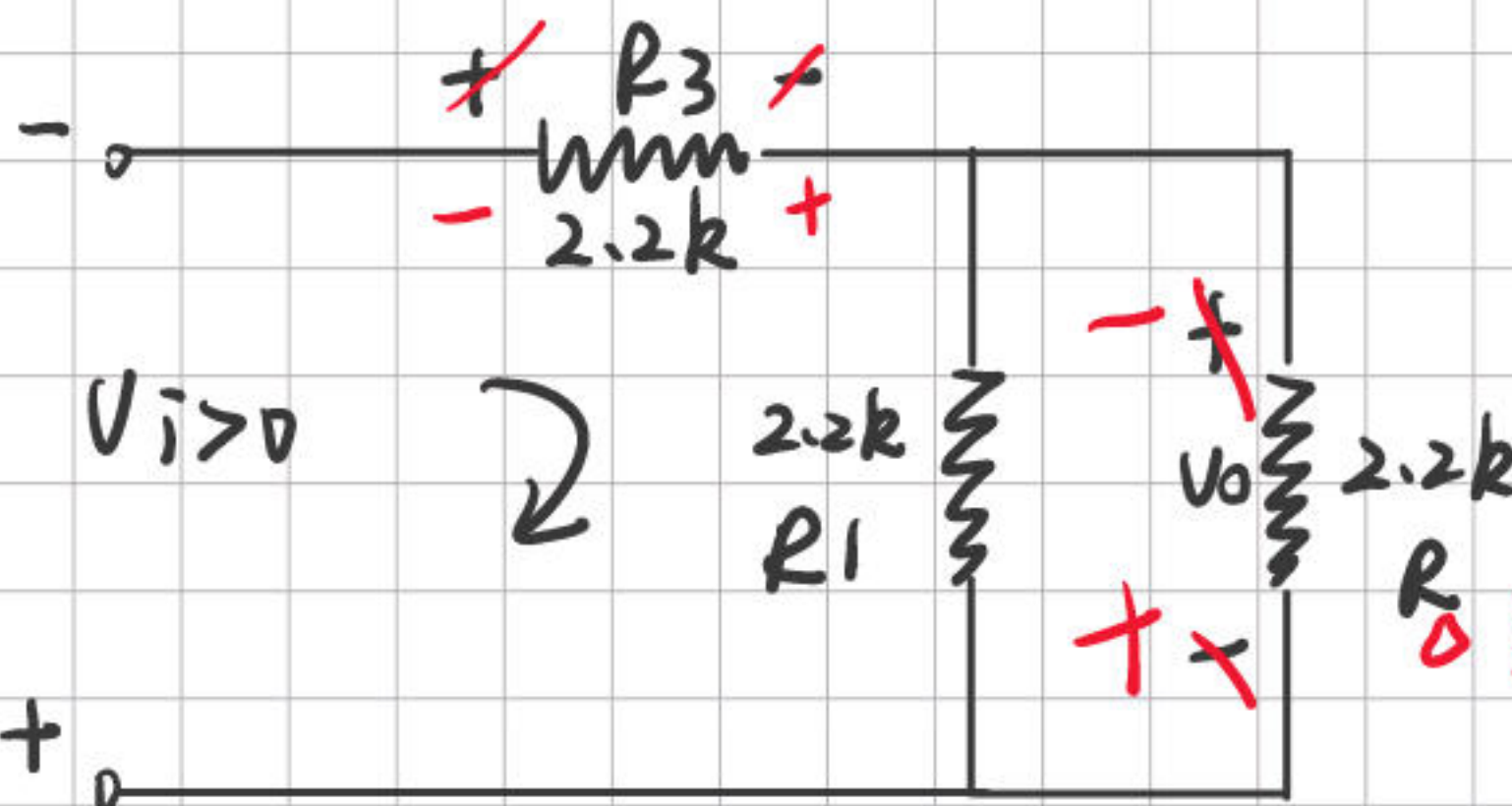2) $t = \frac{T}{2} \sim T$, D_1 is on, D_2 is off, the equivalent circuit is,



$$R_p' = \frac{2.2k \cdot 2.2k}{2.2k + 2.2k} = 1.1k\Omega$$

KVL:

$$V_{R3} + V_{R_p'} + V_i = 0$$

$$2V_{R_p'} + V_i = -V_i$$

$$V_o = V_{R_p'} = -\frac{V_i}{3}$$


$$\therefore V_o = -\frac{1}{3} V_i$$


$$-2V_i - V_o - V_i = 0$$

$$V_o = -3V_i$$

$$V_i = -\frac{V_o}{3}$$

$$V_{dc} = 0.636 V_m \approx 36.04 V$$

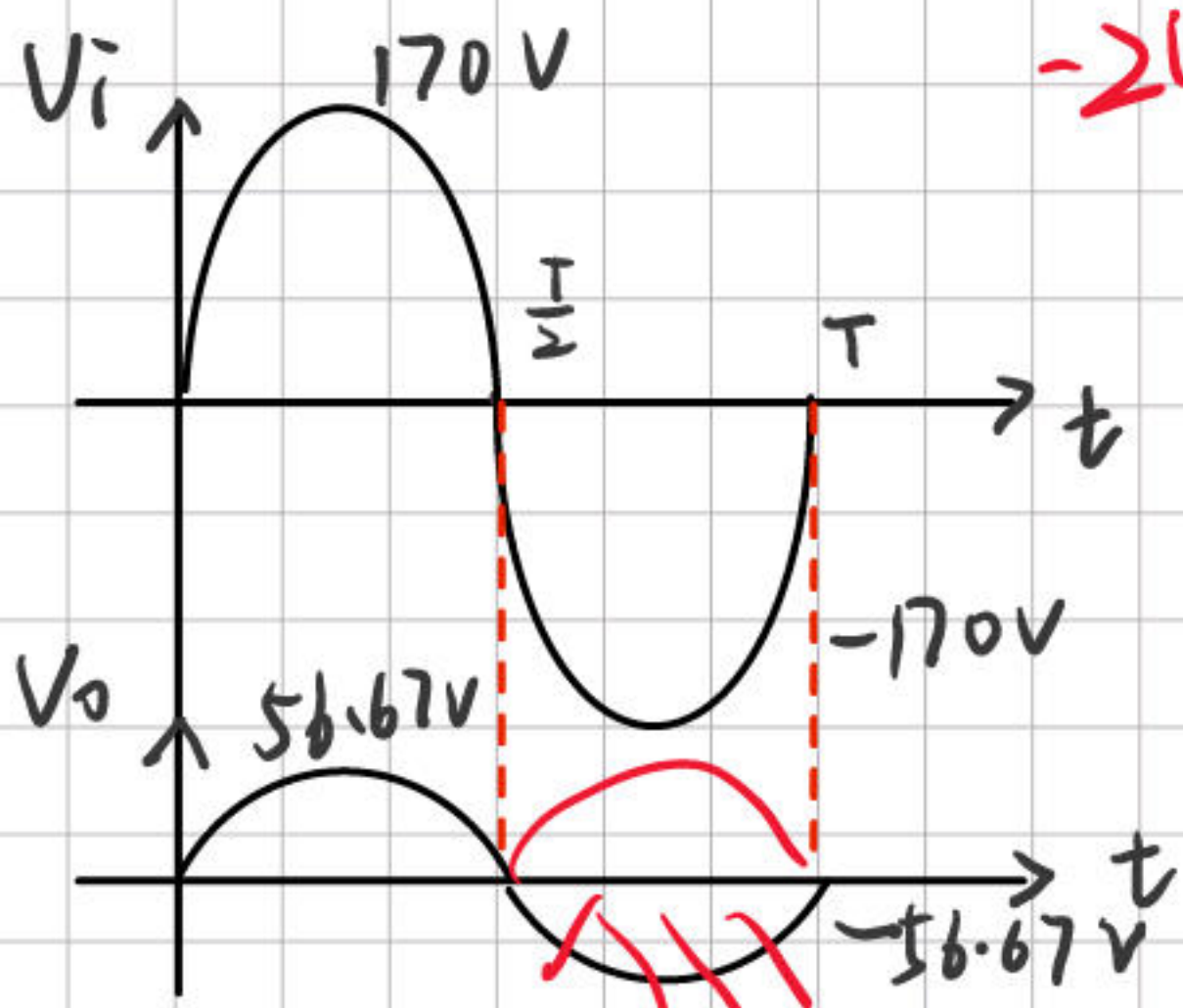

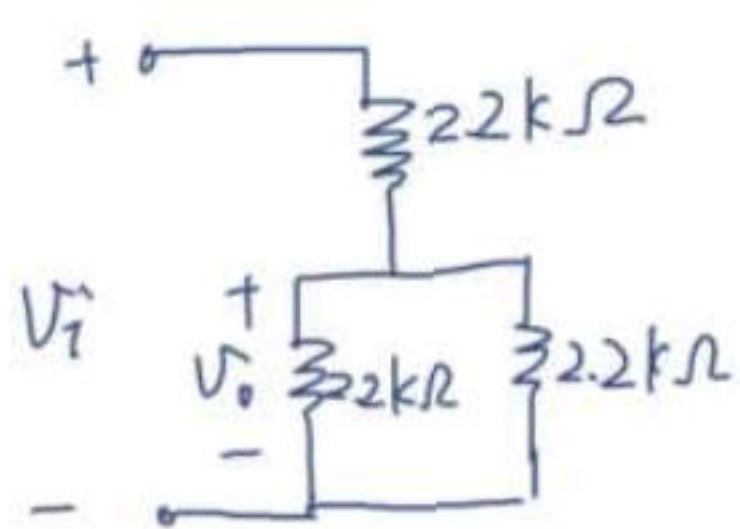


$$V_{dc} = 0.636 \times 16.67$$

$$= 10.604 \text{ V}$$

$$V_o = \frac{1}{3} V_i$$

$$V_{om} = \frac{170}{3} \approx 56.67 \text{ V}$$

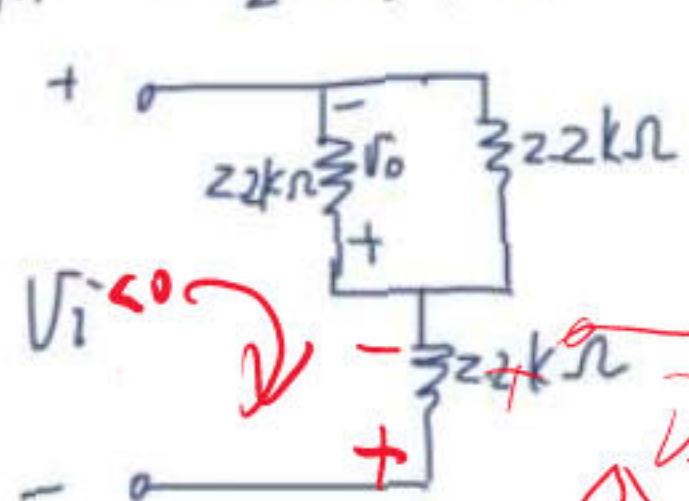for $t = \frac{T}{2} \sim T$, D_1 is on, D_2 is off



$$V_o = -\frac{V_i}{3}$$

$$-V_o + V_R - V_i = 0$$


$$V_R = V_i + V_o$$

$$V_i + 2V_o + V_o = -V_o$$


$$V_i + 2V_o + V_o = -V_o$$

For the emitter bias circuit below ,
determine:

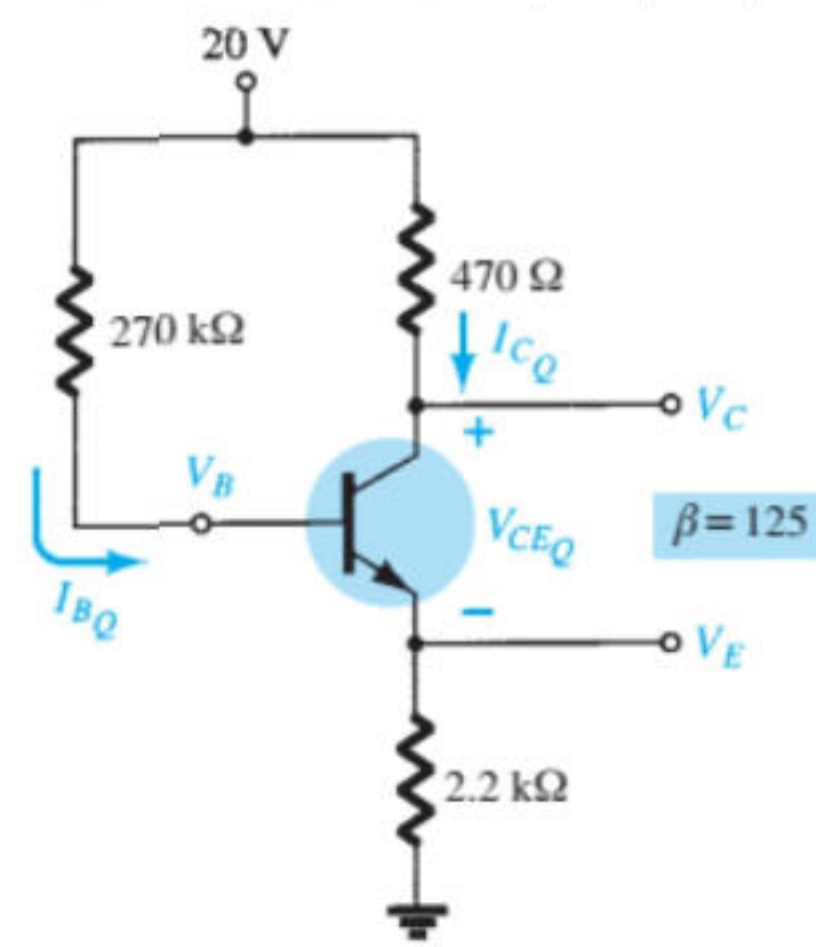- I_{BQ} .
- I_{CQ} .
- V_{CEQ} .
- V_C .
- V_B .
- V_E .



Solution:

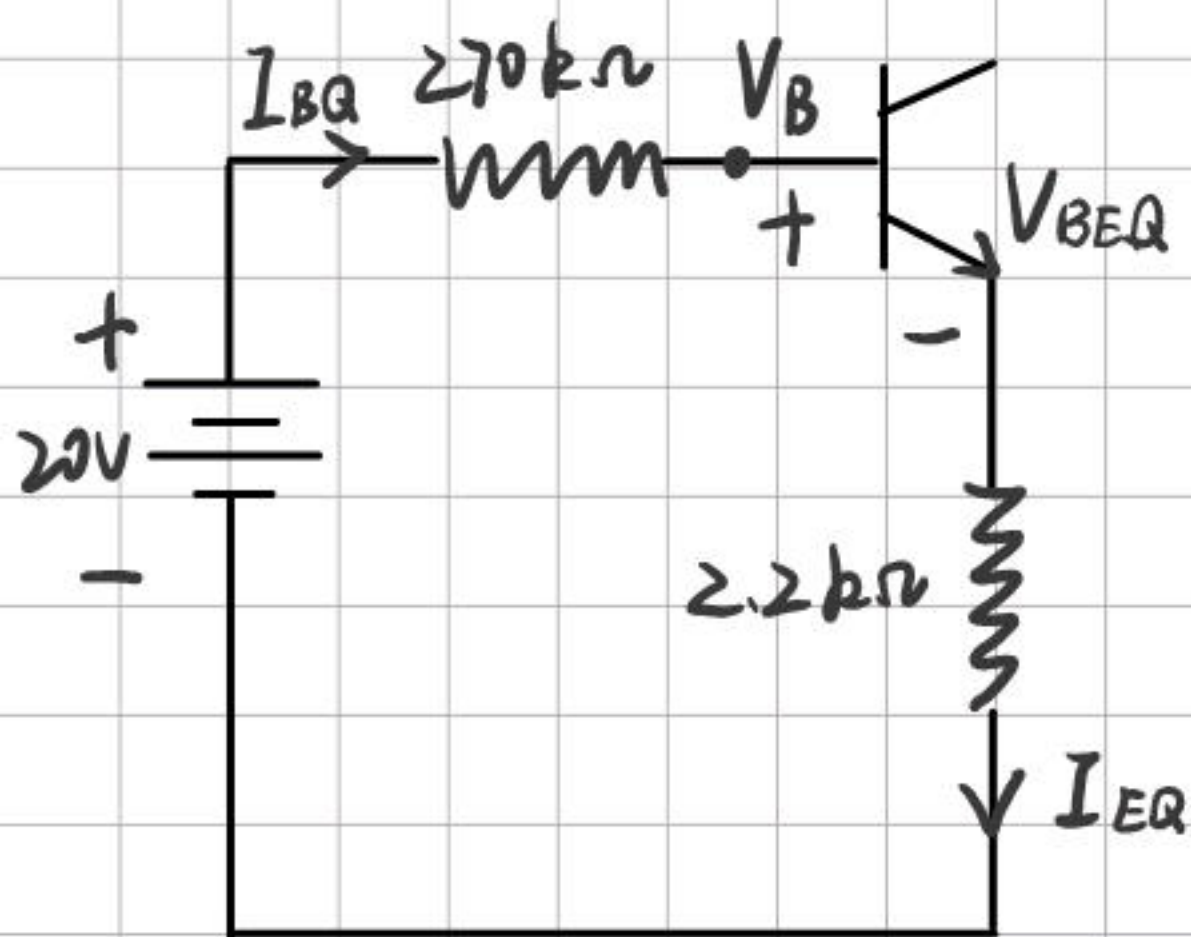

$$\begin{aligned} a: I_{BQ} &= \frac{V_{CC} - V_{BEQ}}{R_B + (1 + \beta) R_E} \\ &= \frac{20 - 0.7}{270k + 126 \times 2.2k} \\ &\approx 35.27 \mu A \end{aligned}$$

$$\begin{aligned} b: I_{CQ} &= \beta I_{BQ} \\ &= 4.41 \text{ mA} \end{aligned}$$


Since $I_{CQ} \approx I_{EQ}$

$$\begin{aligned} c: V_{CEQ} &\approx V_{CC} - I_{CQ}(R_C + R_E) \\ &\approx 20 - 4.41(0.47 + 2.2) \\ &\approx 8.23 \text{ V} \end{aligned}$$

$$\begin{aligned} d: V_C &= V_{CEQ} + V_E \\ &= 8.23 + 9.77 \\ &= 18 \text{ V} \end{aligned}$$

$$\begin{aligned} f: V_E &= I_{EQ} \cdot R_E \\ &= (1 + \beta) I_{BQ} \cdot R_E \\ &= 126 \times 35.27 \mu A \cdot 2.2k\Omega \\ &\approx 4.44 \text{ mA} \cdot 2.2k\Omega \\ &\approx 9.77 \text{ V} \end{aligned}$$

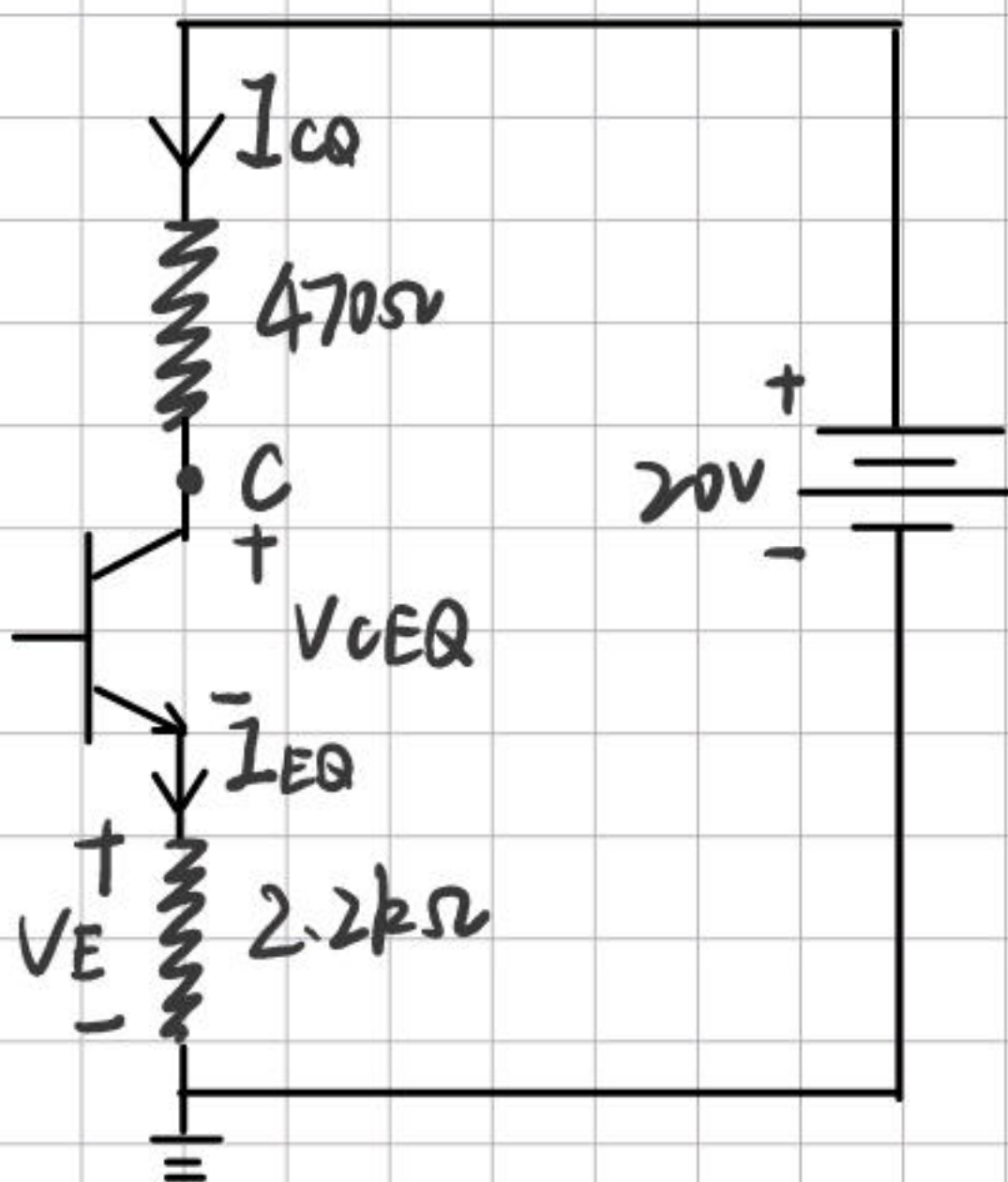
$$\begin{aligned} e: V_B &= V_{BEQ} + I_{EQ} \cdot R_E \\ &= 0.7 + 9.77 \\ &= 10.47 \text{ V} \end{aligned}$$



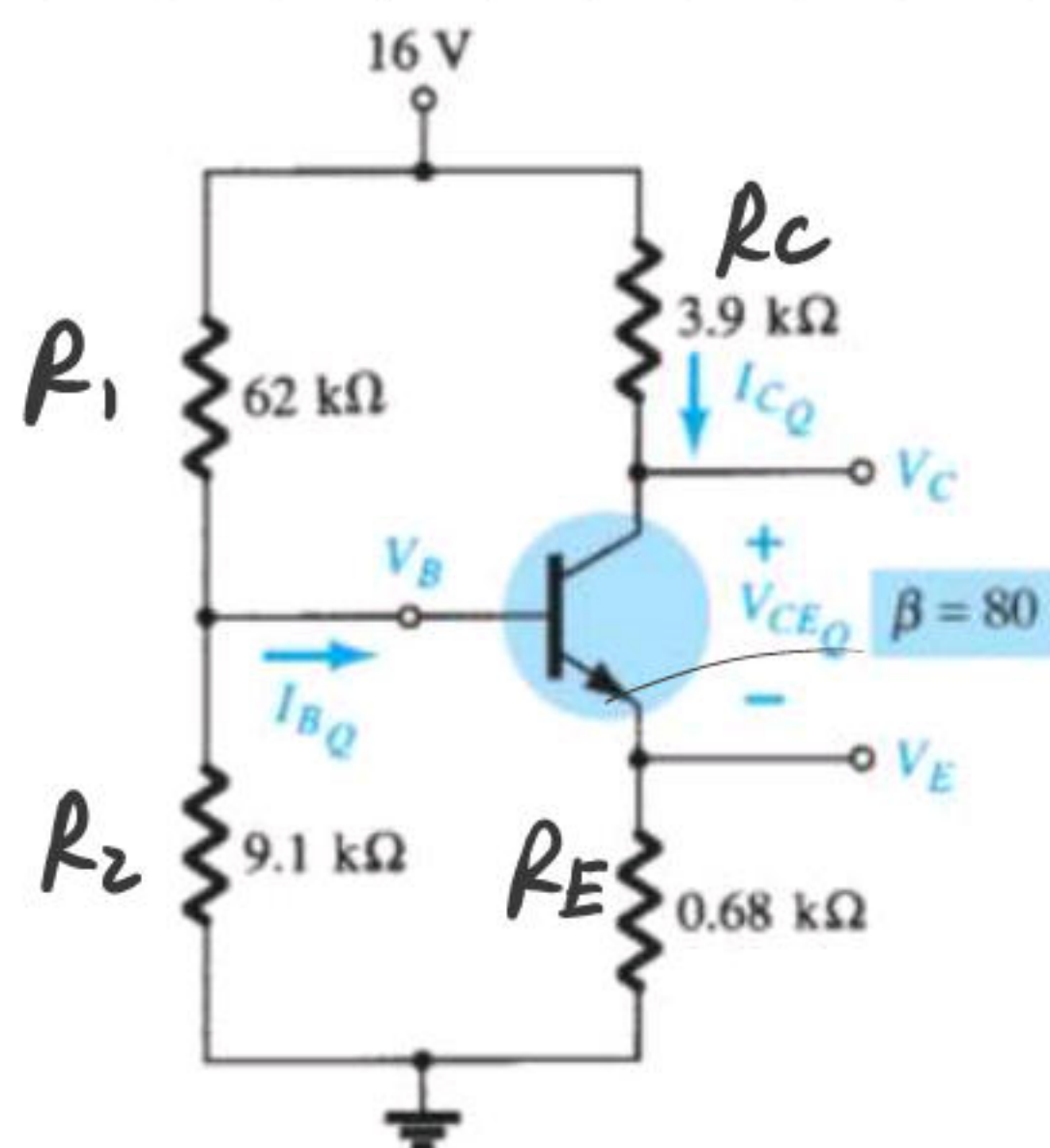2. 计算题

For the voltage-divider bias configuration, determine:

- I_{BQ} .
- I_{CQ} .
- V_{CEQ} .
- V_C .
- V_E .
- V_B .




Solution:

$$\beta R_E = 80 \times 0.68 \text{ k}\Omega = 54400 \Omega$$

$$10R_2 = 91000 \Omega$$

$$10R_2 > \beta R_E$$

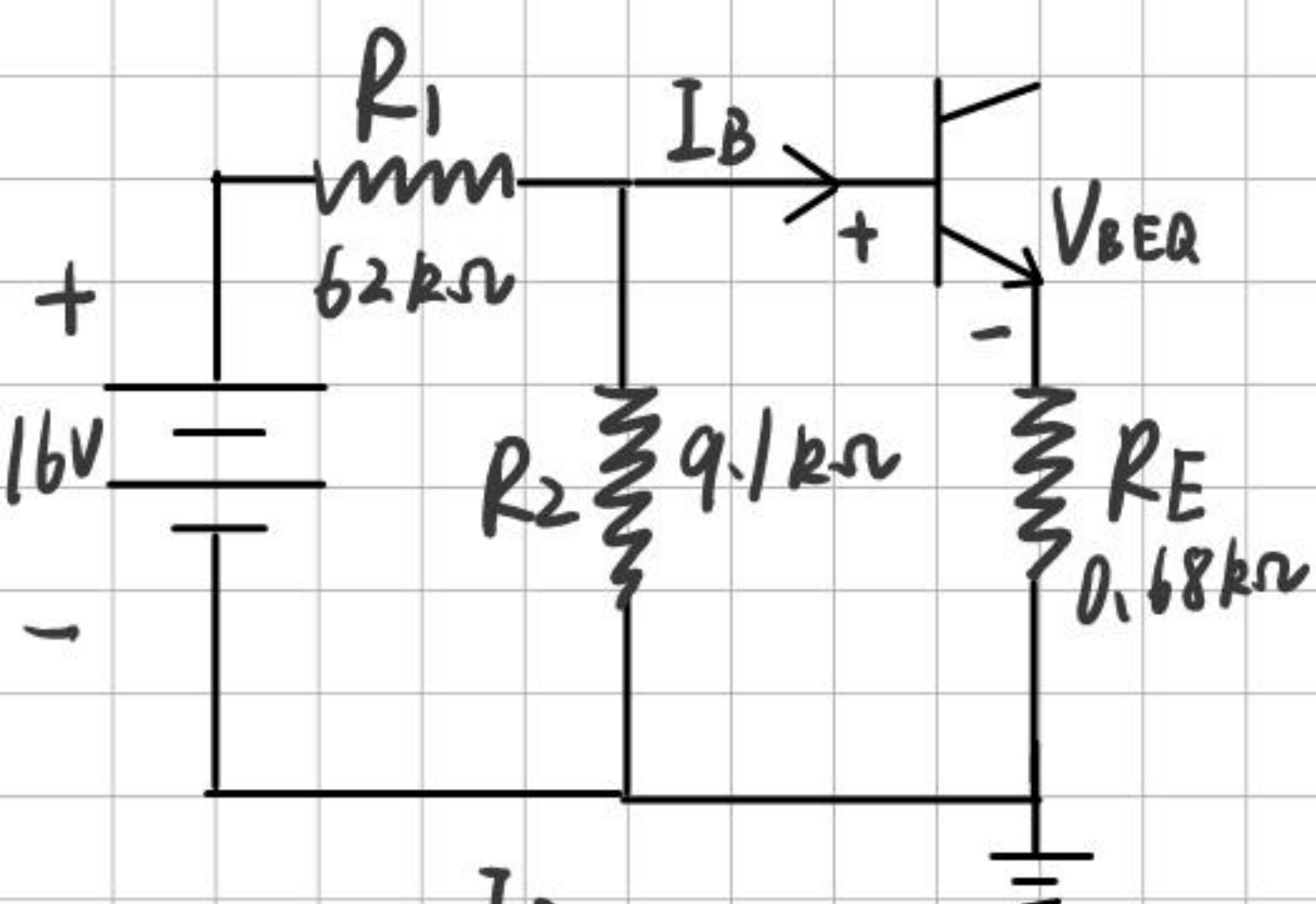$\therefore \beta R_E \approx 10R_2 \therefore$ Using exact analysis




\Rightarrow
Thevenin theorem

$$R_{Th} = R_1 \parallel R_2$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$
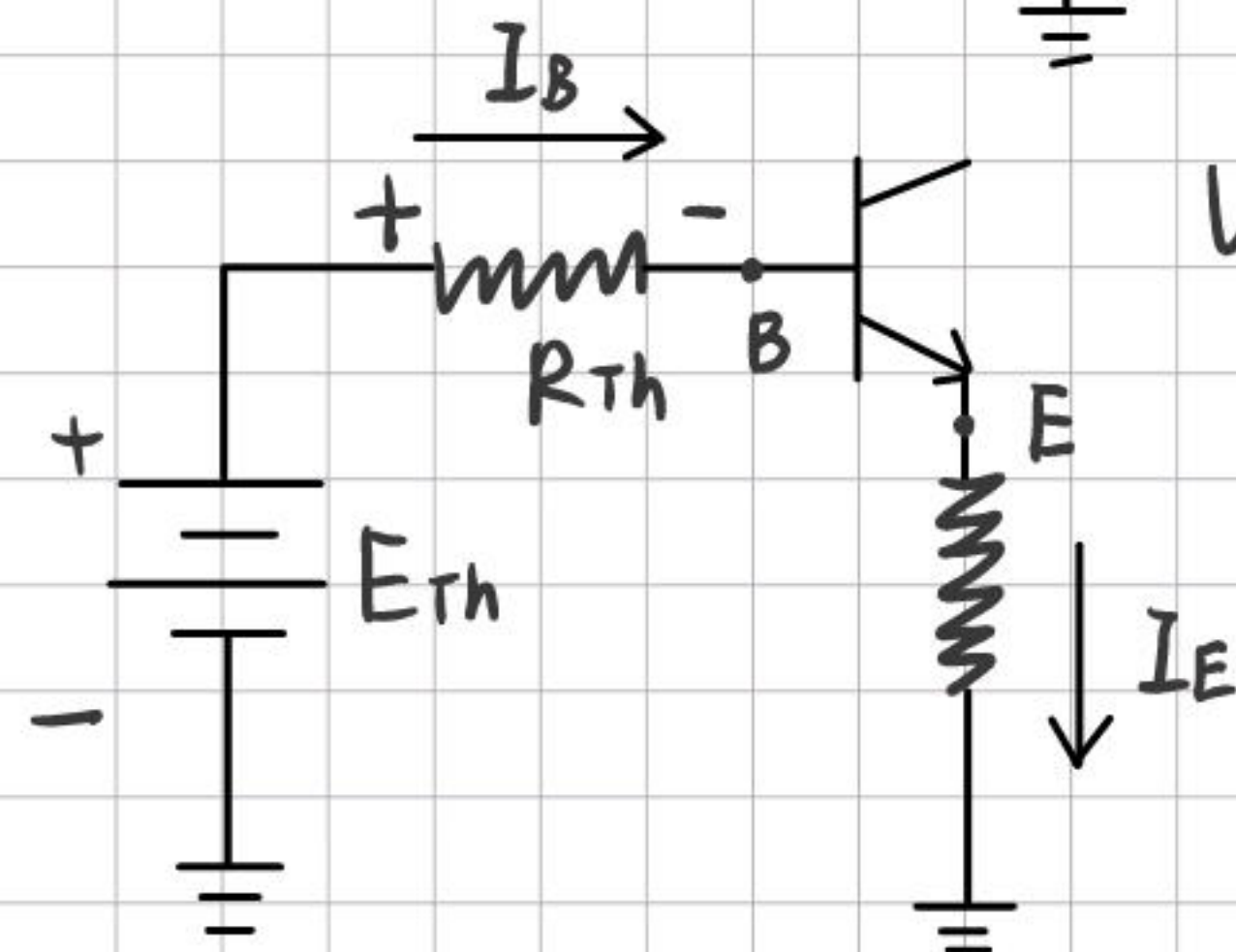
$$= \frac{62 \text{ k}\Omega \cdot 9.1 \text{ k}\Omega}{62 \text{ k}\Omega + 9.1 \text{ k}\Omega} \approx 7935.30 \Omega$$



$$V_E = I_{EQ} \cdot R_E$$

$$= (\beta + 1) I_{BQ} \cdot R_E$$

$$= 81 \times 21.42 \mu\text{A} \cdot 0.68 \text{ k}\Omega$$

$$\approx 1.18 \text{ V}$$

$$E_{Th} = \frac{R_2 V_{CC}}{R_1 + R_2}$$

$$= \frac{9.1 \text{ k}\Omega \times 16 \text{ V}}{62 \text{ k}\Omega + 9.1 \text{ k}\Omega} \approx 2.05 \text{ V}$$

$$a: I_{BQ} = \frac{E_{Th} - V_{BEQ}}{R_{Th} + (\beta + 1) R_E} = \frac{2.05 - 0.7}{7935.30 + 81 \times 680} \approx 21.42 \mu\text{A}$$

$$b: I_{CQ} = \beta I_{BQ} \approx 1.71 \text{ mA}$$

$$d: V_C = V_{CEQ} + V_E$$

$$= 8.17 + 1.18 = 9.35 \text{ V}$$

$$e: V_E = 1.18 \text{ V}$$

$$f: V_B = V_{BEQ} + V_E = 0.7 + 1.18 = 1.88 \text{ V}$$

$$c: V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E) = 16 - 1.71 (3.9 + 0.68)$$

$$\approx 8.17 \text{ V}$$

P294 29


$$\beta R_E = 100 \times 1.2 \text{ k} = 120 \text{ k}$$

$$10 R_2 = 47 \text{ k}\Omega$$

$$\Rightarrow \beta R_E > 10 R_2$$

Using approximate analysis:

Sketch the DC biasing circuit:

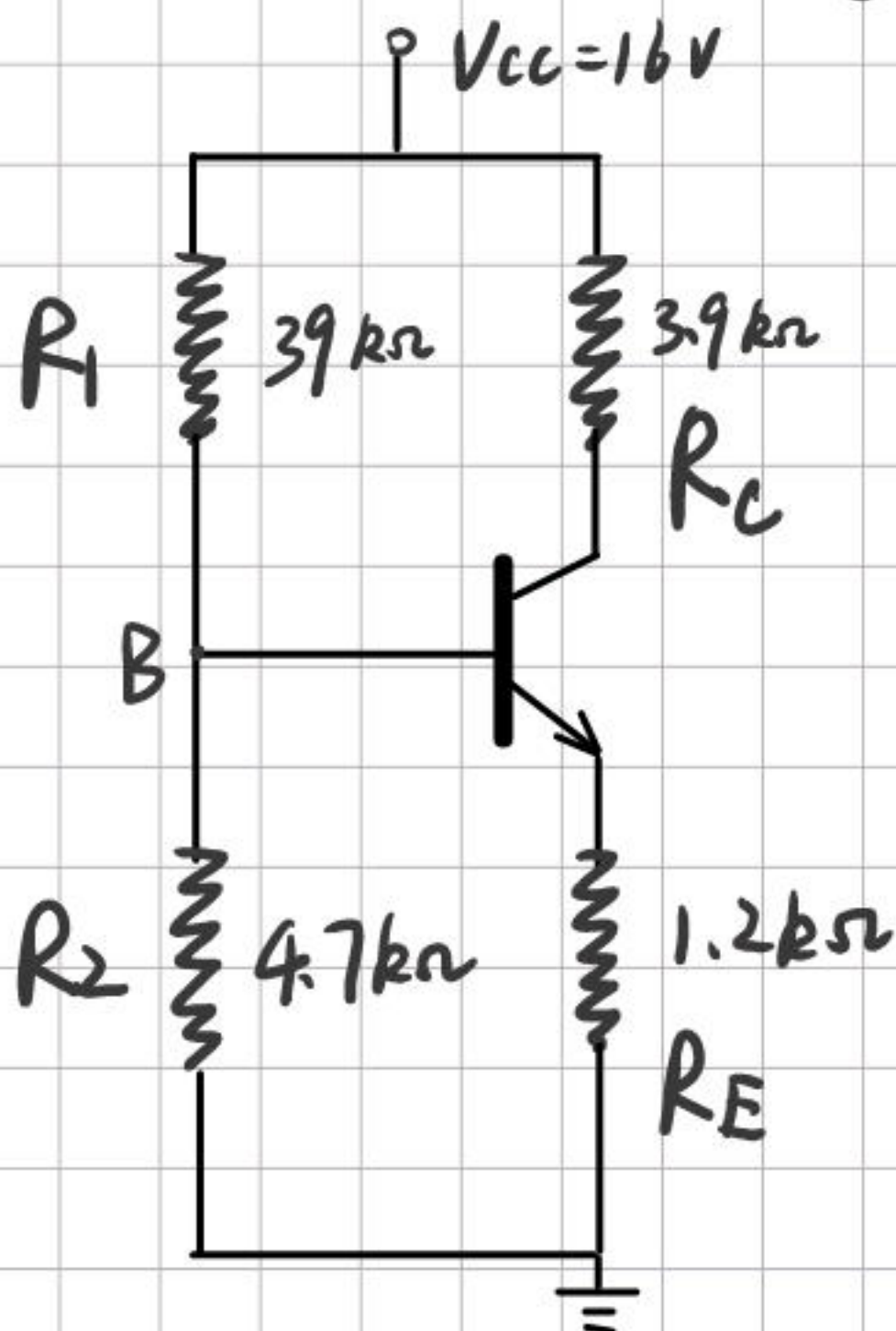

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{39 \text{ k}}{47 \text{ k} + 39 \text{ k}} \times 16 \approx 14.28 \text{ V}$$


$$V_B = V_{BEQ} + V_E = 0.7 + I_{EQ} R_E$$

$$I_{EQ} \cdot 1.2 \text{ k} = 13.58$$

$$I_{EQ} \approx 11.31 \text{ mA}$$

$$a. r_e = \frac{26 \text{ mV}}{I_{EQ}} = \frac{26 \text{ mV}}{11.31 \text{ mA}} \approx 2.30 \Omega$$

Sketch the AC biasing circuit:

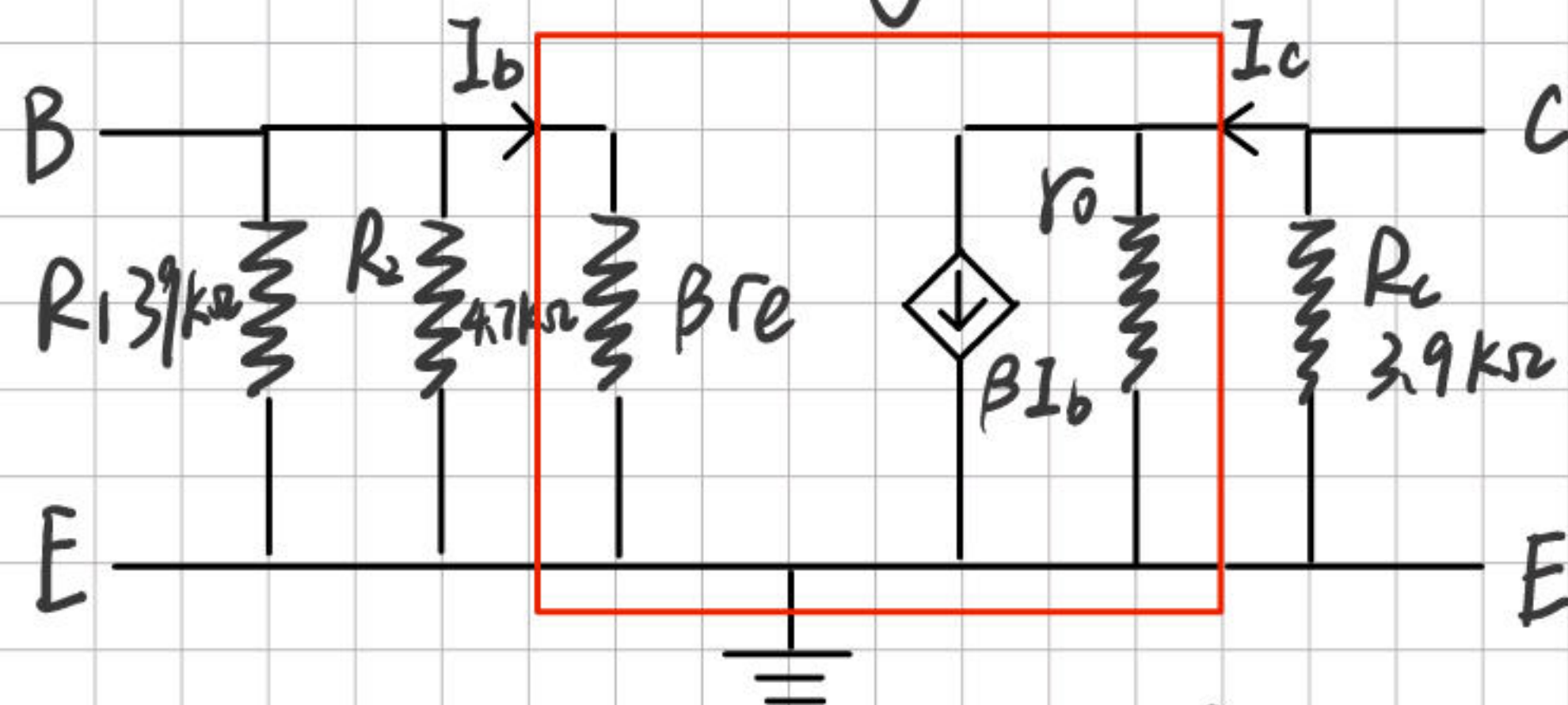

$$b. Z_i = R_1 \parallel R_2 \parallel \beta r_e$$

$$= \frac{1}{\frac{1}{39 \text{ k}} + \frac{1}{47 \text{ k}} + \frac{1}{100 \times 2.30}}$$

$$\approx 218.04 \Omega$$

$$\approx 0.22 \text{ k}\Omega$$

$$r_o = 50 \text{ k}\Omega > 10 R_c$$

$$Z_o = r_o \parallel R_c$$

$$\approx R_c$$

$$\approx 3.9 \text{ k}\Omega$$

$$c. A_v = - \frac{r_o \parallel R_c}{r_e} \approx - \frac{R_c}{r_e} = -1695.65$$


d. if $r_o = 25 \text{ k}\Omega < 10 R_c$

$$Z_i = 0.22 \text{ k}\Omega \quad Z_o = r_o \parallel R_c = \frac{25 \text{ k} \times 3.9 \text{ k}}{25 \text{ k} + 3.9 \text{ k}} \approx 3.37 \text{ k}\Omega$$

$$A_v = - \frac{Z_o}{r_e} = - \frac{3.37 \text{ k}}{2.30} \approx -1465.22$$

P295 34

a. sketch the DC biasing circuit:

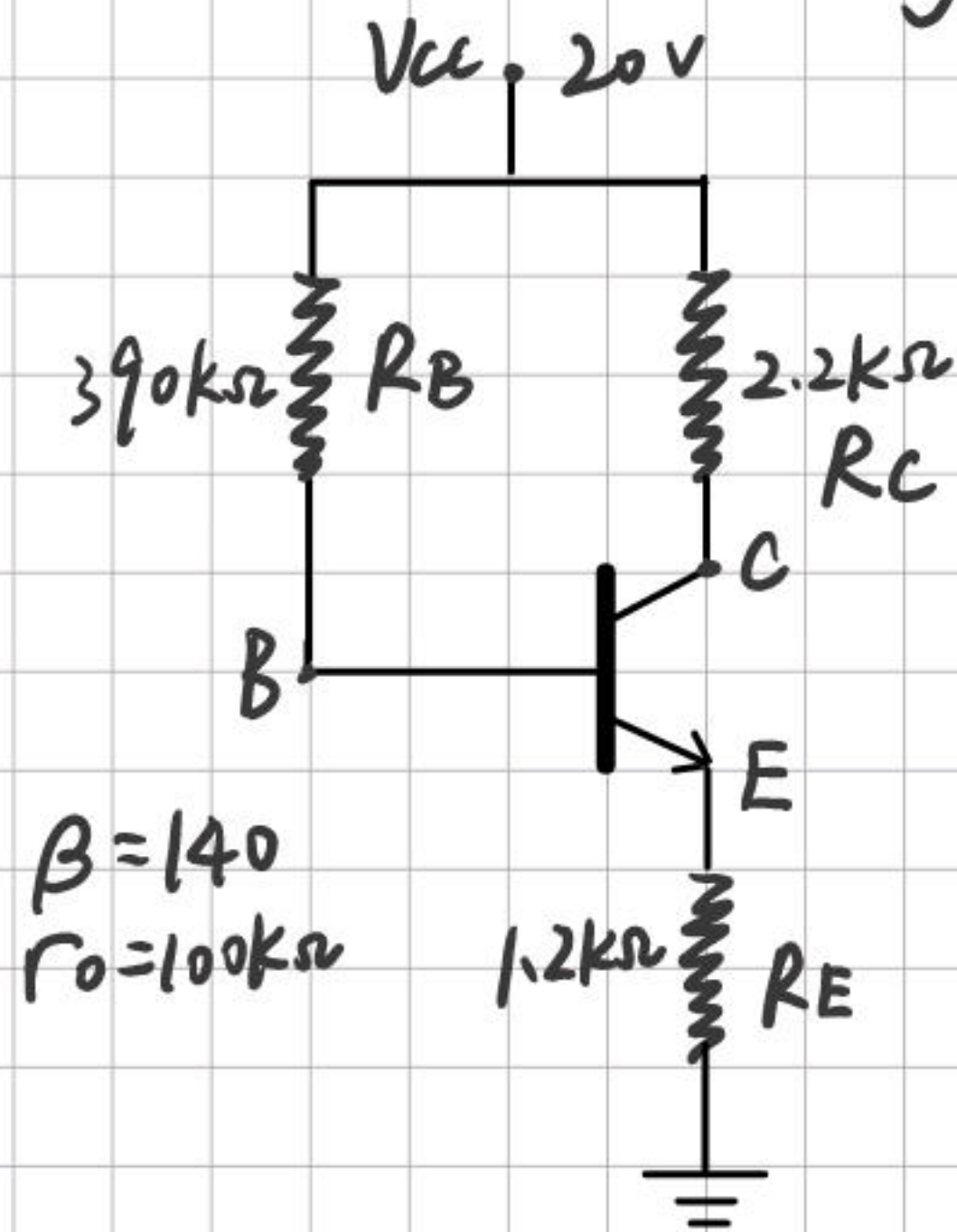

$$-V_{CC} + V_{BEQ} + I_{BQ} \cdot R_B + I_{EQ} \cdot R_E = 0$$

$$I_{BQ} = \frac{V_{CC} - V_{BEQ}}{R_B + (\beta + 1)R_E}$$

$$= \frac{20 - 0.7}{390k + 141 \times 1.2k}$$

$$\approx 34.51 \mu A$$


$$I_{EQ} = (\beta + 1)I_{BQ}$$

$$= 141 \times 34.51 \mu A$$

$$\approx 4.87 mA$$

$$r_e = \frac{26 mV}{I_{EQ}} = \frac{26 mV}{4.87 mA} \approx 5.34 \Omega$$

b. sketch the AC biasing circuit:

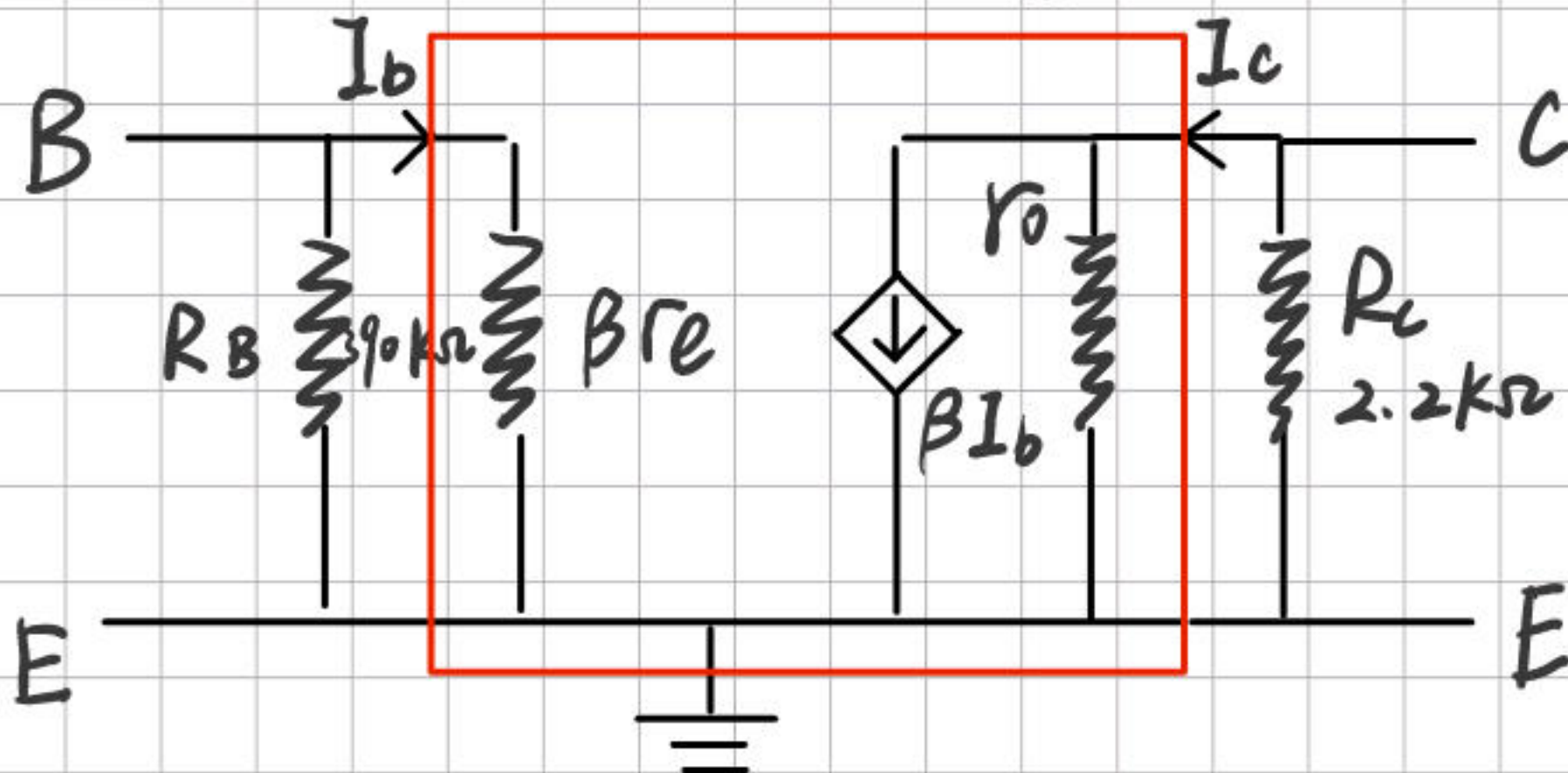

$$R_B = 390 k\Omega > 10 \beta r_e = 7476 \Omega$$

$$Z_i = R_B \parallel \beta r_e$$

$$\approx \beta r_e$$

$$\approx 747.6 \Omega \approx 0.75 k\Omega$$

$$r_0 > 10 R_C$$

$$Z_o = r_0 \parallel R_C$$

$$\approx R_C$$

$$\approx 2.2 k\Omega$$

c.

$$A_v = -\frac{Z_o}{r_e} \approx -\frac{2.2k}{5.34} \approx 411.99$$

d. if $r_0 = 20 k\Omega$

$$Z_i = 0.75 k\Omega \quad r_0 < 10 R_C$$

$$Z_o = r_0 \parallel R_C = \frac{20k \times 2.2k}{20k + 2.2k} \approx 1981.98 \Omega \approx 1.98 k\Omega$$

$$A_v = -\frac{Z_o}{r_e} = \frac{1.98k}{5.34} \approx 370.79$$


For the network below:

a. Determine I_{BQ} , I_{CQ} , I_{EQ} , V_{CEQ} , V_C , V_E .

b. Determine r_e

c. Sketch the AC equivalent circuit.

d. Determine Z_i , Z_o and A_v .

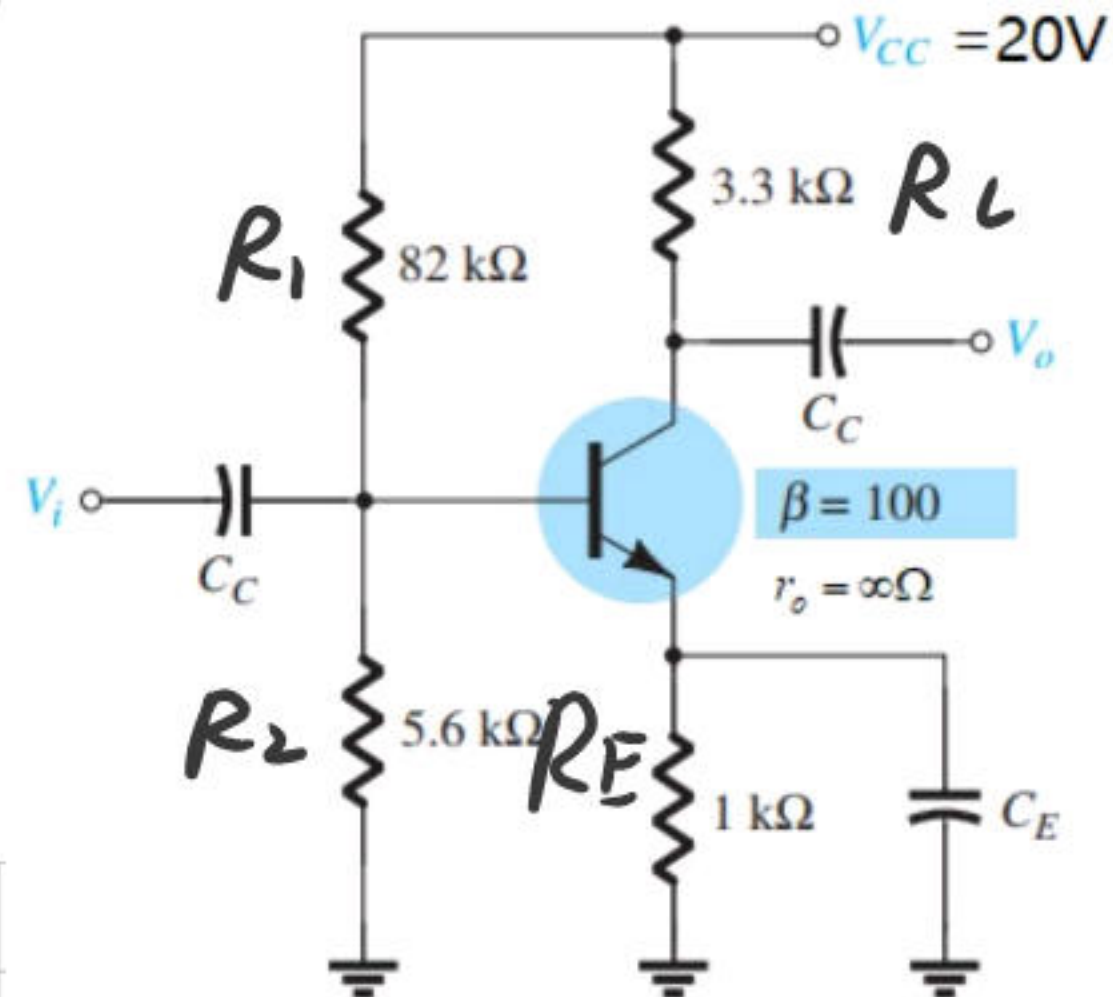

Solution:

a. $\beta r_e = 100 \times 1 \text{ k} = 100 \text{ k} \Omega$

$10 R_2 = 10 \times 5.6 \text{ k} = 56 \text{ k} \Omega$

$\beta r_e > 10 R_2$

\therefore Using approximate analysis

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{5.6 \text{ k}}{82 \text{ k} + 5.6 \text{ k}} \times 20 \approx 1.28 \text{ V}$$

$$V_E = V_B - V_{BEQ} = 1.28 - 0.7 = 0.58 \text{ V}$$

$$I_{EQ} = \frac{V_E}{R_E} = \frac{0.58}{1 \text{ k}} = 0.58 \text{ mA}$$


$$I_{BQ} = \frac{I_{EQ}}{1 + \beta} \approx 5.74 \mu\text{A}$$

$$I_{CQ} \approx I_{EQ} = 0.58 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E) = 20 - 0.58 \text{ mA} \times 4.3 \text{ k} \approx 17.51 \text{ V}$$

$$V_C = I_{CQ} \cdot R_C = 0.58 \text{ mA} \times 3.3 \text{ k} \approx 1.91 \text{ V}$$

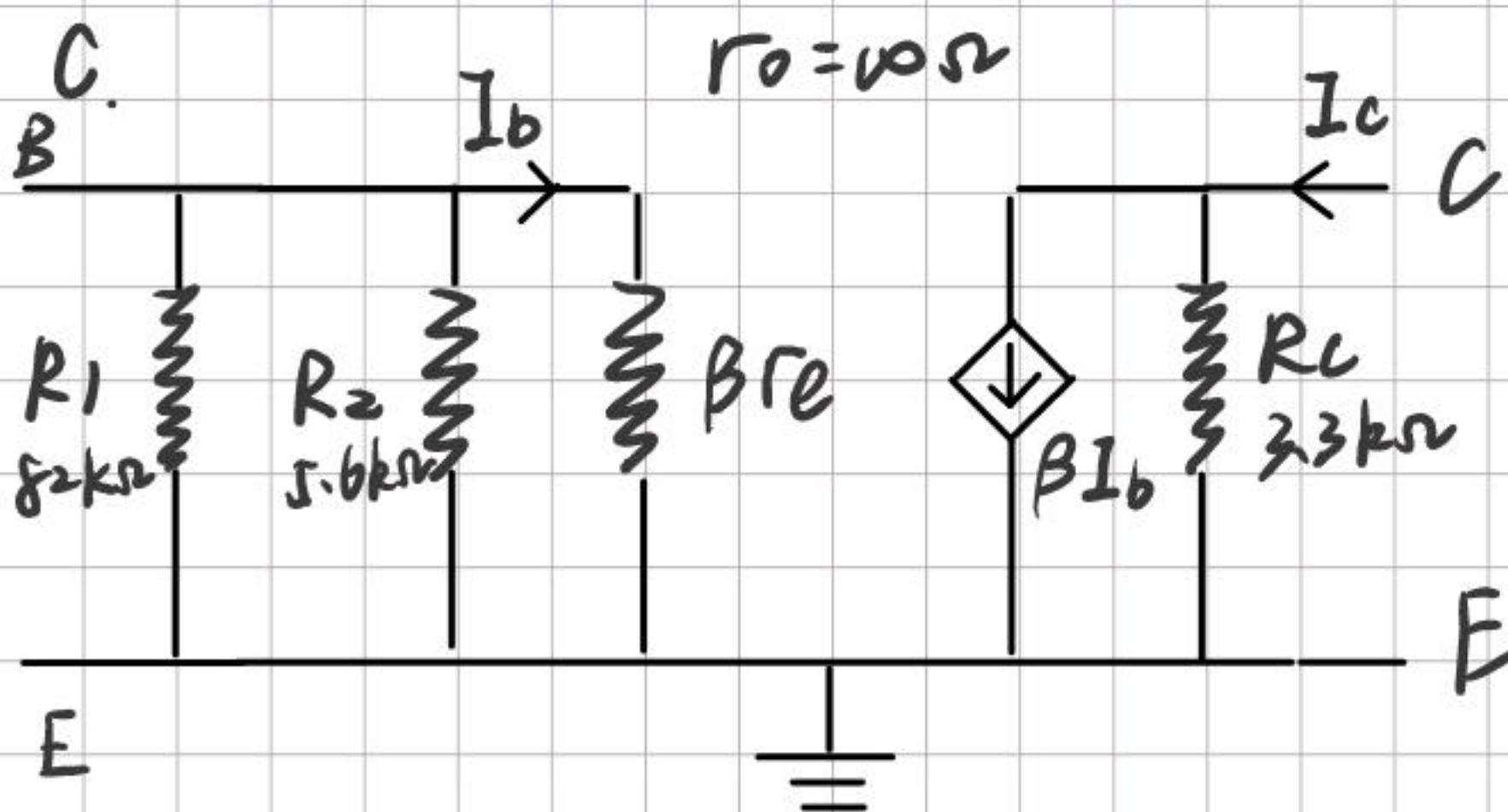b. $r_e = \frac{26 \text{ mV}}{I_{EQ}} = \frac{26 \text{ mV}}{0.58 \text{ mA}} \approx 44.83 \Omega$




d. $R_1 || R_2 = \frac{R_1 R_2}{R_1 + R_2} = \frac{82 \text{ k} \times 5.6 \text{ k}}{82 \text{ k} + 5.6 \text{ k}} \approx 5242.01 \Omega \approx 5.24 \text{ k} \Omega$

$$Z_i = R_1 || R_2 || \beta r_e = \frac{5242.01 \times 100 \times 44.83}{4483 + 5242.01} \approx 2.42 \text{ k} \Omega$$

$$Z_o = R_C = 3.3 \text{ k} \Omega$$

$$A_v = -\frac{Z_o}{r_e} = -\frac{3.3 \text{ k}}{44.83} \approx -73.61$$

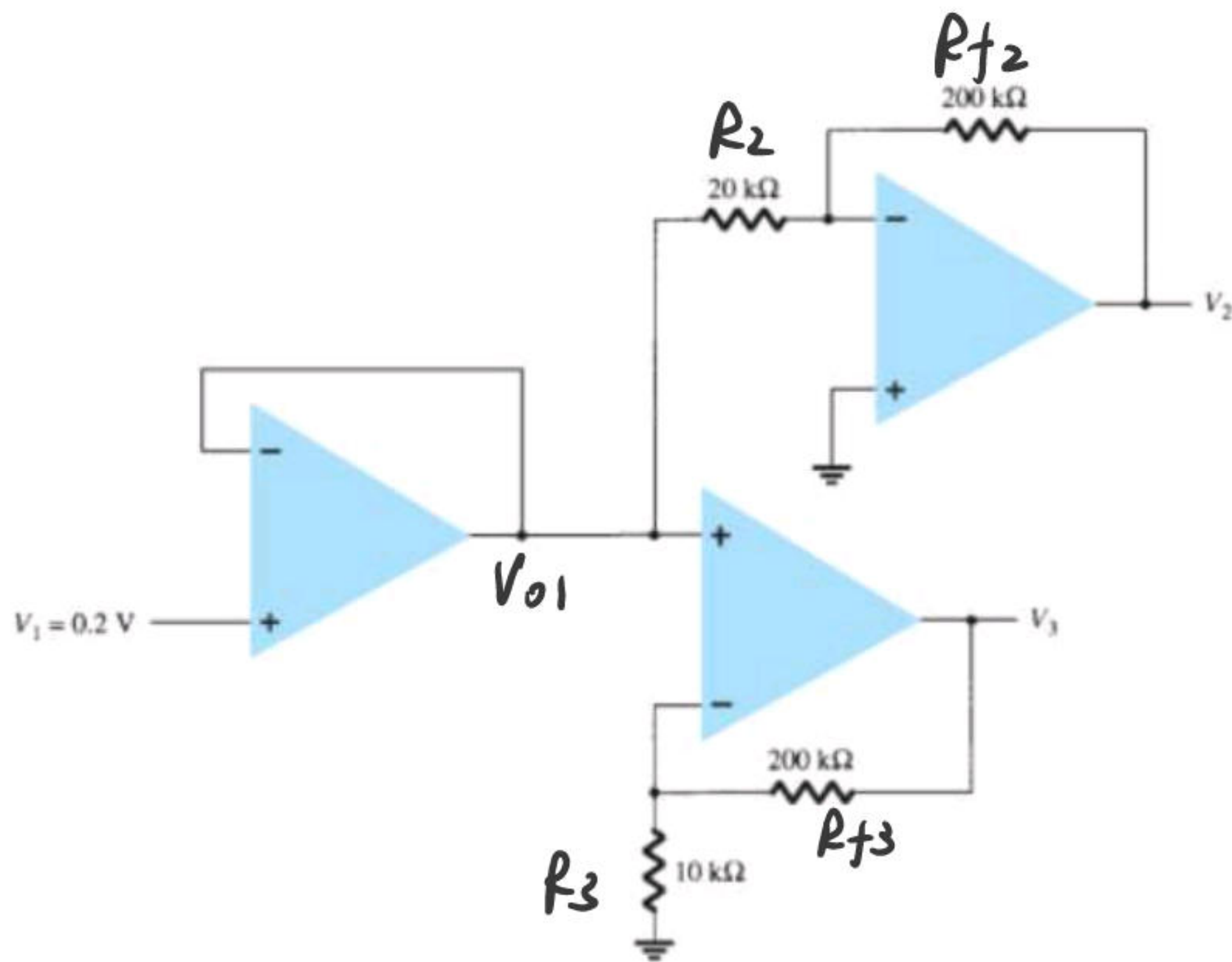Calculate the output voltages V_2 and V_3 in the circuit.



Solution: $V_{01} = V_1 = 0.2\text{ V}$

$$V_3 = \left(1 + \frac{R_{f3}}{R_3}\right) V_{01}$$

$$= \left(1 + \frac{200\text{ k}\Omega}{10\text{ k}\Omega}\right) \times 0.2$$

$$= 21 \times 0.2$$


$$\approx 4.2\text{ V}$$

$$V_2 = -\frac{R_{f2}}{R_2} V_{01}$$

$$= -\frac{200\text{ k}\Omega}{20\text{ k}\Omega} \times 0.2$$

$$= -2\text{ V}$$

Calculate V_o in the circuit below .

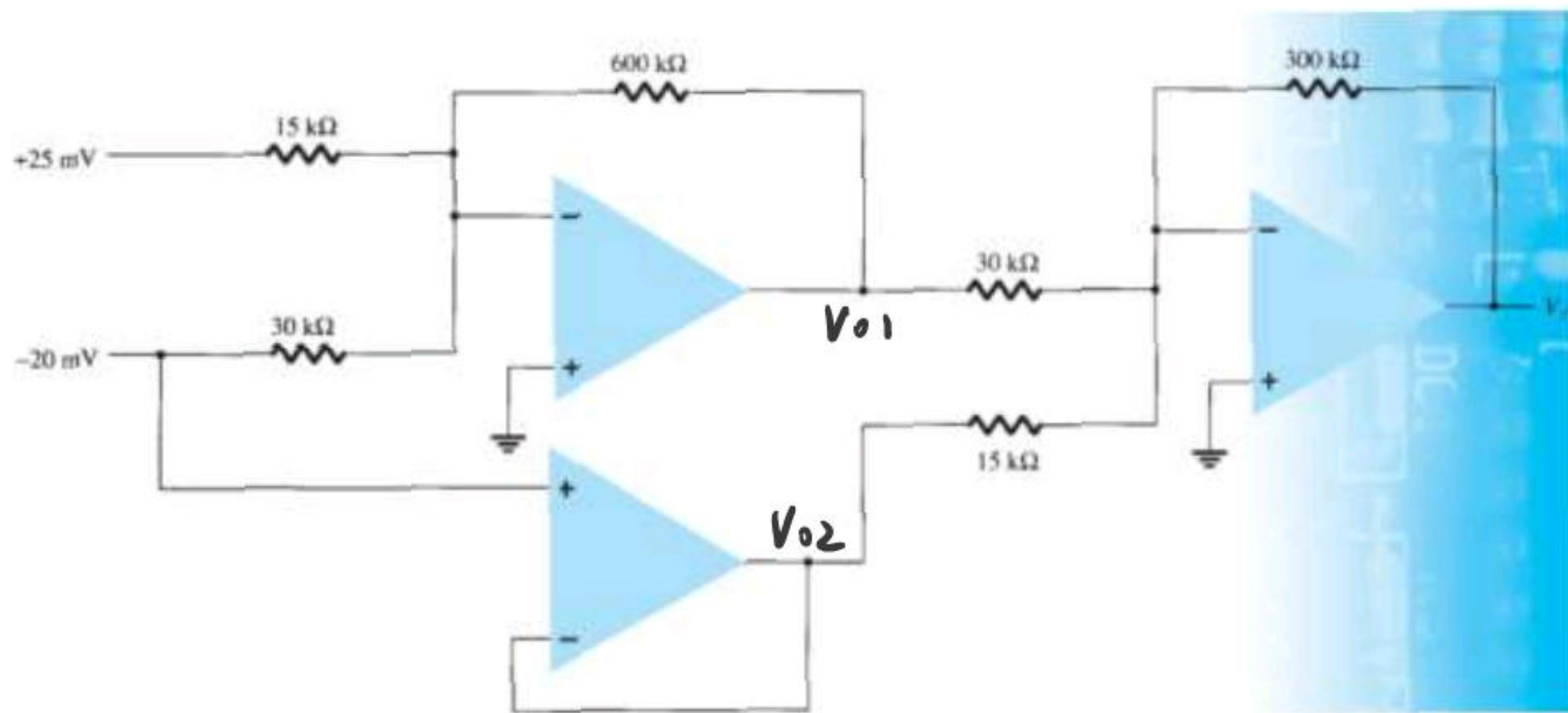

Solution:

$$V_{01} = - \left(\frac{600k}{15k} \times 25mV + \frac{600k}{30k} \times -20mV \right) \quad V_{02} = -20mV$$

$$= - (1000mV - 40mV)$$


$$= -0.6V$$

$$\Rightarrow V_o = - \left(\frac{300k}{30k} \times -600mV + \frac{300k}{15k} \times -20mV \right)$$

$$= - (-600mV - 40mV)$$

$$= 6.4V$$

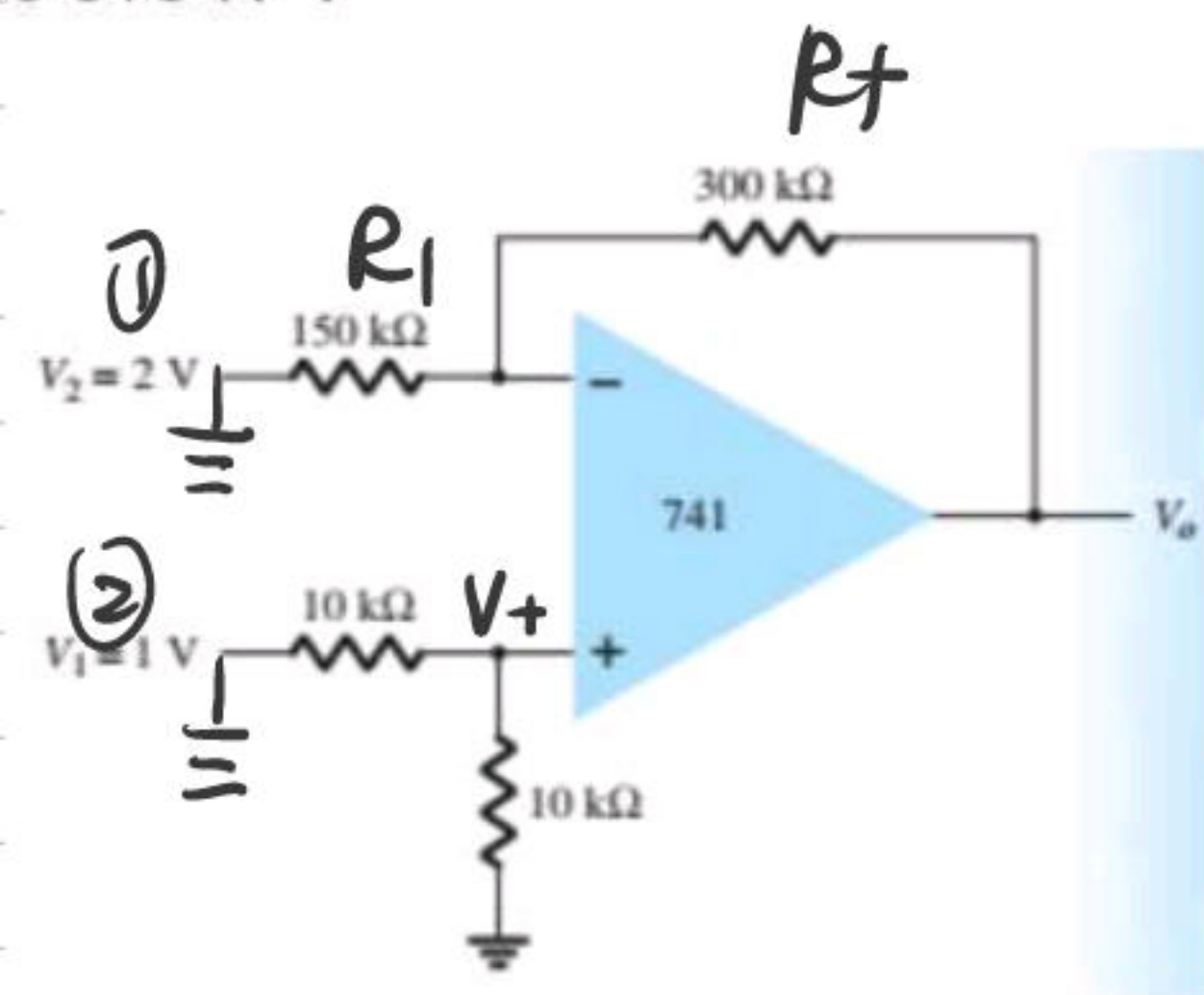Determine the output voltage for the circuit below .



solution: use superposition

$$\begin{aligned} \textcircled{1} \quad V_+ &= \frac{10k}{10k+10k} \times V_1 & V_o' &= \left(1 + \frac{R_f}{R_1}\right) V_+ \\ &= 0.5V & &= \left(1 + \frac{300k}{150k}\right) \times 0.5 \\ & & &= 1.5V \end{aligned}$$

$$\begin{aligned} \textcircled{2} \quad V_o'' &= -\frac{R_f}{R_1} V_2 = -\frac{300k}{150k} \times 2 = -4V \\ \therefore V_o &= V_o' + V_o'' = -2.5V \end{aligned}$$

