

Check your calculations and results by using LTSpice to simulate the circuits

1.

- a. Using the characteristics shown below, determine I_D and V_D for the circuit shown below.
- b. Repeat part (a) with $R = 0.47 \text{ k}\Omega$.
- c. Repeat part (a) with $R = 0.68 \text{ k}\Omega$.
- d. Is the level of V_D relatively close to 0.7 V in each case?
How do the resulting levels of I_D compare? Comment accordingly.

Answers

$$(a) \quad I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.2 \text{ k}\Omega} = 30 \text{ mA}$$

The load line extends from $I_D = 30 \text{ mA}$ to $V_D = 6 \text{ V}$.

$$V_{D_Q} \cong 0.95 \text{ V}, \quad I_{D_Q} \cong 25.3 \text{ mA}$$

$$(b) \quad I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.47 \text{ k}\Omega} = 12.77 \text{ mA}$$

The load line extends from $I_D = 12.77 \text{ mA}$ to $V_D = 6 \text{ V}$.


$$V_{D_Q} \cong 0.8 \text{ V}, \quad I_{D_Q} \cong 11 \text{ mA}$$


$$(c) \quad I_D = \frac{E}{R} = \frac{6 \text{ V}}{0.68 \text{ k}\Omega} = 8.82 \text{ mA}$$

The load line extends from $I_D = 8.82 \text{ mA}$ to $V_D = 6 \text{ V}$.

$$V_{D_Q} \cong 0.78 \text{ V}, \quad I_{D_Q} \cong \boxed{7.8 \text{ mA}}$$

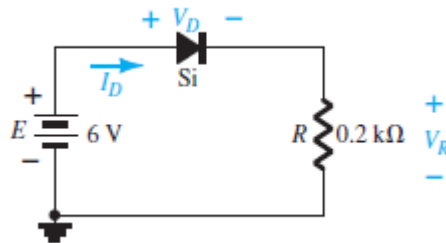The resulting values of V_{D_Q} are quite close, while I_{D_Q} extends from 7.8 mA to 25.3 mA .



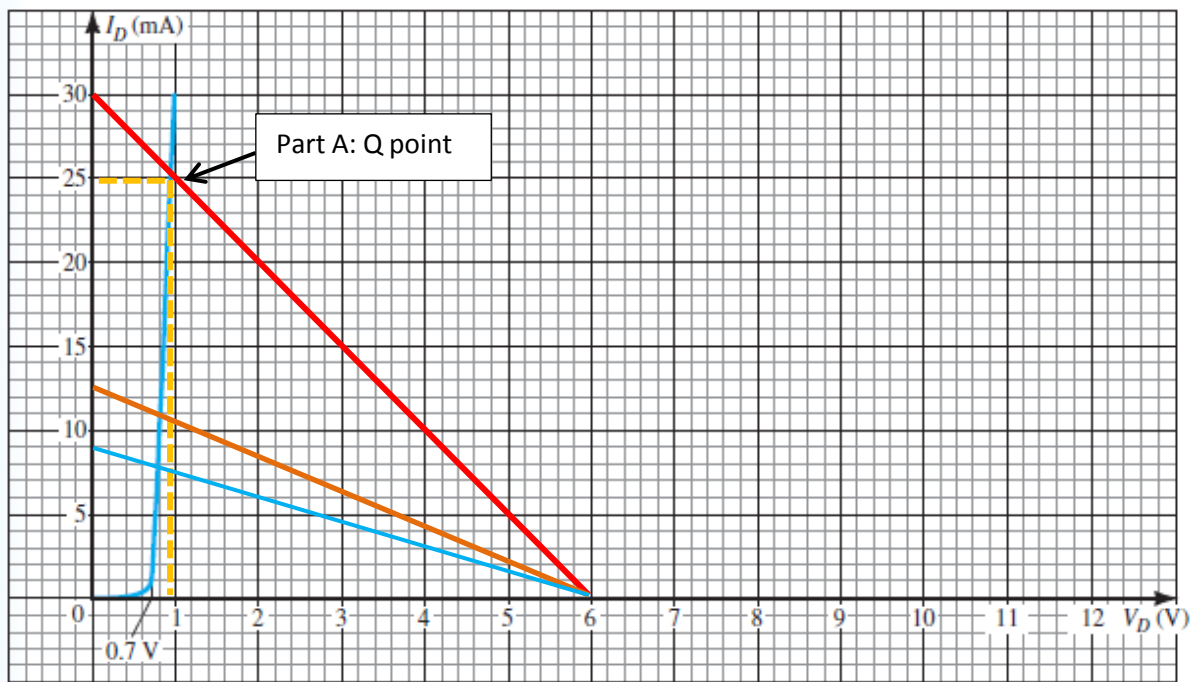

2.

- Using the approximate characteristics for the Si diode, determine V_D , I_D , and V_R for the circuit shown below.
- Perform the same analysis as part (a) using the ideal model for the diode.
- Do the results obtained in parts (a) and (b) suggest that the ideal model can provide a good approximation for the actual response under some conditions?

Answer


$$(a) \quad I_D = I_R = \frac{E - V_D}{R} = \frac{30 \text{ V} - 0.7 \text{ V}}{1.5 \text{ k}\Omega} = 19.53 \text{ mA}$$

$$V_D = 0.7 \text{ V}, V_R = E - V_D = 30 \text{ V} - 0.7 \text{ V} = 29.3 \text{ V}$$

$$(b) \quad I_D = \frac{E - V_D}{R} = \frac{30 \text{ V} - 0 \text{ V}}{1.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$V_D = 0 \text{ V}, V_R = 30 \text{ V}$$

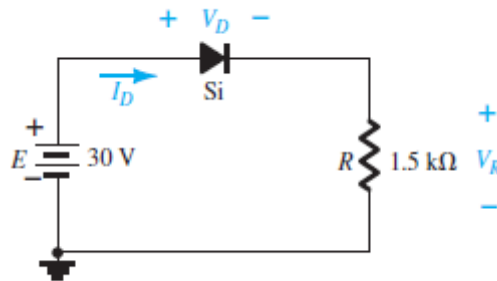Yes, since $E \gg V_T$ the levels of I_D and V_R are quite close.



3. Determine the current I for each of the configurations shown below, using the approximate equivalent model for the diode.

Answer:

(a) $I = 0 \text{ mA}$; diode reverse-biased.

(b) $V_{20\Omega} = 20 \text{ V} - 0.7 \text{ V} = 19.3 \text{ V}$ (Kirchhoff's voltage law)


$$I(20 \Omega) = \frac{19.3 \text{ V}}{20 \Omega} = 0.965 \text{ A}$$

$$V(10 \Omega) = 20 \text{ V} - 0.7 \text{ V} = 19.3 \text{ V}$$


$$I(10 \Omega) = \frac{19.3 \text{ V}}{10 \Omega} = 1.93 \text{ A}$$

$$I = I(10 \Omega) + I(20 \Omega) = 2.895 \text{ A}$$

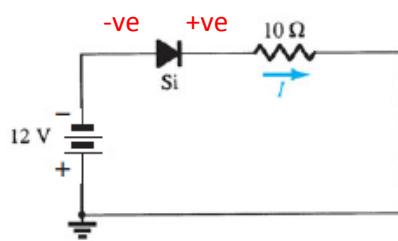
(c) $I = \frac{10 \text{ V}}{10 \Omega} = 1 \text{ A}$; center branch open



(a)

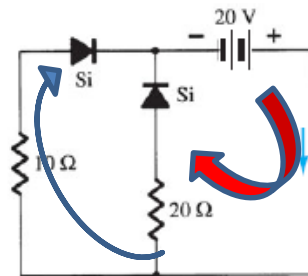

(b)

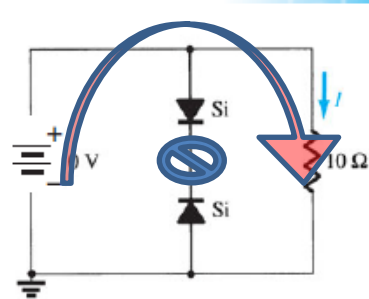

(c)

4. Determine the level of V_o for each network shown below


Answer:

For circuit A, use a voltage divider network calculation


For circuit B, both supplies are 10 volts so the output is 10 V, this is because the diode is not biased

$$(a) V_o = \frac{10 \text{ k}\Omega(12 \text{ V} - 0.7 \text{ V} - 0.3 \text{ V})}{2 \text{ k}\Omega + 10 \text{ k}\Omega} = 9.17 \text{ V}$$

$$(b) V_o = 10 \text{ V}$$

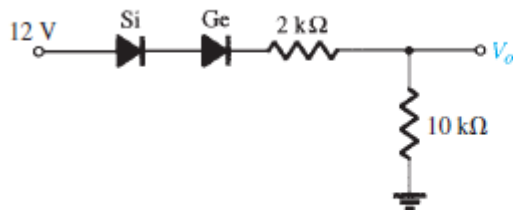

(a)

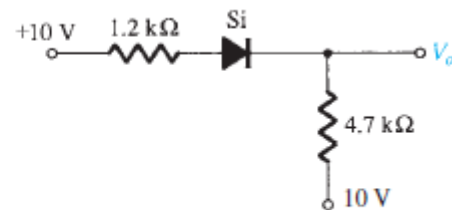

(b)

5. Determine V_o and I for the networks shown below.

Answer:

For Part A, The Si diode will be “on” when the voltage is 0.7 Volts, this means the GaAs diode will not reach V_k or on voltage of 1.2 V because the Si diode will “hold” the voltage across both diodes at 0.7 V

For Part B, use KVL


(a) Si diode “on” preventing GaAs diode from turning “on”:

$$I = \frac{1\text{ V} - 0.7\text{ V}}{1\text{ k}\Omega} = \frac{0.3\text{ V}}{1\text{ k}\Omega} = 0.3\text{ mA}$$


$$V_o = 1\text{ V} - 0.7\text{ V} = 0.3\text{ V}$$

$$(b) I = \frac{16\text{ V} - 0.7\text{ V} - 0.7\text{ V} + 4\text{ V}}{4.7\text{ k}\Omega} = \frac{18.6\text{ V}}{4.7\text{ k}\Omega} = 3.96\text{ mA}$$
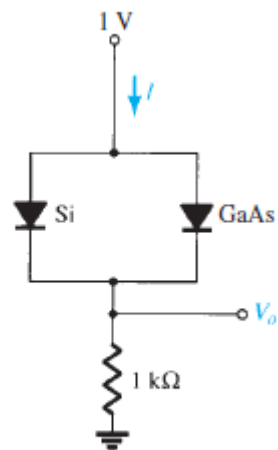
$$V_o = 16\text{ V} - 0.7\text{ V} - 0.7\text{ V} = 14.6\text{ V}$$



(a)

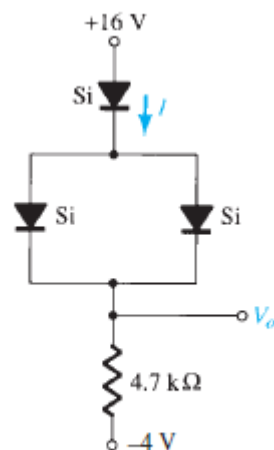

(b)