

1. For the cascade amplifier calculate the dc bias voltages currents of each stage.

From graph $V_{GS_Q} = -0.95 \text{ V}$, $I_{D_Q} = 2.9 \text{ mA}$

$$V_D = 10 \text{ V} - I_D(1.8 \text{ k}\Omega) = 10 \text{ V} - (2.9 \text{ mA})(1.8 \text{ k}\Omega) = 10 \text{ V} - 5.22 \text{ V} \\ = 4.78 \text{ V}$$

$$V_S = I_D R_S = (2.9 \text{ mA})(330 \text{ }\Omega) = 0.957 \text{ V}$$

$$V_{DS} = V_D - V_S = 4.78 \text{ V} - 0.957 \text{ V} = 3.82 \text{ V}$$

$$V_G = 0 \text{ V}$$

$$I_D = I_S = 2.9 \text{ mA}$$

$$I_G = 0 \text{ A}$$

$$B_{RE} \geq 10R_2$$

$$(150)(2.2 \text{ k}\Omega) \geq 10(8.2 \text{ k}\Omega)$$

$$330 \text{ k}\Omega \geq 82 \text{ k}\Omega \text{ checks}$$

$$V_B = \frac{8.2 \text{ k}\Omega(10 \text{ V})}{8.2 \text{ k}\Omega + 24 \text{ k}\Omega} = 2.55 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.55 \text{ V} - 0.7 \text{ V} = 1.85 \text{ V}$$

$$I_E \cong I_C = \frac{V_E}{R_E} = \frac{1.85 \text{ V}}{2.2 \text{ k}\Omega} = 0.84 \text{ mA}$$

$$V_C = 10 \text{ V} - I_C 2.7 \text{ k}\Omega = 10 \text{ V} - (0.84 \text{ mA})(2.7 \text{ k}\Omega) \\ = 10 \text{ V} - 2.27 \text{ V} = 7.73 \text{ V}$$

$$V_{CE} = V_C - V_E = 7.73 \text{ V} - 1.85 \text{ V} = 5.88 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = \frac{0.84 \text{ mA}}{150} = 5.6 \text{ }\mu\text{A}$$

2. For the amplifier circuit calculate the voltage gain of each stage and the overall amplifier voltage gain. Include the dynamic model.

$$Z_{i_2} = 8.2 \text{ k}\Omega \parallel 24 \text{ k}\Omega \parallel \beta(2.2 \text{ k}\Omega)$$

$$= 6.11 \text{ k}\Omega \parallel 330 \text{ k}\Omega \cong 6 \text{ k}\Omega$$

$$A_{v_1} = -g_m (R_D \parallel Z_{i_2})$$

$$g_m = \frac{2I_{DSS}}{|V_P|} \left(1 - \frac{V_{GS}}{V_P}\right) = \frac{2(6 \text{ mA})}{3} \left(1 - \frac{0.95 \text{ V}}{3 \text{ V}}\right)$$

$$= 2.73 \text{ mS}$$

$$A_{v_1} = -(2.73 \text{ mS})(1.8 \text{ k}\Omega \parallel 6 \text{ k}\Omega)$$

$$= -3.77$$

$$A_{v_2} = -\frac{R_C}{r_e}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{0.84 \text{ mA}} = 30.95 \Omega$$

$$A_{v_2} = -\frac{2.7 \text{ k}\Omega}{30.95 \Omega} = -87.2$$


$$A_{v_T} = A_{v_1} \cdot A_{v_2} = (-3.77)(-87.2) = 328.74$$

3. Calculate the input impedance (Z_i) and output impedance (Z_o) for the amplifier circuit

$$Z_i = 10 \text{ M}\Omega$$

$$Z_o \cong R_C = 2.7 \text{ k}\Omega$$

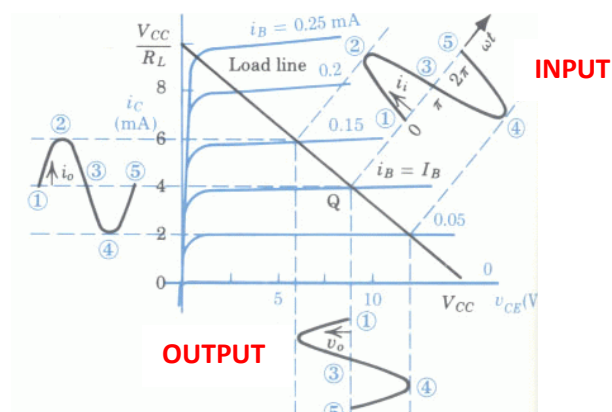
4. What is the maximum input voltage (V_{pp}) allowed to prevent distortion.
For no distortion the output must be less than the supply voltage V_{CC} , this is 10 Volts, allowing for the saturation and cutoff areas of the BJT response curve the output should be no greater than 8 Vpp



$$A_v = \frac{V_o}{V_i}$$

$$\therefore 328.74 = \frac{8}{V_i}$$

$$V_i < 24 \text{ mV}$$

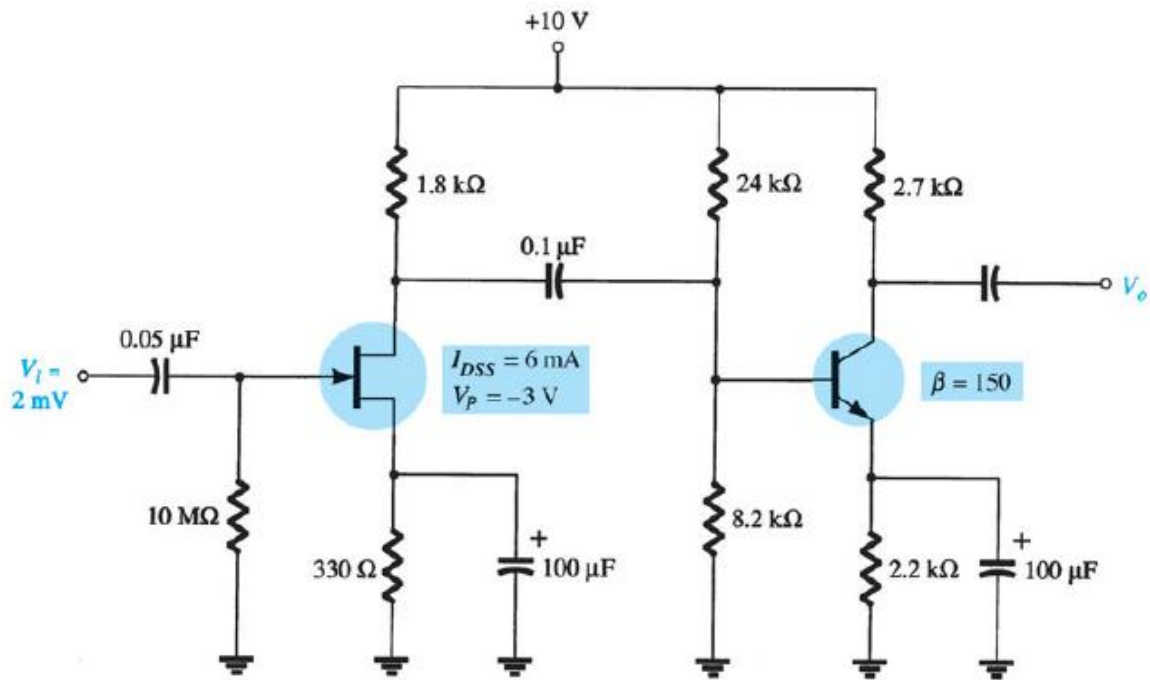

5. Design the self-bias network below to have a gain of 10. The device should be biased at $V_{GSQ} = 1/3 V_P$.

$$V_{GSQ} = \frac{1}{3} V_P = \frac{1}{3} (-3 \text{ V}) = -1 \text{ V}$$

$$I_{DQ} = I_{DSS} \left(1 - \frac{V_{GSQ}}{V_P} \right)^2 = 12 \text{ mA} \left(1 - \frac{-1 \text{ V}}{-3 \text{ V}} \right)^2 = 5.33 \text{ mA}$$

$$R_S = \frac{V_S}{I_{DQ}} = \frac{1 \text{ V}}{5.33 \text{ mA}} = 187.62 \Omega \therefore \text{Use } R_S = 180 \Omega$$

$$g_m = \frac{2I_{DSS}}{V_P} \left(1 - \frac{V_{GSQ}}{V_P} \right) = \frac{2(12 \text{ mA})}{3 \text{ V}} \left(1 - \frac{-1 \text{ V}}{-3 \text{ V}} \right) = 5.33 \text{ mS}$$

$$A_v = -g_m (R_D \parallel r_d) = -10$$

$$\text{or } R_D \parallel 40 \text{ k}\Omega = \frac{-10}{5.33 \text{ mS}} = 1.876 \text{ k}\Omega$$

$$= 1.876 \text{ k}\Omega$$

$$40 \text{ k}\Omega R_D = 1.876 \text{ k}\Omega R_D + 75.04 \text{ k}\Omega^2$$

$$38.124 R_D = 75.04 \text{ k}\Omega$$

$$R_D = 1.97 \text{ k}\Omega \Rightarrow R_D = 2 \text{ k}\Omega$$

