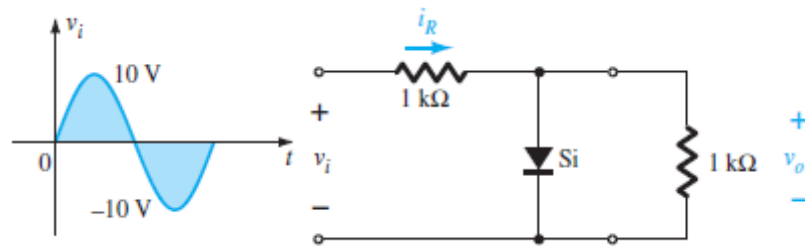


Remember to check your calculations using LTSpice

1. For the network below, sketch v_o and i_R



Answer:

Diode will conduct when $v_o = 0.7 \text{ V}$; that is,

$$v_o = 0.7 \text{ V} = \frac{1 \text{ k}\Omega(v_i)}{1 \text{ k}\Omega + 1 \text{ k}\Omega}$$

Solving: $v_i = 1.4 \text{ V}$

For $v_i \geq 1.4 \text{ V}$ Si diode is “on” and $v_o = 0.7 \text{ V}$.

For $v_i < 1.4 \text{ V}$ Si diode is open and level of v_o is determined by voltage divider rule:

$$v_o = \frac{1 \text{ k}\Omega(v_i)}{1 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.5 v_i$$



For $v_i = -10 \text{ V}$:

$$v_o = 0.5(-10 \text{ V}) = -5 \text{ V}$$


When $v_o = 0.7 \text{ V}$, $v_{R_{\max}} = v_{i_{\max}} - 0.7 \text{ V}$
 $= 10 \text{ V} - 0.7 \text{ V} = 9.3 \text{ V}$

$$I_{R_{\max}} = \frac{9.3 \text{ V}}{1 \text{ k}\Omega} = 9.3 \text{ mA}$$
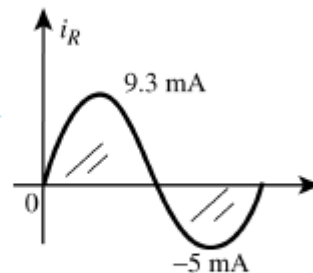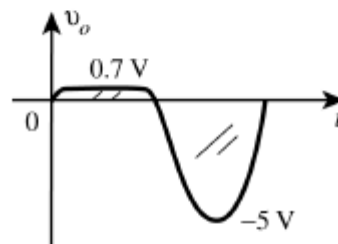
$$I_{\max}(\text{reverse}) = \frac{10 \text{ V}}{1 \text{ k}\Omega + 1 \text{ k}\Omega} = 0.5 \text{ mA}$$



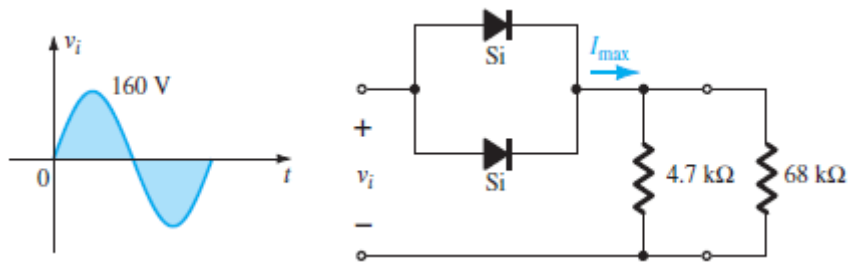2. a. Given $P_{\max} = 14 \text{ mW}$ for each diode at Fig. 2.172, determine the maximum current rating of each diode (using the approximate equivalent model).
- b. Determine I_{\max} for the parallel diodes.
- c. Determine the current through each diode at V_{\max} using the results of part (b).
- d. If only one diode were present, which would be the expected result?



Answer:

$$(a) \quad P_{\max} = 14 \text{ mW} = (0.7 \text{ V})I_D$$

$$I_D = \frac{14 \text{ mW}}{0.7 \text{ V}} = 20 \text{ mA}$$

$$(b) \quad I_{\max} = 2 \times 20 \text{ mA} = 40 \text{ mA}$$


$$(c) \quad 4.7 \text{ k}\Omega \parallel 68 \text{ k}\Omega = 4.4 \text{ k}\Omega$$

$$V_R = 160 \text{ V} - 0.7 \text{ V} = 159.3 \text{ V}$$

$$I_{\max} = \frac{159.3 \text{ V}}{4.4 \text{ k}\Omega} = 36.2 \text{ mA}$$

$$I_d = \frac{I_{\max}}{2} = 18.1 \text{ mA}$$

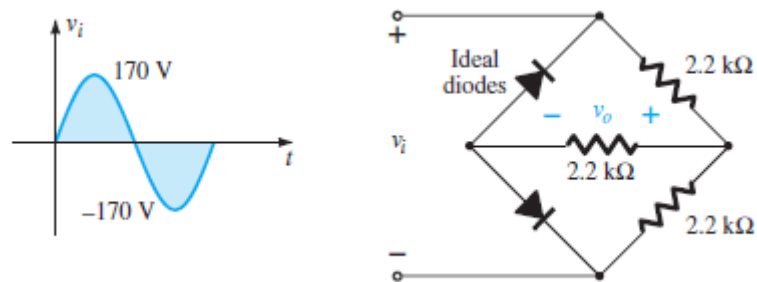3. Sketch v_o for the network below and determine the dc voltage available.



Answer:

Positive pulse of v_i :

Top left diode “off”, bottom left diode “on”

$$2.2 \text{ k}\Omega \parallel 2.2 \text{ k}\Omega = 1.1 \text{ k}\Omega$$

$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega (170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$




Negative pulse of v_i :

Top left diode “on”, bottom left diode “off”

$$V_{o_{\text{peak}}} = \frac{1.1 \text{ k}\Omega (170 \text{ V})}{1.1 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 56.67 \text{ V}$$

$$V_{\text{dc}} = 0.636(56.67 \text{ V}) = 36.04 \text{ V}$$

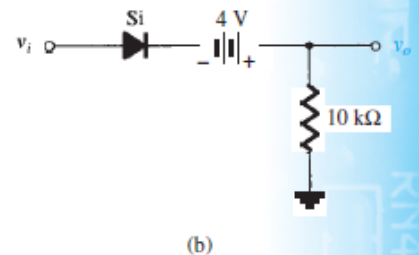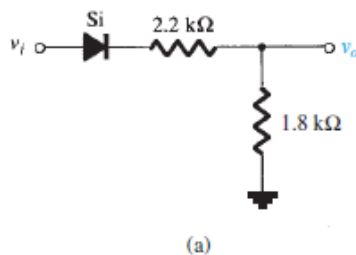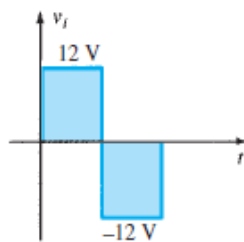4. Determine v_o for each network shown below, for the input shown.



Answer:

- (a) Positive pulse of v_i :

$$V_o = \frac{1.8 \text{ k}\Omega (12 \text{ V} - 0.7 \text{ V})}{1.8 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 5.09 \text{ V}$$

Negative pulse of v_i :


diode “open”, $v_o = 0 \text{ V}$

- (b) Positive pulse of v_i :


$$V_o = 12 \text{ V} - 0.7 \text{ V} + 4 \text{ V} = 15.3 \text{ V}$$

Negative pulse of v_i :

diode “open”, $v_o = 0 \text{ V}$

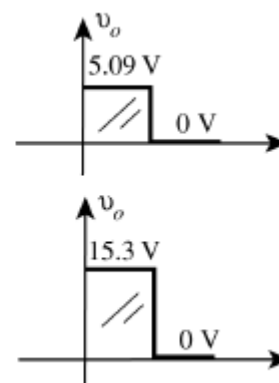

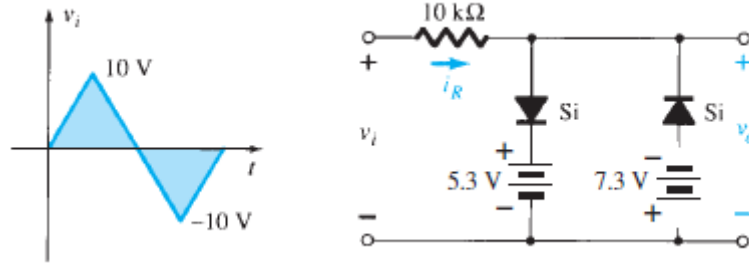5. Sketch i_R and v_o for the network shown below for the input shown.



Answer:

For the positive region of v_i :

The right Si diode is reverse-biased.

The left Si diode is “on” for levels of v_i greater than $5.3 \text{ V} + 0.7 \text{ V} = 6 \text{ V}$. In fact, $v_o = 6 \text{ V}$ for $v_i \geq 6 \text{ V}$.


For $v_i < 6 \text{ V}$ both diodes are reverse-biased and $v_o = v_i$.

For the negative region of v_i :


The left Si diode is reverse-biased.

The right Si diode is “on” for levels of v_i more negative than $7.3 \text{ V} + 0.7 \text{ V} = 8 \text{ V}$. In fact, $v_o = -8 \text{ V}$ for $v_i \leq -8 \text{ V}$.

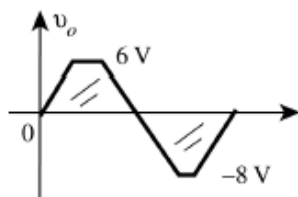
For $v_i > -8 \text{ V}$ both diodes are reverse-biased and $v_o = v_i$.



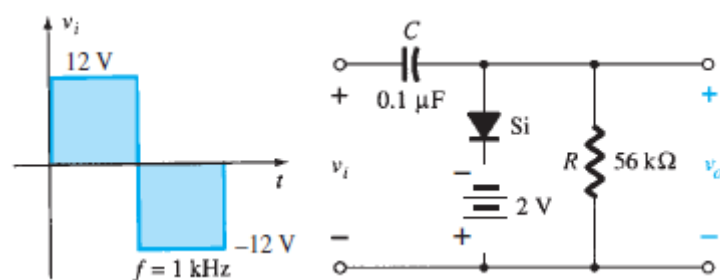
6. For the network shown below :
- Calculate $5t$.
 - Compare $5t$ to half the period of the applied signal.
 - Sketch v_o .



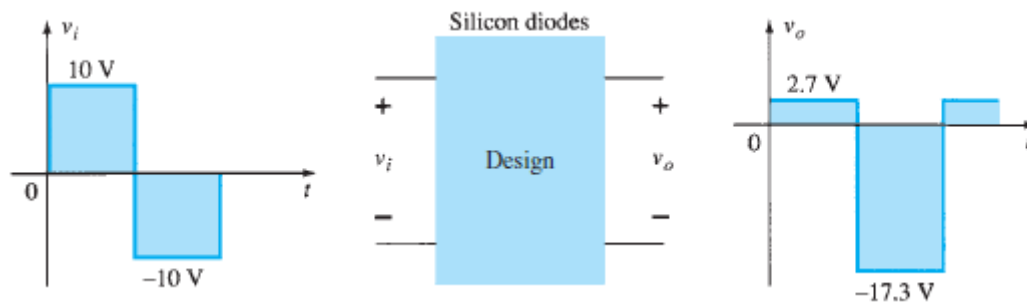
7. Design a clamper to perform the function indicated



Answer:

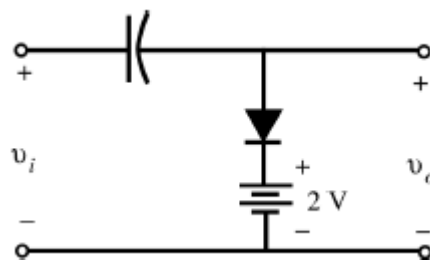

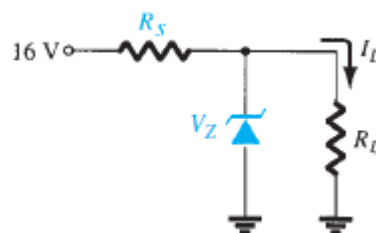8. a. Design the network shown below to maintain V_L at 12 V for a load variation (I_L) from 0 mA to 200 mA. That is, determine R_s and V_Z .
- b. Determine $P_{Z_{\max}}$ for the Zener diode of part (a).



Answer:

$$(a) \quad V_Z = 12 \text{ V}, R_L = \frac{V_L}{I_L} = \frac{12 \text{ V}}{200 \text{ mA}} = 60 \, \Omega$$

$$V_L = V_Z = 12 \text{ V} = \frac{R_L V_i}{R_L + R_s} = \frac{60 \, \Omega (16 \text{ V})}{60 \, \Omega + R_s}$$

$$720 + 12R_s = 960$$

$$12R_s = 240$$

$$R_s = 20 \, \Omega$$

$$(b) \quad P_{Z_{\max}} = V_Z I_{Z_{\max}} \\ = (12 \text{ V})(200 \text{ mA}) \\ = 2.4 \text{ W}$$