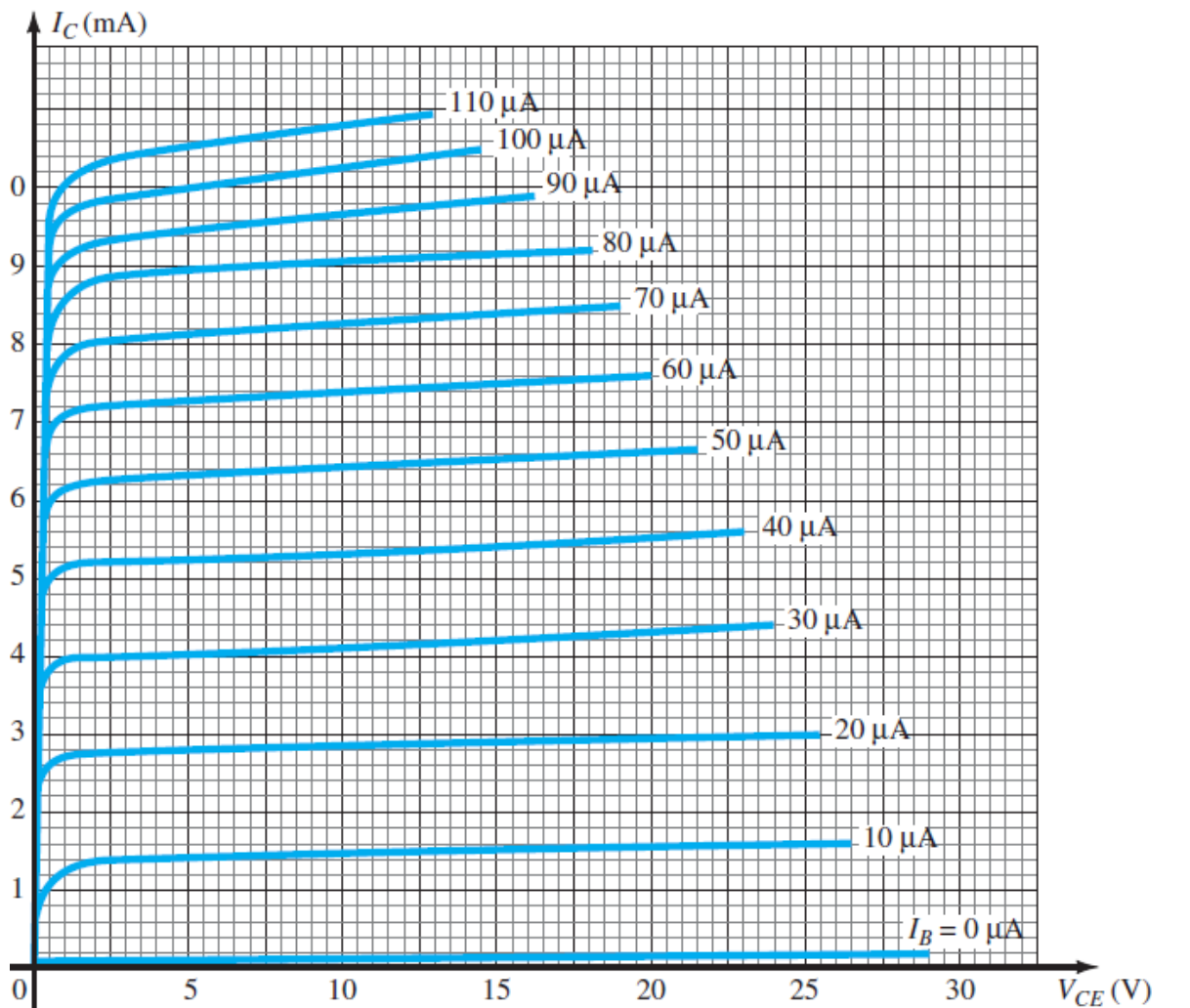


1. Given the BJT transistor characteristics below:

- Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_C = 3\text{ k}_\Omega$ for a fixed-bias configuration.
- Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
- What are the resulting values of I_{CQ} and V_{CEQ} ?
- What is the value of β at the operating point?
- What is the value of α defined by the operating point?
- What is the saturation current ($I_{C_{sat}}$) for the design?
- Sketch the resulting fixed-bias configuration.
- What is the dc power dissipated by the device at the operating point?
- What is the power supplied by V_{CC} ?
- Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).



ANSWER:

(a) Load line intersects vertical axis at $I_C = \frac{21 \text{ V}}{3 \text{ k}\Omega} = 7 \text{ mA}$
and horizontal axis at $V_{CE} = 21 \text{ V}$.

(b) $I_B = 25 \text{ }\mu\text{A}$: $R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{21 \text{ V} - 0.7 \text{ V}}{25 \text{ }\mu\text{A}} = 812 \text{ k}\Omega$

(c) $I_{C_Q} \cong 3.4 \text{ mA}$, $V_{CE_Q} \cong 10.75 \text{ V}$

(d) $\beta = \frac{I_C}{I_B} = \frac{3.4 \text{ mA}}{25 \text{ }\mu\text{A}} = 136$

(e) $\alpha = \frac{\beta}{\beta + 1} = \frac{136}{136 + 1} = \frac{136}{137} = 0.992$

(f) $I_{C_{\text{sat}}} = \frac{V_{CC}}{R_C} = \frac{21 \text{ V}}{3 \text{ k}\Omega} = 7 \text{ mA}$

(g) —


(h) $P_D = V_{CE_Q} I_{C_Q} = (10.75 \text{ V})(3.4 \text{ mA}) = 36.55 \text{ mW}$

(i) $P_s = V_{CC}(I_C + I_B) = 21 \text{ V}(3.4 \text{ mA} + 25 \text{ }\mu\text{A}) = 71.92 \text{ mW}$

(j) $P_R = P_s - P_D = 71.92 \text{ mW} - 36.55 \text{ mW} = 35.37 \text{ mW}$

2. Given $V_B = 4 \text{ V}$ for the network below, determine:

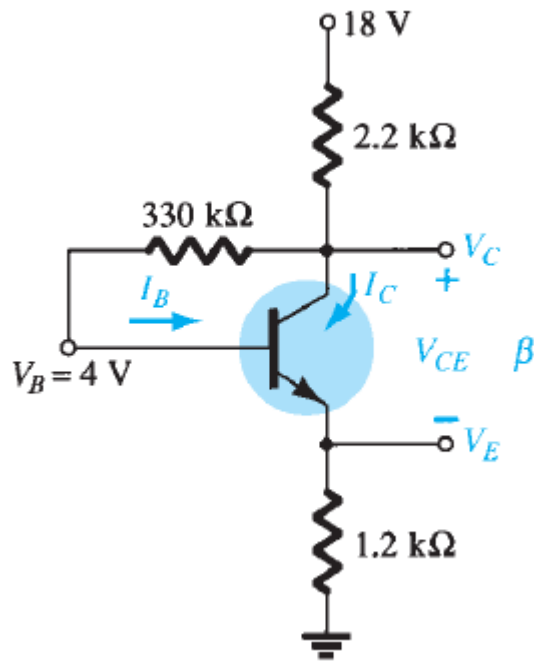- a. V_E .
- b. I_C .
- c. V_C .
- d. V_{CE} .
- e. I_B .
- f. β .



ANSWER:

$$(a) \quad V_E = V_B - V_{BE} = 4 \text{ V} - 0.7 \text{ V} = 3.3 \text{ V}$$

$$(b) \quad I_C \cong I_E = \frac{V_E}{R_E} = \frac{3.3 \text{ V}}{1.2 \text{ k}\Omega} = 2.75 \text{ mA}$$


$$(c) \quad V_C = V_{CC} - I_C R_C = 18 \text{ V} - (2.75 \text{ mA})(2.2 \text{ k}\Omega) \\ = 11.95 \text{ V}$$

$$(d) \quad V_{CE} = V_C - V_E = 11.95 \text{ V} - 3.3 \text{ V} = 8.65 \text{ V}$$

$$(e) \quad I_B = \frac{V_{R_B}}{R_B} = \frac{V_C - V_B}{R_B} = \frac{11.95 \text{ V} - 4 \text{ V}}{330 \text{ k}\Omega} = 24.09 \mu\text{A}$$

$$(f) \quad \beta = \frac{I_C}{I_B} = \frac{2.75 \text{ mA}}{24.09 \mu\text{A}} = 114.16$$

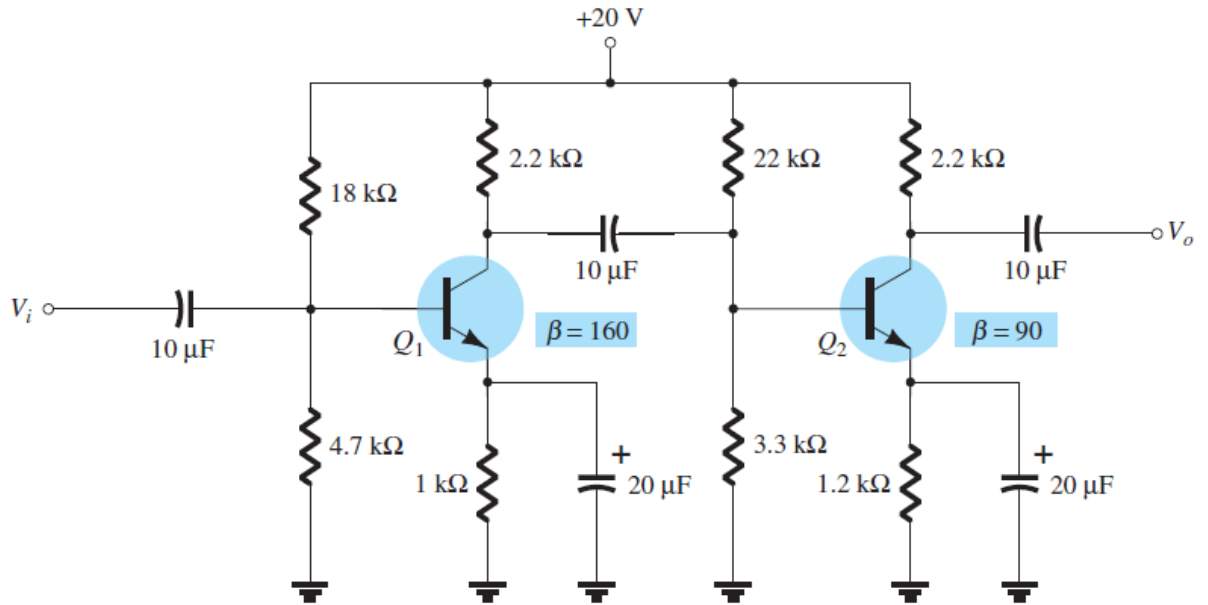3. For the R - C -coupled amplifier of below determine
- the voltages V_B , V_C , and V_E for each transistor.
 - the currents I_B , I_C , and I_E for each transistor



ANSWER:

$$(a) \quad V_{B_1} = \frac{4.7 \text{ k}\Omega (20 \text{ V})}{4.7 \text{ k}\Omega + 18 \text{ k}\Omega} = 4.14 \text{ V}$$

$$V_{E_1} = 4.14 \text{ V} - 0.7 \text{ V} = 3.44 \text{ V}$$

$$I_{C_1} \cong I_{E_1} = \frac{3.44 \text{ V}}{1 \text{ k}\Omega} = 3.44 \text{ mA}$$

$$V_{C_1} = 20 \text{ V} - (3.44 \text{ mA})(2.2 \text{ k}\Omega) = 12.43 \text{ V}$$

$$V_{B_2} = \frac{3.3 \text{ k}\Omega (20 \text{ V})}{3.3 \text{ k}\Omega + 22 \text{ k}\Omega} = 2.61 \text{ V}$$

$$V_{E_2} = 2.61 \text{ V} - 0.7 \text{ V} = 1.91 \text{ V}$$


$$I_{E_2} \cong I_{C_2} = \frac{1.91 \text{ V}}{1.2 \text{ k}\Omega} = 1.59 \text{ mA}$$

$$V_{C_2} = 20 \text{ V} - (1.59 \text{ mA})(2.2 \text{ k}\Omega) = 16.5 \text{ V}$$

$$(b) \quad I_{B_1} = \frac{I_{C_1}}{\beta} = \frac{3.44 \text{ mA}}{160} = 21.5 \mu\text{A}, \quad I_{C_1} \cong I_{E_1} = 3.44 \text{ mA}$$

$$I_{B_2} = \frac{I_{C_2}}{\beta} = \frac{1.59 \text{ mA}}{90} = 17.67 \mu\text{A}, \quad I_{C_2} \cong I_{E_2} = 1.59 \text{ mA}$$

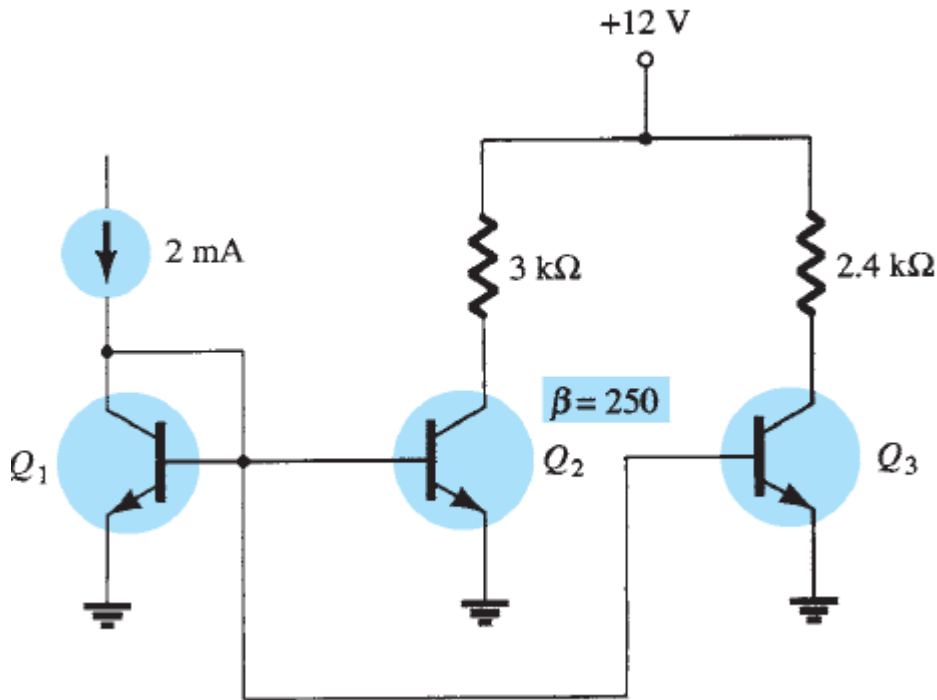4. Calculate collector currents for Q_1 and Q_2 in figure below




ANSWER:

For current mirror:

$$I(3 \text{ k}\Omega) = I(2.4 \text{ k}\Omega) = I = 2 \text{ mA}$$

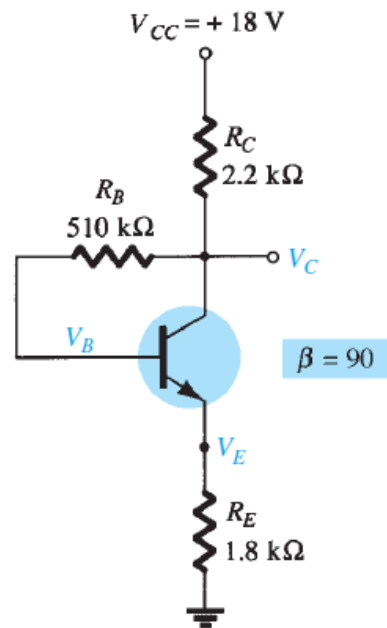5. Answer the following questions about the circuit below :

- What happens to the voltage V_C if the resistor R_B is open?
- What should happen to V_{CE} if β increases due to temperature?
- How will V_E be affected when replacing the collector resistor with one whose resistance is at the lower end of the tolerance range?
- If the transistor collector connection becomes open, what will happen to V_E ?
- What might cause V_{CE} to become nearly 18 V?



ANSWER:

- (a) R_B open, $I_B = 0 \mu\text{A}$, $I_C = I_{CEO} \cong 0 \text{ mA}$
and $V_C \cong V_{CC} = 18 \text{ V}$
- (b) $\beta \uparrow$, $I_C \uparrow$, $V_{R_C} \uparrow$, $V_{R_E} \uparrow$, $V_{CE} \downarrow$
- (c) $R_C \downarrow$, $I_B \uparrow$, $I_C \uparrow$, $V_E \uparrow$
- (d) Drop to a relatively low voltage $\cong 0.06 \text{ V}$
- (e) Open in the base circuit