
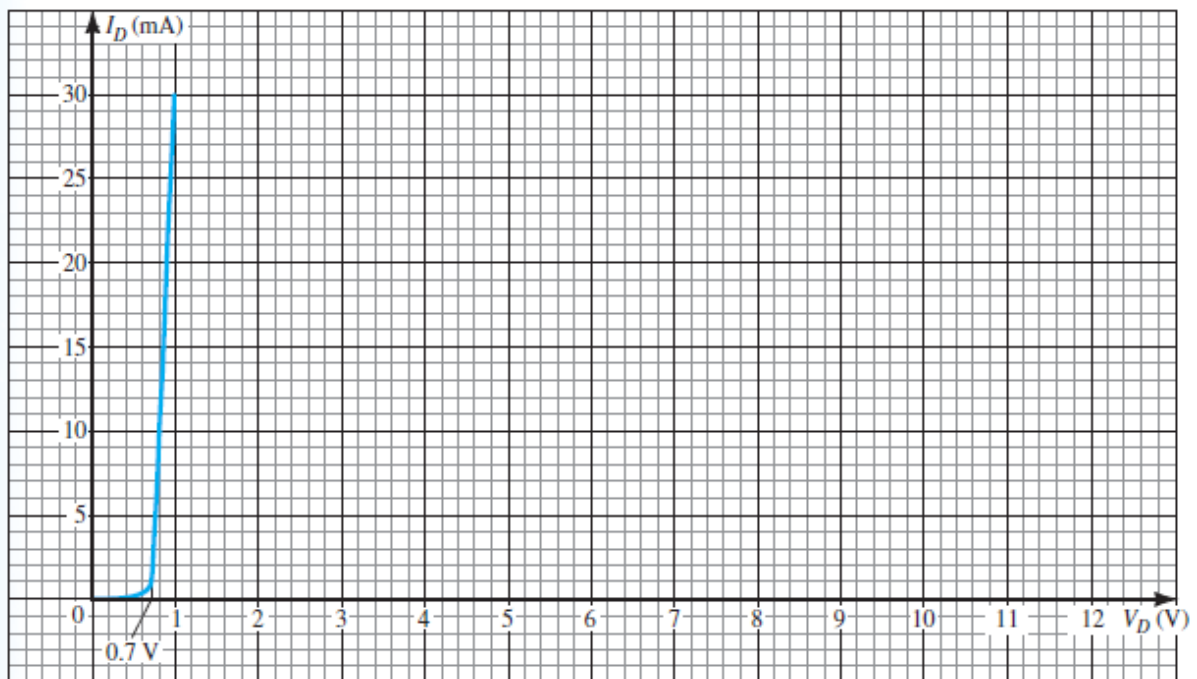


Check your calculations and results by using LTSpice to simulate the circuits

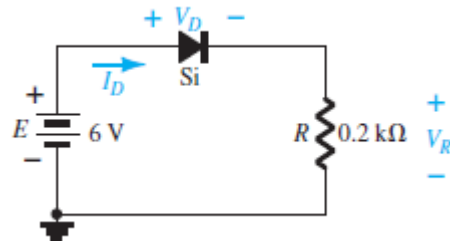
1.

- Using the characteristics shown below, determine I_D and V_D for the circuit shown below.
- Repeat part (a) with $R = 0.47 \text{ k}\Omega$.
- Repeat part (a) with $R = 0.68 \text{ k}\Omega$.
- Is the level of V_D relatively close to 0.7 V in each case?
How do the resulting levels of I_D compare? Comment accordingly.




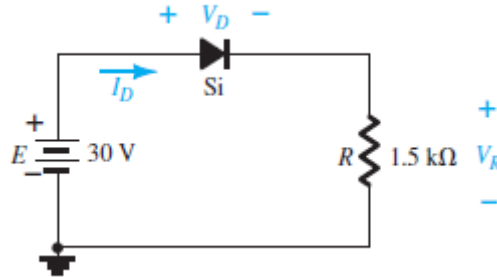2.


- Using the approximate characteristics for the Si diode, determine V_D , I_D , and V_R for the circuit shown below.
- Perform the same analysis as part (a) using the ideal model for the diode.
- Do the results obtained in parts (a) and (b) suggest that the ideal model can provide a good approximation for the actual response under some conditions?



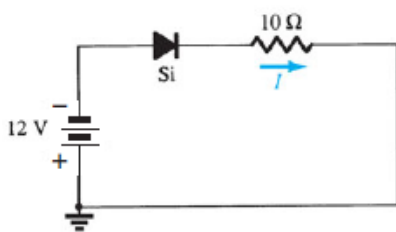
3. Determine the current I for each of the configurations shown below, using the approximate equivalent model for the diode.



(a)

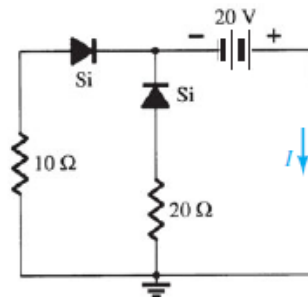


(b)

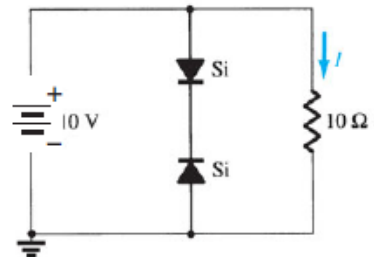


(c)

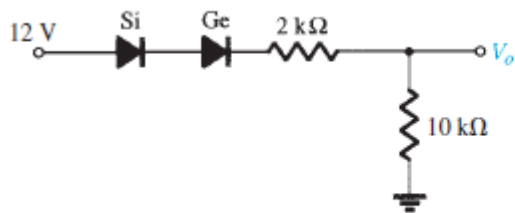4. Determine the level of V_o for each network shown below



(a)

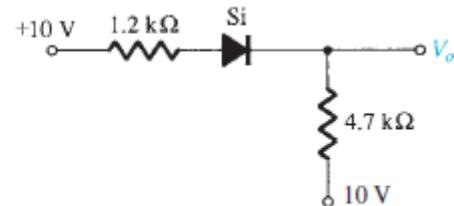

(b)

5. Determine V_o and I for the networks shown below.

