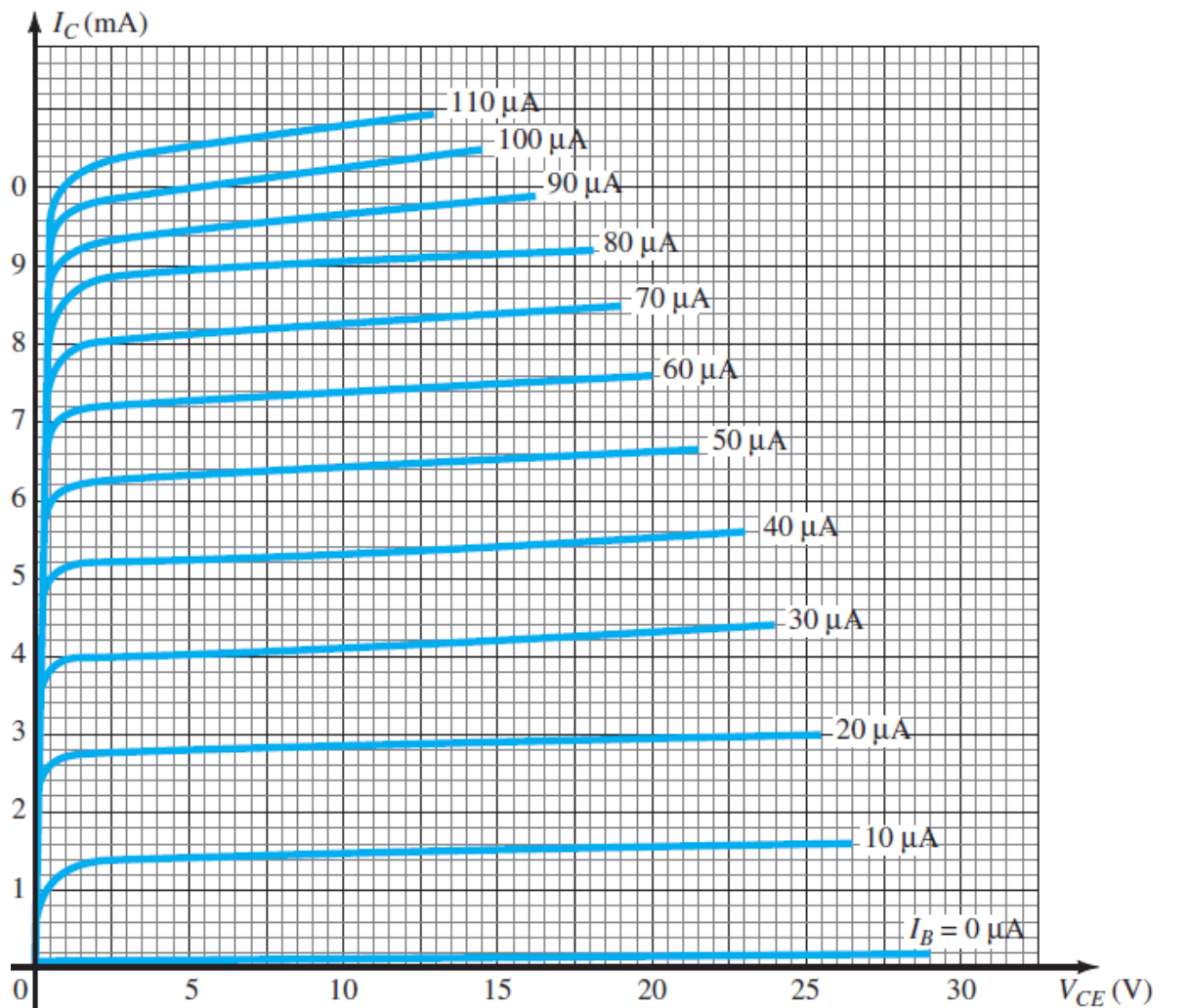



1. Given the BJT transistor characteristics below:

- Draw a load line on the characteristics determined by $E = 21\text{ V}$ and $R_C = 3\text{ k}_\Omega$ for a fixed-bias configuration.
- Choose an operating point midway between cutoff and saturation. Determine the value of R_B to establish the resulting operating point.
- What are the resulting values of I_{CQ} and V_{CEQ} ?
- What is the value of β at the operating point?
- What is the value of α defined by the operating point?
- What is the saturation current ($I_{C_{sat}}$) for the design?
- Sketch the resulting fixed-bias configuration.
- What is the dc power dissipated by the device at the operating point?
- What is the power supplied by V_{CC} ?
- Determine the power dissipated by the resistive elements by taking the difference between the results of parts (h) and (i).



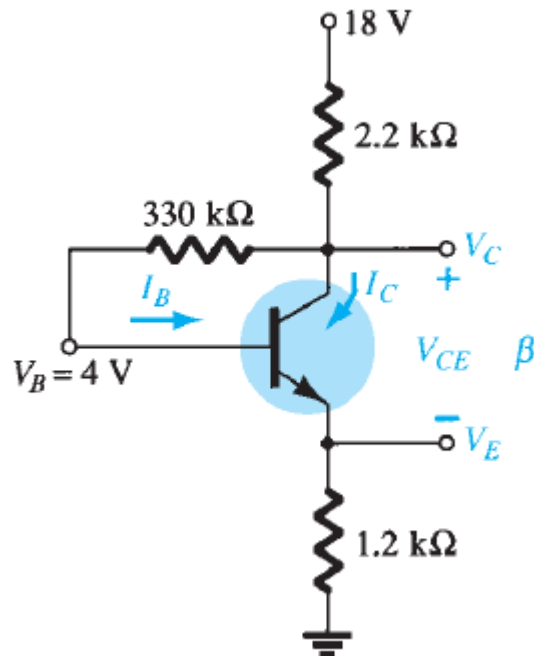
2. Given $V_B = 4\text{ V}$ for the network below, determine:

- V_E .
- I_C .
- V_C .
- V_{CE} .
- I_B .
- β .




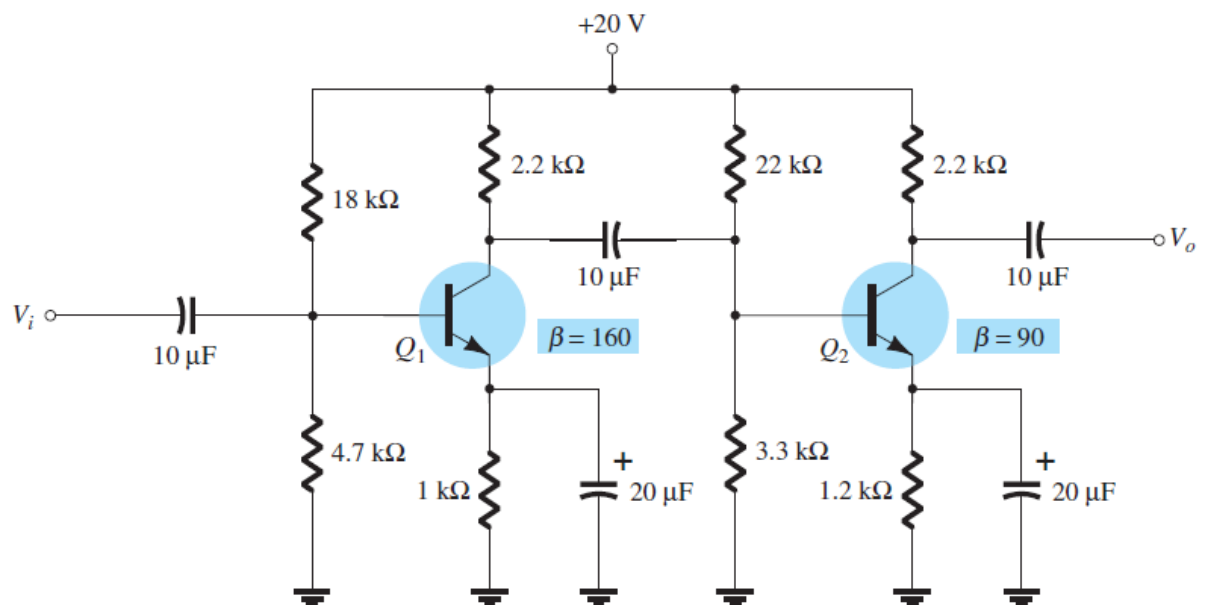3. For the R - C -coupled amplifier of below determine

- the voltages V_B , V_C , and V_E for each transistor.
- the currents I_B , I_C , and I_E for each transistor



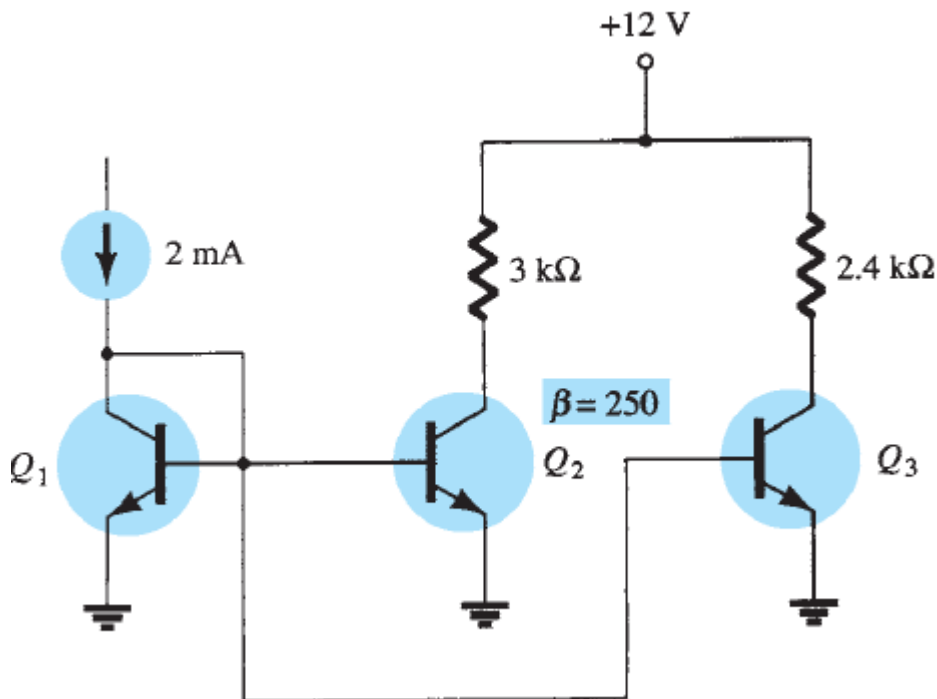4. Calculate collector currents for Q_1 and Q_2 in figure below



5. Answer the following questions about the circuit below :

- What happens to the voltage V_C if the resistor R_B is open?
- What should happen to V_{CE} if β increases due to temperature?
- How will V_E be affected when replacing the collector resistor with one whose resistance is at the lower end of the tolerance range?
- If the transistor collector connection becomes open, what will happen to V_E ?
- What might cause V_{CE} to become nearly 18 V?

