



山东科技大学
济南校区

SHANDONG UNIVERSITY OF SCIENCE & TECHNOLOGY IN JINAN



Frequency Response

Kong Yingying

Shandong University of Science & Technology (Jinan Campus)



Contents


- General Frequency Considerations
- Bode Plot
- Low&High Frequency Response




General Frequency Considerations

The **frequency response** of an amplifier refers to the frequency range in which the amplifier will operate with negligible effects from capacitors and capacitance in devices. This range of frequencies can be called the **mid-range**.

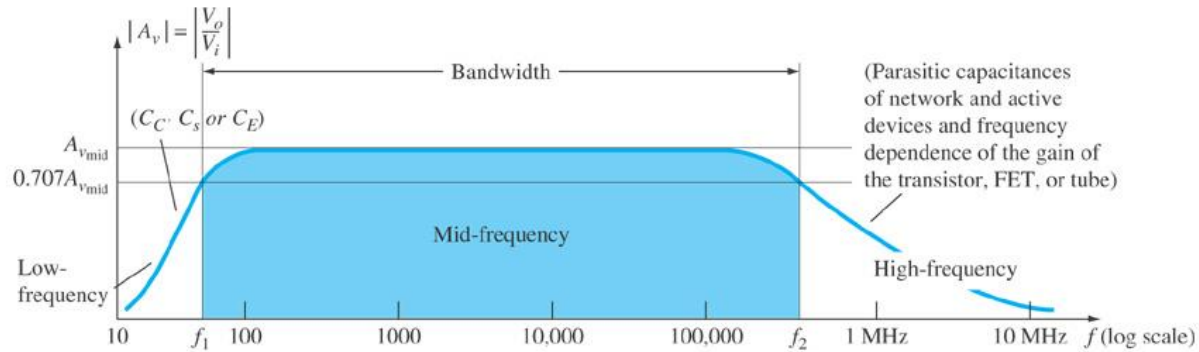
- At frequencies above and below the midrange, capacitance and any inductance will affect the gain of the amplifier.
- At low frequencies the coupling and bypass capacitors lower the gain.
- At high frequencies stray capacitances associated with the active device lower the gain.
- Also, cascading amplifiers limits the gain at high and low frequencies.




(a)

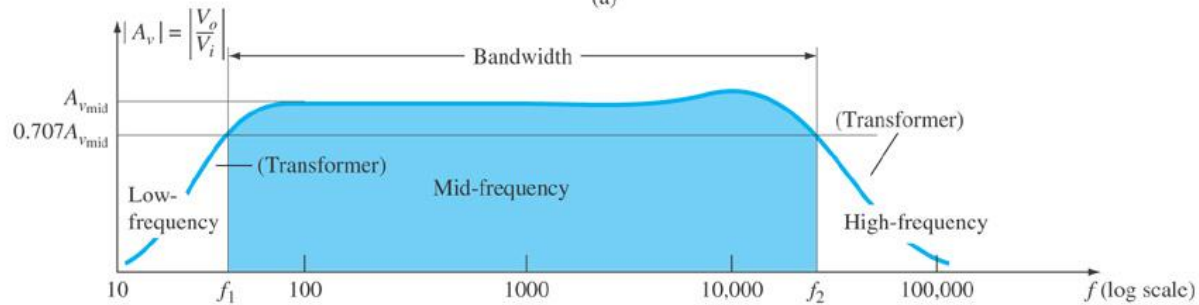


(b)

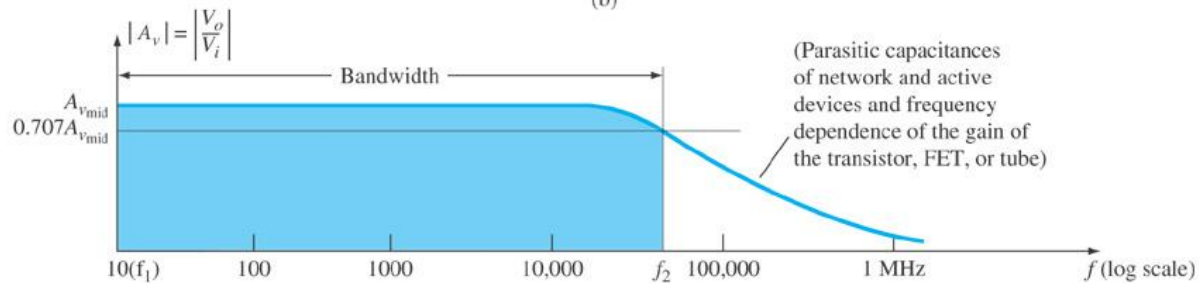




(c)

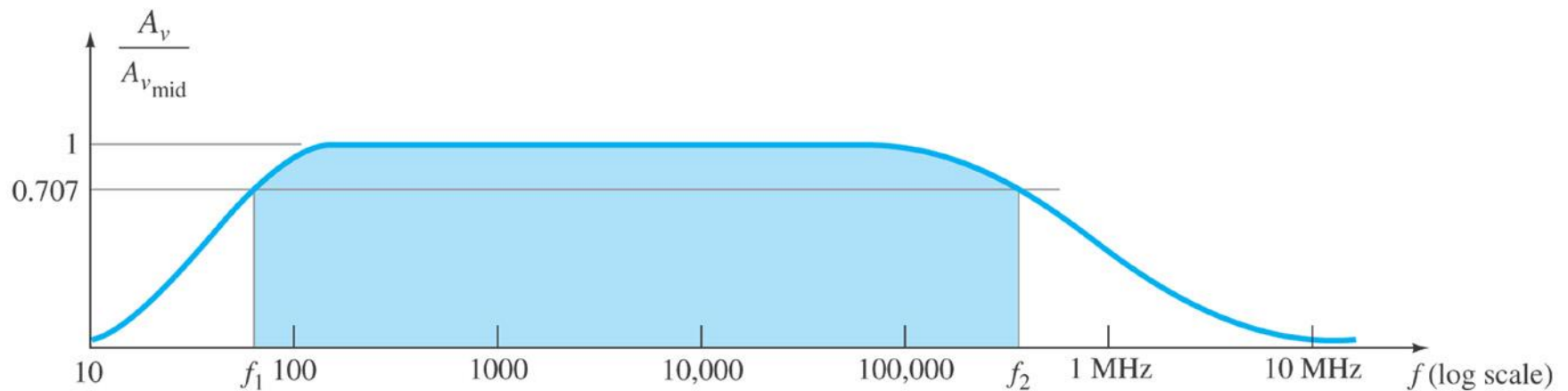


Normalized gain versus frequency plot

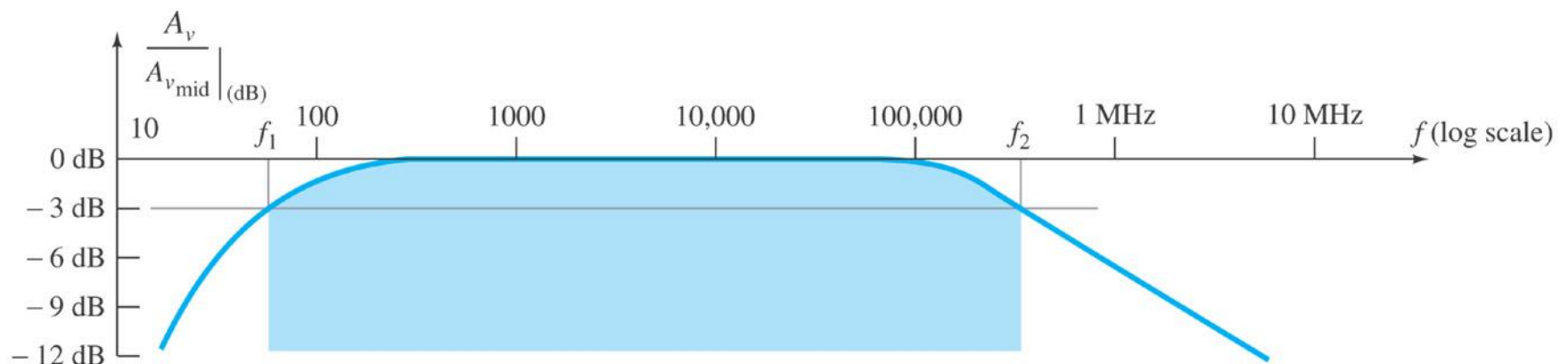

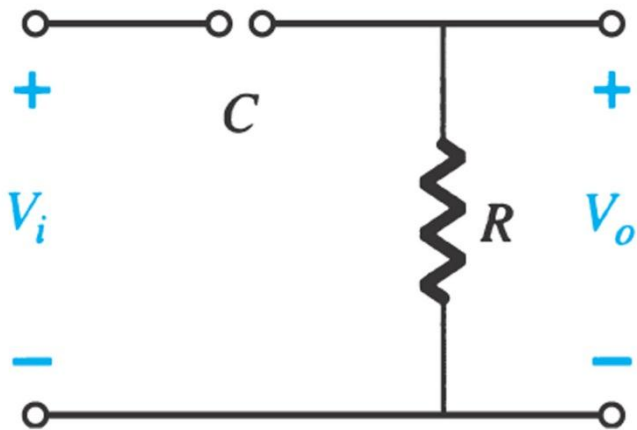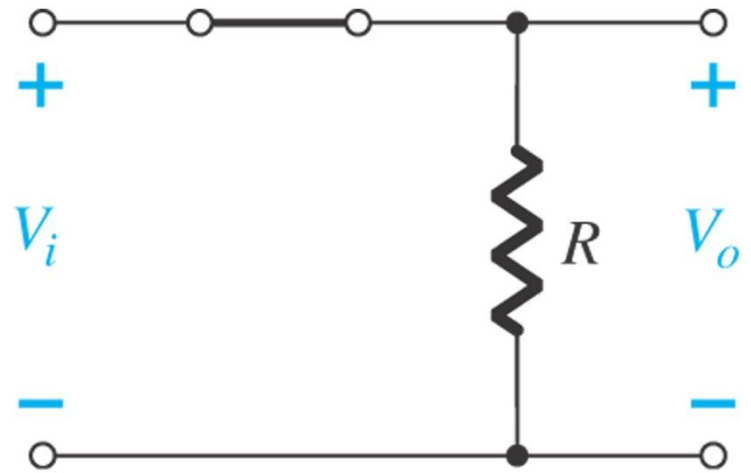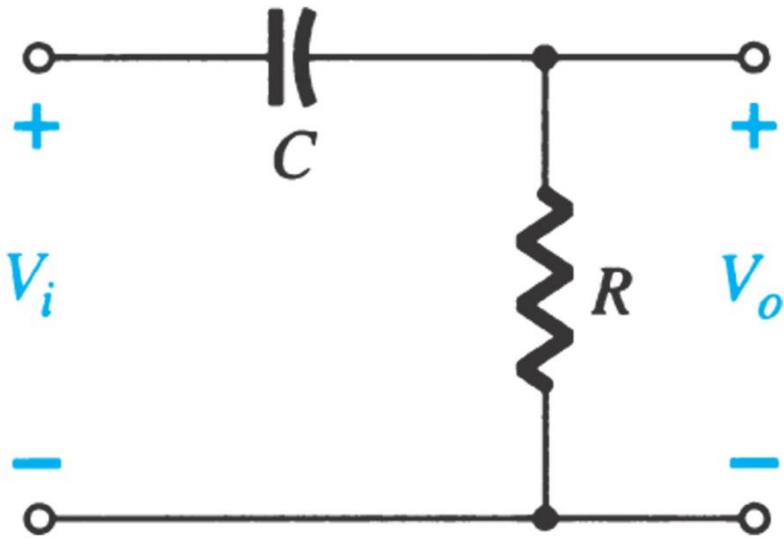
Decibel plot of the normalized gain versus frequency plot



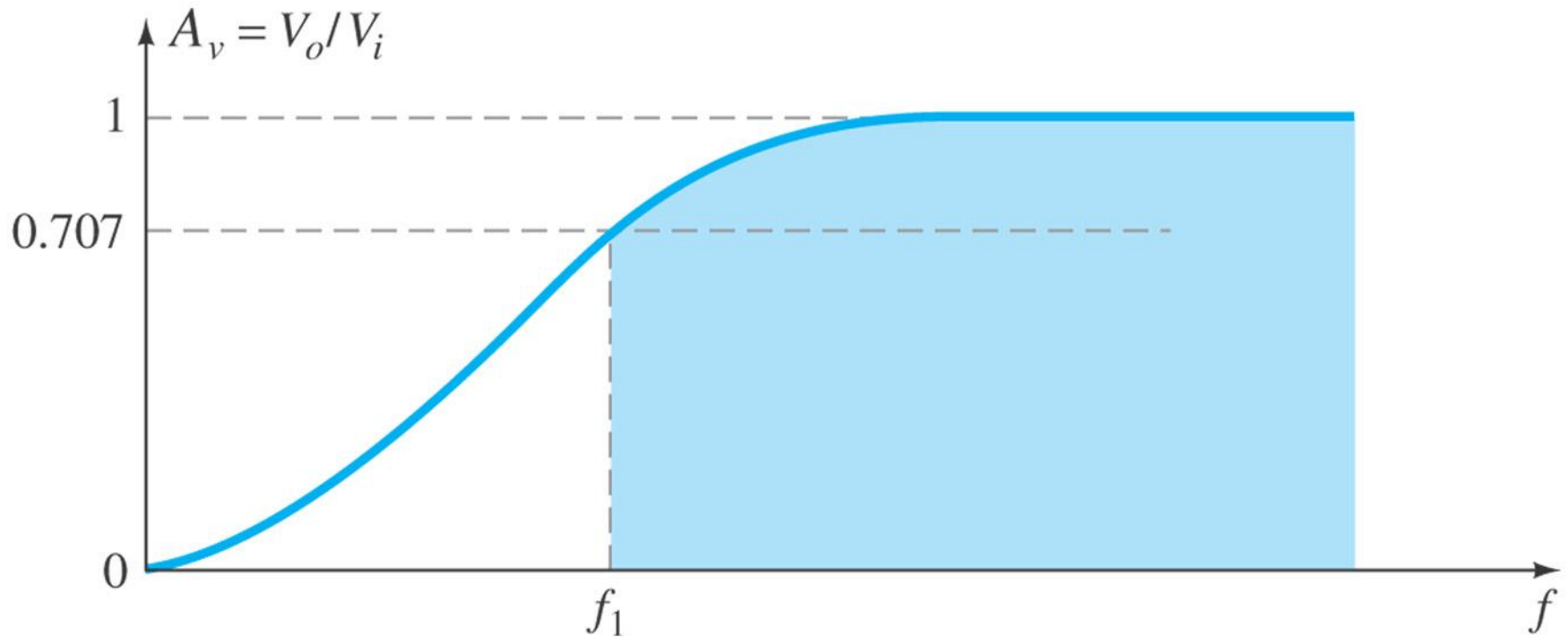
$$A_v = \frac{V_o}{V_i} = \frac{R}{R + X_C}$$



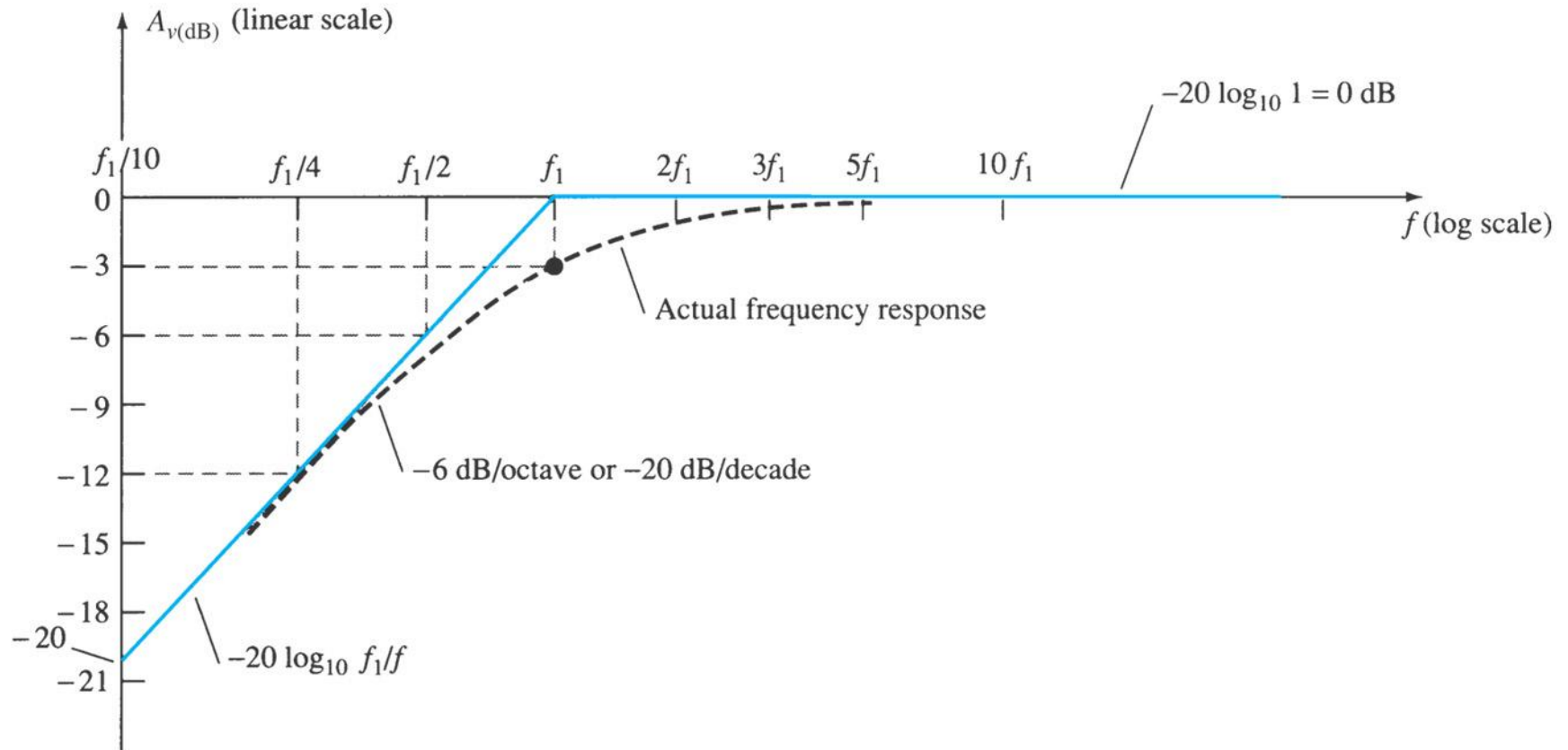
Low-frequency response for the RC circuit of



Bode plot for the low-frequency region.

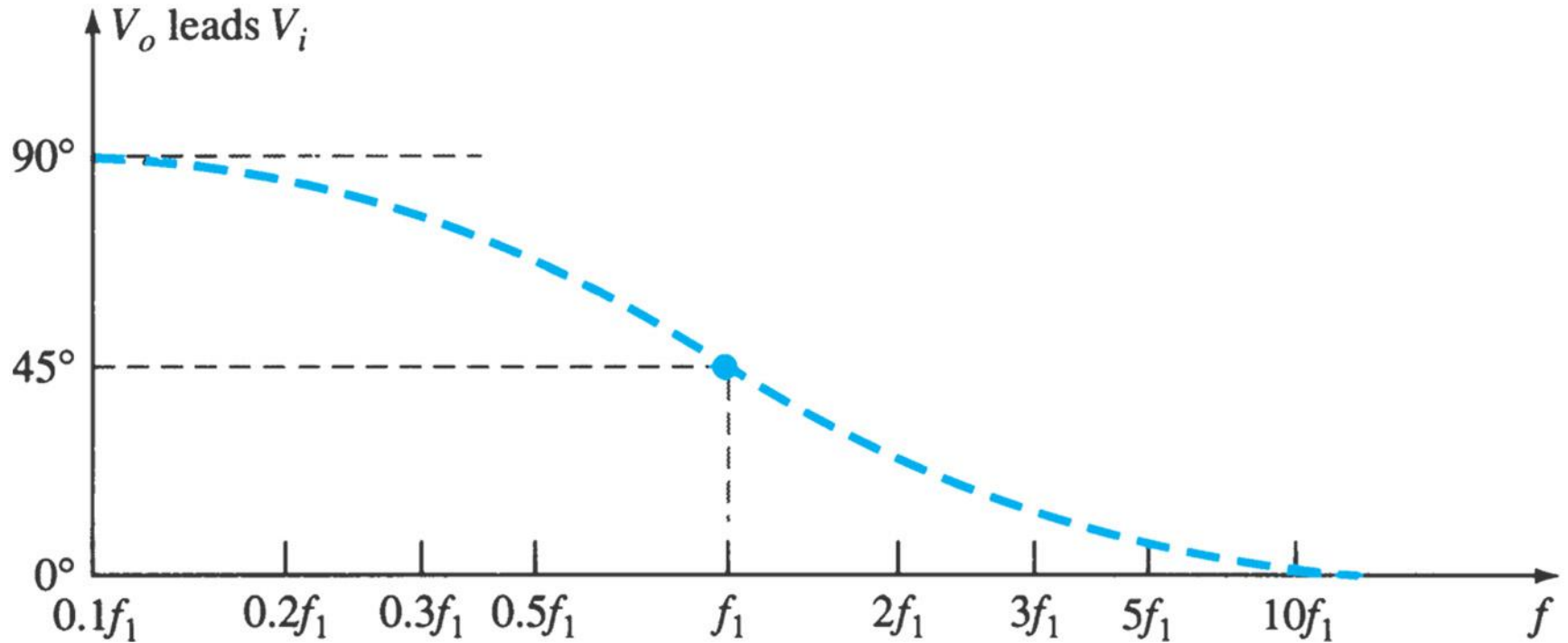

Phase response for the RC circuit

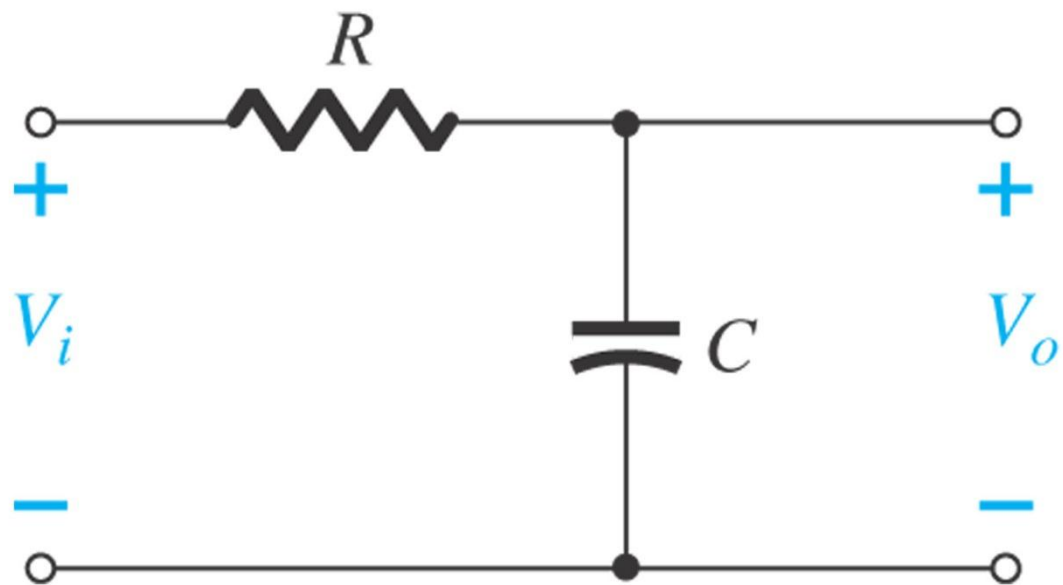




Miller Effect Capacitance

Any p - n junction can develop capacitance. This was mentioned in the chapter on diodes.

In a BJT amplifier, this capacitance becomes noticeable between


- The base-collector junction at high frequencies in common-emitter BJT amplifier configurations**
- The gate-drain junction at high frequencies in common-source FET amplifier configurations.**

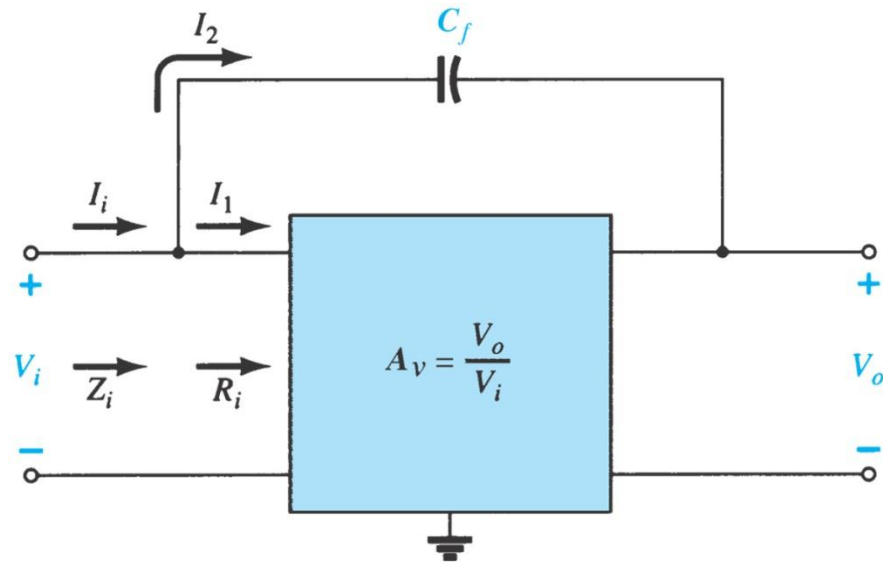
It is called the **Miller Capacitance, and it affects the input and output circuits.**



$$C_{Mi} = (1 - A_v)C_f$$

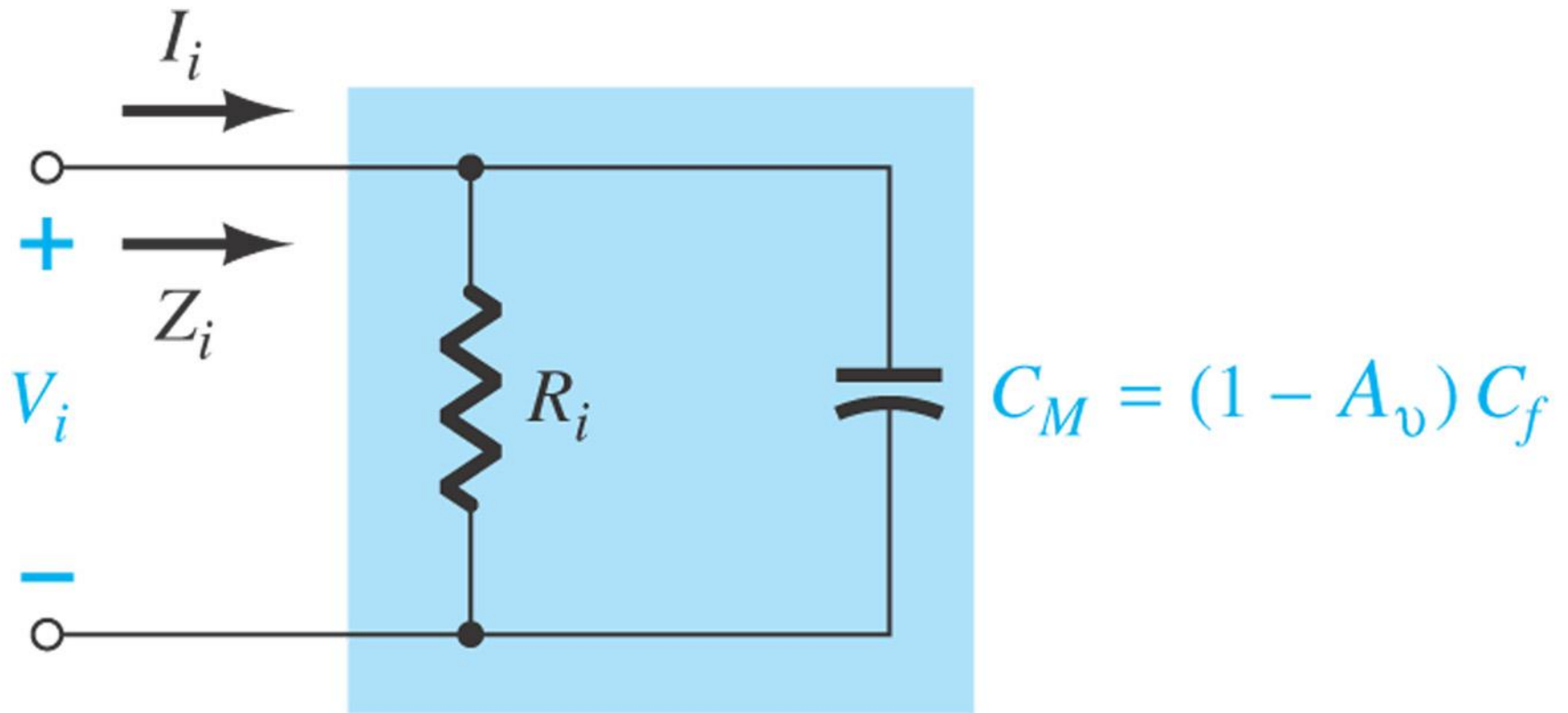Note that the amount of Miller capacitance is dependent on interelectrode capacitance from input to output (C_f) and the gain (A_v).



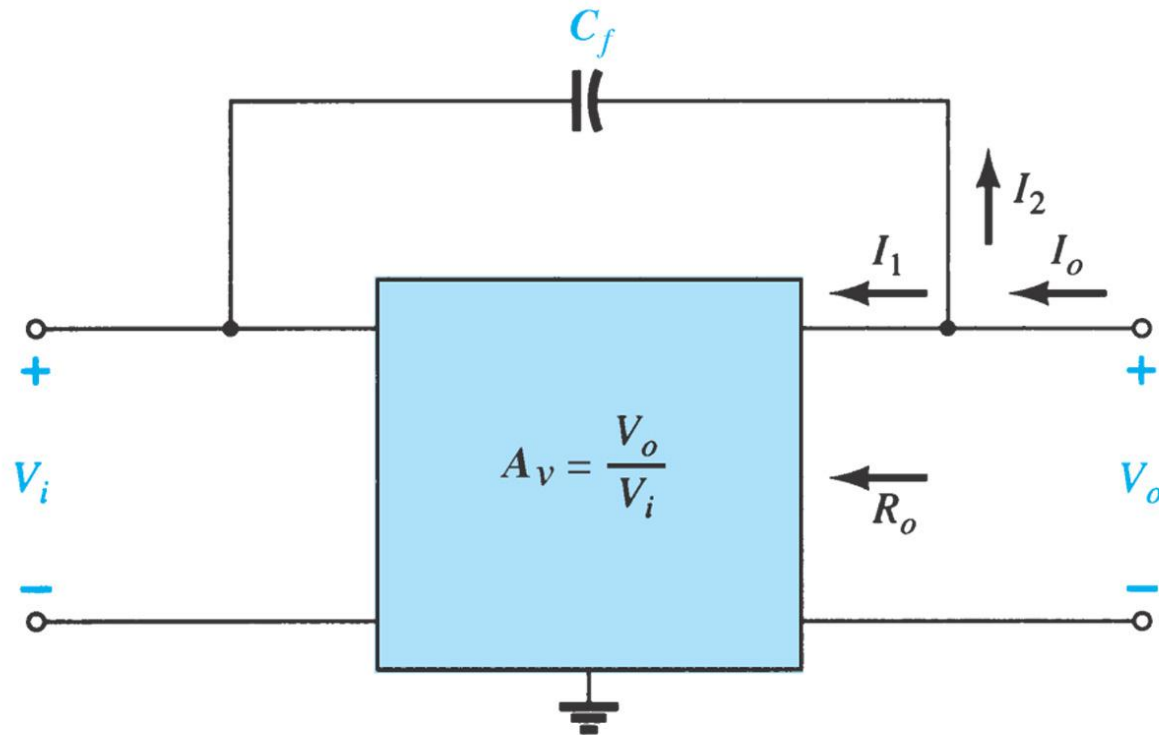

If the gain (A_v) is considerably greater than 1, then

$$C_{M0} \cong C_f$$



Capacitances that affect the high-frequency response are

- **Junction capacitances**

C_{be} , C_{bc} , C_{ce}

- **Wiring capacitances**

C_{wi} , C_{wo}

- **Coupling capacitors**

C_s , C_c

- **Bypass capacitor**

C_E

