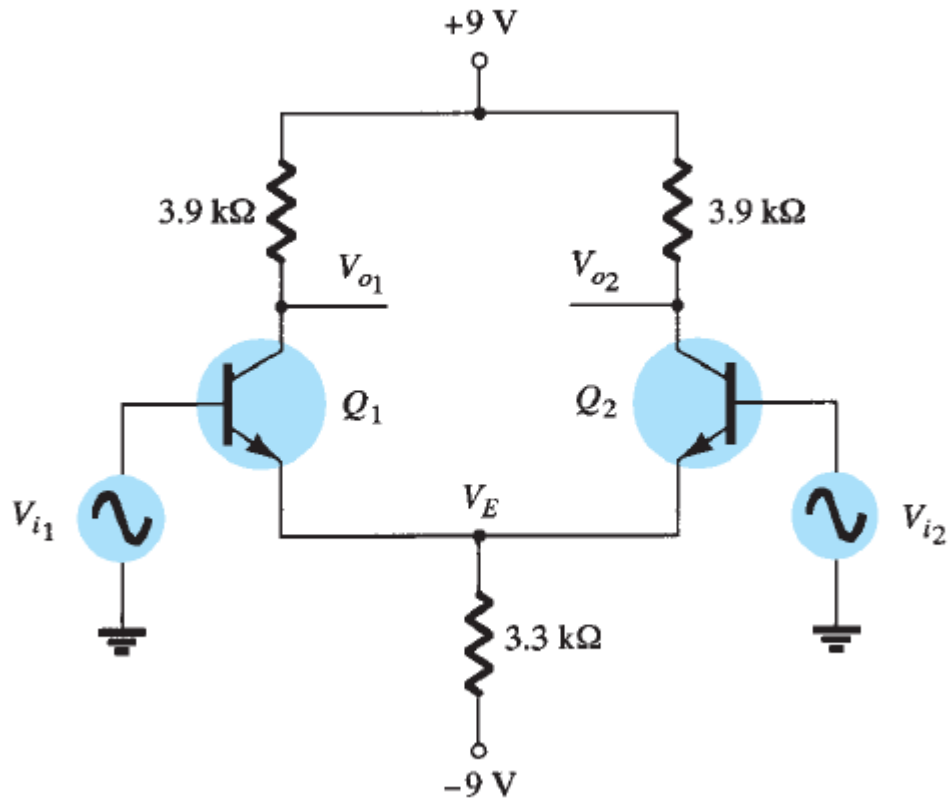


1. Calculate the dc voltages and currents in the circuit and draw the small signal hybrid equivalent model



Solution is example 10.1

**Solution:**

$$\text{Eq. (10.1): } I_E = \frac{V_{EE} - 0.7 \text{ V}}{R_E} = \frac{9 \text{ V} - 0.7 \text{ V}}{3.3 \text{ k}\Omega} \approx 2.5 \text{ mA}$$

The collector current is then


$$\text{Eq. (10.2): } I_C = \frac{I_E}{2} = \frac{2.5 \text{ mA}}{2} = 1.25 \text{ mA}$$

resulting in a collector voltage of

$$\text{Eq. (10.3): } V_C = V_{CC} - I_C R_C = 9 \text{ V} - (1.25 \text{ mA})(3.9 \text{ k}\Omega) \approx 4.1 \text{ V}$$

The common-emitter voltage is thus  $-0.7 \text{ V}$ , whereas the collector bias voltage is near  $4.1 \text{ V}$  for both outputs.

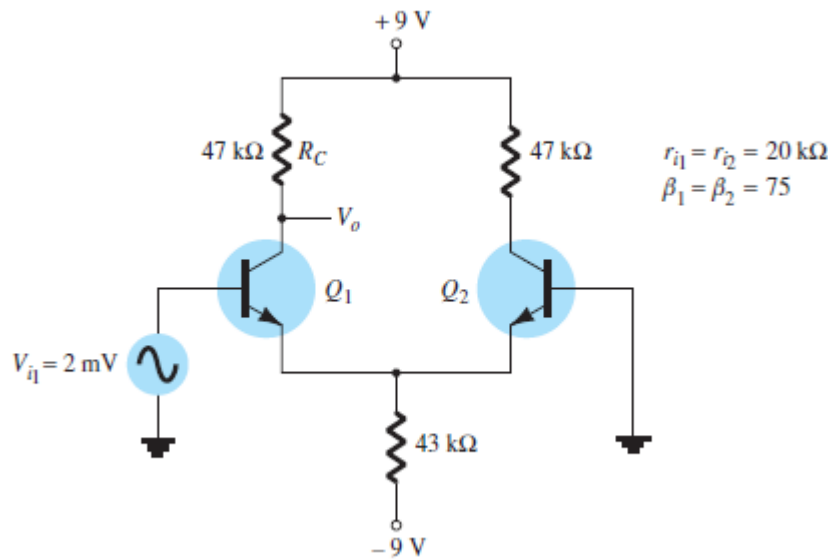2. Calculate the single-ended output voltage  $V_o$  for the circuit and calculate the differential and common mode gain and the CMRR



Solution is example 10.2 and 10.3

**Solution:** The dc bias calculations provide

$$I_E = \frac{V_{EE} - 0.7 \text{ V}}{R_E} = \frac{9 \text{ V} - 0.7 \text{ V}}{43 \text{ k}\Omega} = 193 \mu\text{A}$$

The collector dc current is then

$$I_C = \frac{I_E}{2} = 96.5 \mu\text{A}$$

so that  $V_C = V_{CC} - I_C R_C = 9 \text{ V} - (96.5 \mu\text{A})(47 \text{ k}\Omega) = 4.5 \text{ V}$

The value of  $r_e$  is then

$$r_e = \frac{26}{0.0965} \cong 269 \Omega$$

The ac voltage gain magnitude can be calculated using Eq. (10.31):

$$A_v = \frac{R_C}{2r_e} = \frac{(47 \text{ k}\Omega)}{2(269 \Omega)} = 87.4$$

providing an output ac voltage of magnitude

$$V_o = A_v V_i = (87.4)(2 \text{ mV}) = 174.8 \text{ mV} = 0.175 \text{ V}$$


**EXAMPLE 10.3** Calculate the common-mode gain for the amplifier circuit of Fig. 10.17.

**Solution:**

$$\text{Eq. (10.6): } A_c = \frac{V_o}{V_i} = \frac{\beta R_C}{r_i + 2(\beta + 1)R_E} = \frac{75(47 \text{ k}\Omega)}{20 \text{ k}\Omega + 2(76)(43 \text{ k}\Omega)} = 0.54$$

The CMRR is  $A_d/A_c = 87.4/0.54 = 162$

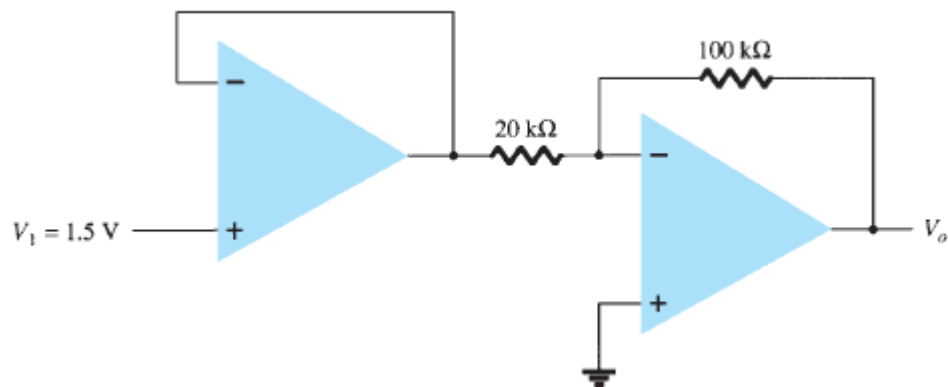3. Calculate the output voltage of the circuit



Solution

$$V_o = -\frac{R_f}{R_i} V_1 = -\frac{100 \text{ k}\Omega}{20 \text{ k}\Omega} (1.5 \text{ V})$$

$$= -5(1.5 \text{ V}) = -7.5 \text{ V}$$

4. For an op-amp having a slew rate of  $SR = 2.4 \text{ V}/\mu\text{s}$ , what is the maximum closed-loop voltage gain that can be used when the input signal varies by  $0.3 \text{ V}$  in  $10 \text{ ms}$ ?

$$A_{CL} = \frac{SR}{\Delta V_i / \Delta t} = \frac{2.4 \text{ V}/\mu\text{s}}{0.3 \text{ V}/10 \mu\text{s}} = 80$$

5. For an input of  $V_i = 50 \text{ mV}$  in the circuit, determine the maximum frequency that may be used. The op-amp slew rate  $SR = 0.4 \text{ V}/\mu\text{s}$ .

$$A_{CL} = \frac{R_f}{R_i} = \frac{200 \text{ k}\Omega}{2 \text{ k}\Omega} = 100$$

$$K = A_{CL} V_i = 100(50 \text{ mV}) = 5 \text{ V}$$


$$\omega_s \leq \frac{SR}{K} = \frac{0.4 \text{ V}/\mu\text{s}}{5 \text{ V}} = 80 \times 10^3 \text{ rad/s}$$

$$f_s = \frac{\omega_s}{2\pi} = \frac{80 \times 10^3}{2\pi} = 12.73 \text{ kHz}$$

6. Using the specifications listed in the table below , calculate the typical offset voltage for the circuit below

$\mu A741$  Electrical Characteristics:  $V_{CC} = \pm 15\text{ V}$ ,  $T_A = 25^\circ\text{C}$

Characteristic	Minimum	Typical	Maximum	Unit
$V_{IO}$ Input offset voltage		1	6	mV
$I_{IO}$ Input offset current		20	200	nA
$I_{IB}$ Input bias current		80	500	nA
$V_{ICR}$ Common-mode input voltage range	$\pm 12$	$\pm 13$		V
$V_{OM}$ Maximum peak output voltage swing	$\pm 12$	$\pm 14$		V
$A_{VD}$ Large-signal differential voltage amplification	20	200		V/mV
$r_i$ Input resistance	0.3	2		M $\Omega$
$r_o$ Output resistance		75		$\Omega$
$C_i$ Input capacitance		1.4		pF
CMRR Common-mode rejection ratio	70	90		dB
$I_{CC}$ Supply current		1.7	2.8	mA
$P_D$ Total power dissipation		50	85	mW

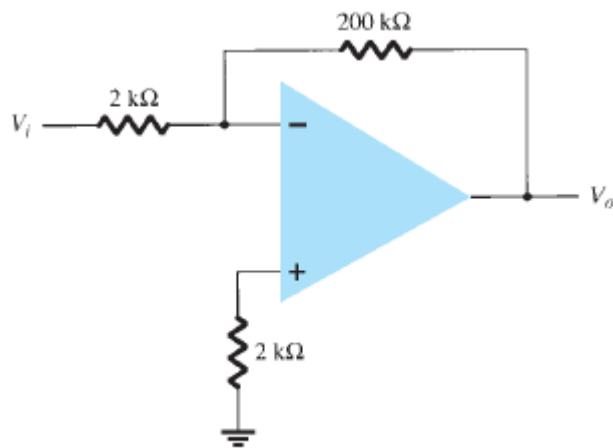

$V_{Io} = 1\text{ mV}$ , typical

$I_{Io} = 20\text{ nA}$ , typical

$$\begin{aligned}
 V_o(\text{offset}) &= 1 + \frac{R_f}{R_i} V_{Io} + I_{Io} R_f \\
 &= 1 + \frac{200\text{ k}\Omega}{20\text{ k}\Omega} (1\text{ mV}) + (200\text{ k}\Omega)(20\text{ nA}) \\
 &= 101(1\text{ mV}) + 4000 \times 10^{-6} \\
 &= 101\text{ mV} + 4\text{ mV} = \mathbf{105\text{ mV}}
 \end{aligned}$$

7. For the typical characteristics of the 741 op-amp, calculate the following values for the circuit above
- $A_{CL}$ .
  - $Z_i$ .
  - $Z_o$ .

Typical characteristics for 741

$$R_o = 25 \, \Omega, A = 200 \, K$$

$$(a) \quad A_{CL} = -\frac{R_f}{R_1} = -\frac{200 \, k\Omega}{2 \, k\Omega} = \mathbf{-100}$$

$$(b) \quad Z_i = R_1 = \mathbf{2 \, k\Omega}$$

$$(c) \quad Z_o = \frac{R_o}{1 + \beta A} = \frac{25 \, \Omega}{1 + \frac{1}{100}(200,000)}$$

$$= \frac{25 \, \Omega}{2001} = \mathbf{0.0125 \, \Omega}$$